

#1	#2	#3	#4


- Open-book, one 8.5 by 11 inch page of handwritten notes (two sided)
- Write all your work and answers on the exam sheet
- | |
|---|
| Clearly mark results with a box around them |
|---|
- Show your work (large and small-signal circuit diagrams, design equations)
- ~~Cross-out incorrect answers.~~ If you present two or more inconsistent answers we invariably grade the wrong one.
- All problems have equal weight.
- Notation: $V_x = V_X + v_x$, where V_X is the large signal bias and v_x is the small signal value.
- The math is trivial for all problems, if approached correctly. This is not a course about complicated algebra and calculus! Even I could solve the problems, and I had many years to forget whatever math I learned.

Use the following parameters in all problems, unless otherwise specified:

Device	Parameter values
BJT	$I_s = 1 \text{ fA}$, $\beta = 100$, and $V_A = 100 \text{ V}$
NMOS	$ V_{TH} = 400 \text{ mV}$, $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, $\lambda = 0.02 \text{ V}^{-1}$, $\gamma = 0 \text{ V}$.
PMOS	$ V_{TH} = 400 \text{ mV}$, $\mu_p C_{ox} = \mathbf{100} \mu\text{A}/\text{V}^2$, $\lambda = 0.02 \text{ V}^{-1}$, $\gamma = 0 \text{ V}$.


Unless otherwise specified, assume room temperature and $V_t = 25 \text{ mV}$.

 1. Calculate the small-signal output resistance R_o at terminal V_o of the circuit below. The circuit is biased such that the large signal output voltage $V_O = 1$ V.
 - a) Draw the small-signal model and calculate the numerical values of all small-signal parameters.
 - b) Derive an algebraic expression for R_o . You may use the shorthand $r_x \parallel r_y$.
 - c) Calculate the numerical value of R_o .




Use $V_{CC} = 3$ V, $R_1 = 1$ k Ω , $R_2 = 5$ k Ω , $I_1 = 500$ μ A.

 2. Determine the value of V_G such that the channel resistance (resistance between the source and the drain of M_1) is $1\text{ k}\Omega$ for $V_i = 2\text{ V}$ and $I_D = 0\text{ A}$.
Use $W_1 = 2\text{ }\mu\text{m}$ and $L_1 = 180\text{ nm}$.



3. Analyze the amplifier shown below for $V_{dd} = 3\text{ V}$, $V_O = V_{dd}/2$, $W_1 = W_2 = 5\ \mu\text{m}$ and $L_1 = L_2 = 350\ \text{nm}$. M_2 is biased in saturation.
- What is the region of operation of M_1 ?
 - Draw the small-signal model and calculate the values of all small-signal parameters. Beware: $|V_{DS1}| \ll |2(V_{GS1} - V_{TH})|$.
 - Derive an algebraic expression for the small-signal voltage gain $a_v = v_o/v_i$. You may use the shorthand $r_x \parallel r_y$.
 - Calculate the value of a_v .

 

4. Design a circuit such that $v_o = r_x i_s$ with $r_x = 10\text{ k}\Omega \pm 2\%$ using a single NPN transistor ($V_A = 0\text{ V}$) and as many resistors and (ideal) bias sources (current or voltage) as you like (fewer is better and helps avoid mistakes). The value of R_s varies in the range $1 \dots 10\text{ M}\Omega$. The source i_s is a reverse biased diode and requires V_s in the range $2\text{ V} \leq V_s \leq 3\text{ V}$ to work properly. Stay close to the minimum power dissipation (not more than $2\times$).

Use the following sequence (you may need to iterate):

- Determine the type of amplifier configuration (CE, CB, CC) best suited for this problem.
- Draw a prototype large signal model including all biasing elements. You may need to iterate, e.g. modify or add biasing elements during the design process.
- Draw the small-signal diagram and determine the small-signal parameters required to meet the specifications.
- Calculate the large signal parameters including the values of all bias sources.
- Verify that your circuit meets the specifications. You get points for this, even if you determine that you miss a spec and run out of time (or ideas) for addressing the problem.

