

Hello

Advanced Analog Integrated Circuits


Electronic Noise

Bernhard E. Boser

University of California, Berkeley


boser@eecs.berkeley.edu

Copyright © 2016 by Bernhard Boser

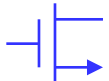

Types of Noise

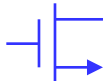
- Interference, “Man-made” Noise
 - Substrate coupling
 - Supply noise
 - Signal coupling
 - Solutions:
 - Fully differential circuits
 - Layout techniques
 - Shielding
- Electronic noise
 - Fundamental physics based
 - Thermal and shot noise ← Focus of this discussion
 - Technology related
 - Flicker noise (see later), drift




Noisy Signals

$$\text{Information} = \boxed{\text{DR}} \cdot \text{BW}$$



↑
harmful noise

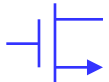

Thermal Noise Manifestations

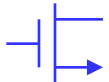


Example: Resistor

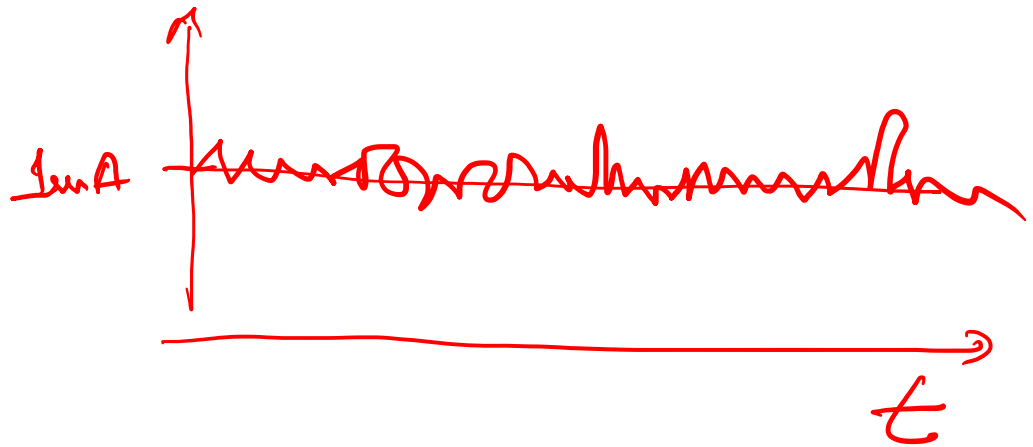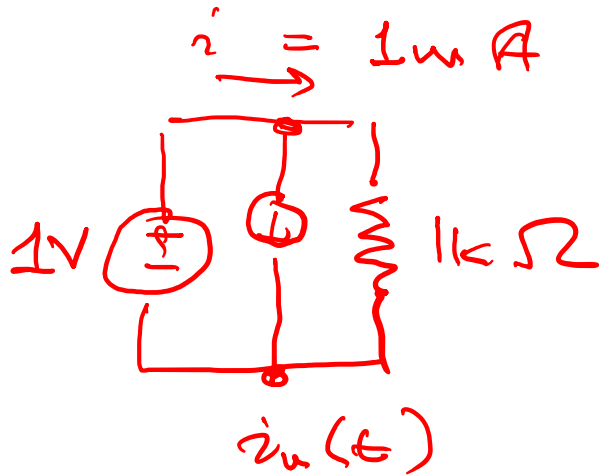


- J. B. Johnson, "Thermal Agitation of Electricity in Conductors," Phys. Rev., pp. 97-109, July 1928.

Properties of Thermal Noise


- All "dissipative systems"

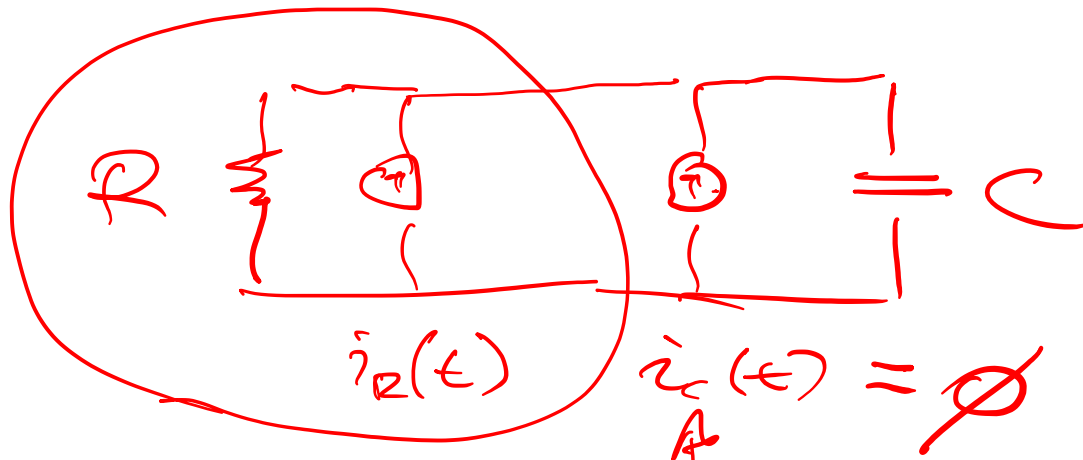

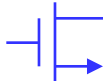- * indep of current flow
- * zero mean
- * iid
- * average power



Thermal Noise Power Spectrum

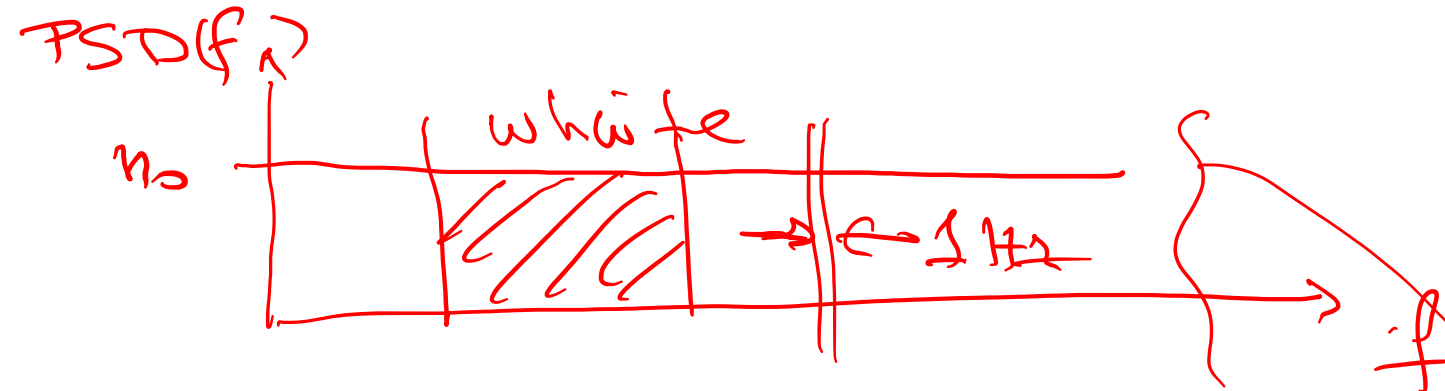

$$PSD(f) = n_0 = 4k_B \cdot T \cdot T \cdot f^2$$


$$= 2 \cdot 10^{-20} \text{ J} \quad [\text{W/Hz}]$$

@ 100 °C

noise in Δf

$$P_n = \int_{f_1}^{f_2} PSD \cdot df$$

$$= 4k_B T \cdot \Delta f$$

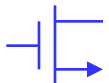

Advanced Analog Integrated Circuits


Modeling Noise

Bernhard E. Boser

University of California, Berkeley


boser@eecs.berkeley.edu

Copyright © 2016 by Bernhard Boser

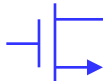

Resistor Noise Models

$$\overline{v_n^2} = 4k_B T R \Delta f$$

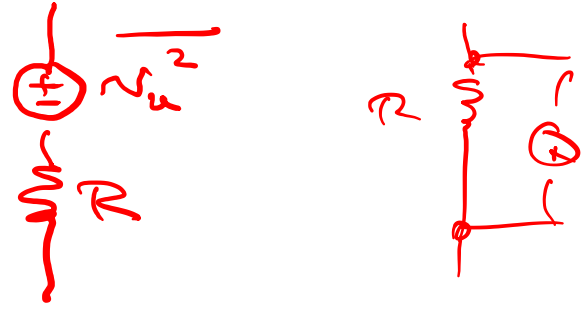

$$\overline{i_n^2} = \frac{P_n}{R \Delta f}$$

$$R = 1 \text{ k}\Omega$$


$$\frac{\overline{v_n^2}}{\Delta f}$$

$$= 4 \frac{\mu\text{V}}{\sqrt{\text{Hz}}}$$

$$\Delta f = 1 \text{ MHz}$$


$$\overline{v_n^2}$$

$$= 4 \mu\text{V rms}$$

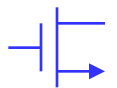


Sloppy Nomenclature


- For convenience, noise in circuits is usually represented by the mean squared noise voltage $\overline{v_n^2}$ or current $\overline{i_n^2}$
- It is customary to refer to these quantities as “noise power”, especially when comparing them to signals which are usually represented by voltages or currents, not power
- The actual noise power is easily obtained by dividing or multiplying the mean squared values by the resistance

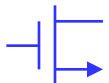


Resistors in Series

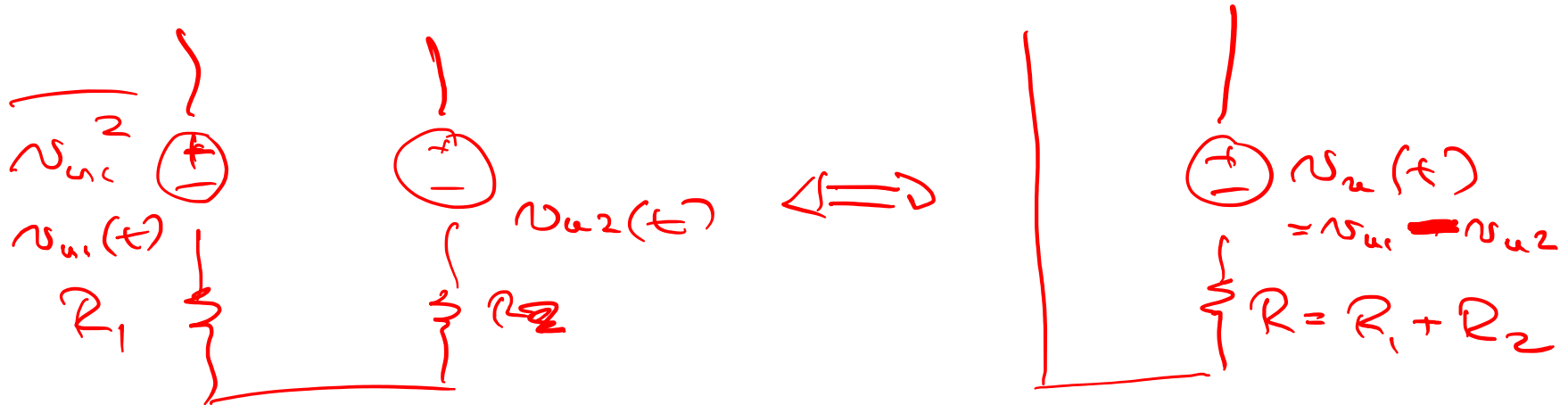
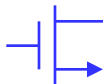
$$\begin{aligned}
 \overline{v_u^2} &= \overline{(v_{u1} - v_{u2})^2} \\
 &= \overline{v_{u1}^2} + \overline{v_{u2}^2} - \cancel{2v_{u1}v_{u2}} \\
 &= 4kT \cdot (R_1 + R_2) \cdot \Delta f
 \end{aligned}$$



Signal-to-Noise Ratio

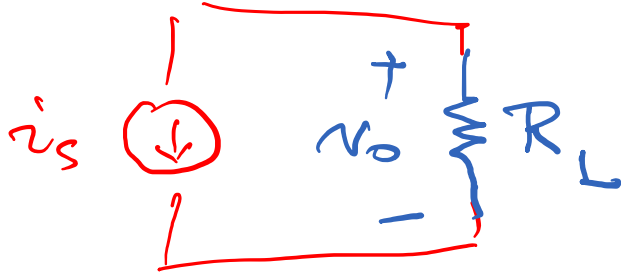

$$P_s = \frac{1}{2} I_s^2 \cdot R_L$$

$$P_n = 4 kT \cdot \Delta f \cdot R_L$$


$$SNR = \frac{P_s}{P_n} = \frac{\frac{1}{2} I_s^2 \cdot R_L}{4 kT \cdot \Delta f \cdot R_L}$$

$$P_{s, \text{min}} = 4 kT \cdot$$

60 dB
SNR · Δf

↑
I_a f_o


$$= 2 \text{ nW}$$

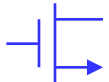


Noise Bandwidth

a) BW set by app \leftarrow rec.
human ear

b) Total noise $0 - \infty$ Hz

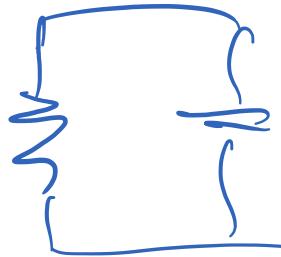

Band-Limited Noise Example

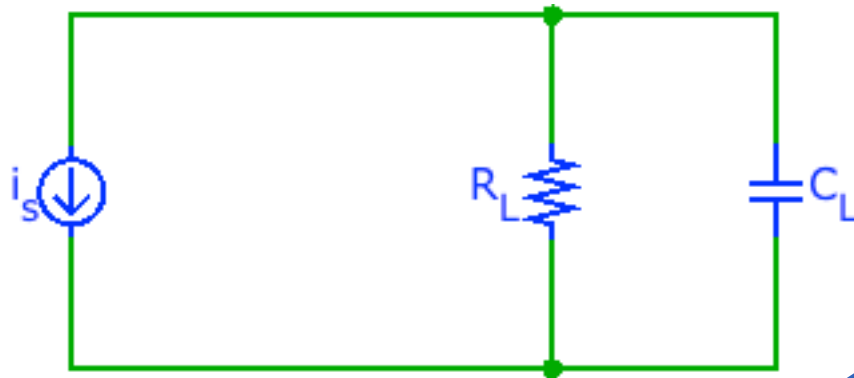


$$v_o = \frac{R_L}{1 + j\omega R_L C} i_s$$

PSD




$$\frac{v_o^2}{\Delta f} = \frac{i_s^2}{\Delta f} \cdot \left| \frac{R_L}{1 + j\omega R_L C} \right|^2$$

$$v_{out}^2 = \int_0^{\infty} \frac{i_s^2}{\Delta f} \cdot \left| \frac{R_L}{1 + j\omega R_L C} \right|^2 \cdot \Delta f$$

$$= \frac{kT}{C}$$

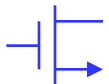

RC Noise Spectral Density

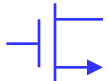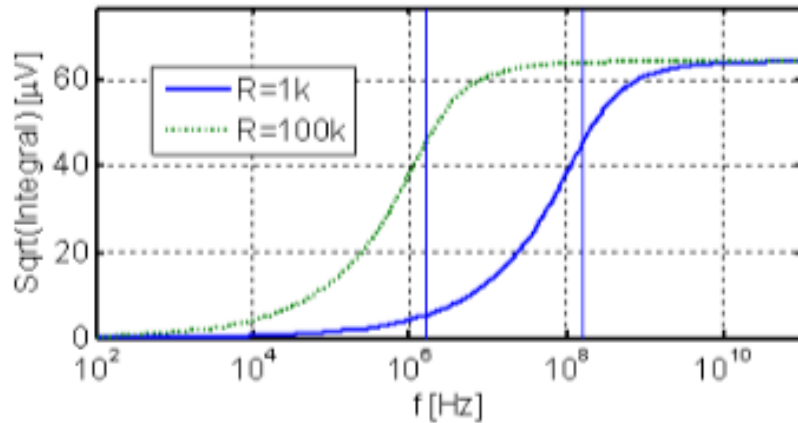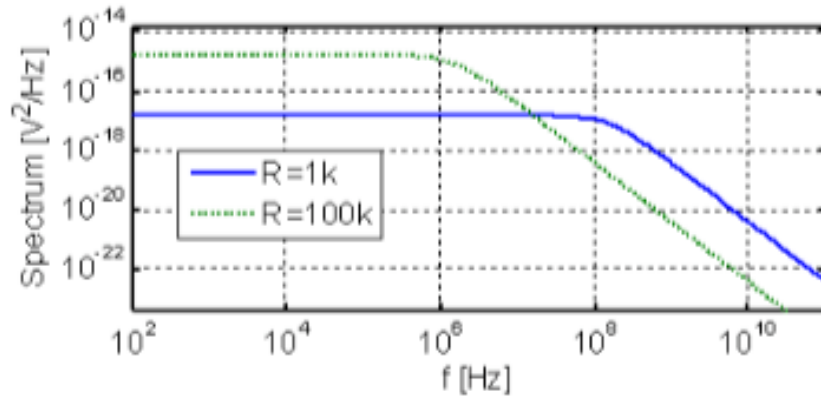

Useful Integrals

$$\int_0^{\infty} \left| \frac{1}{1 + \frac{s}{\omega_o}} \right|^2 df = \frac{\omega_o}{4}$$

$$\int_0^{\infty} \left| \frac{1}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \frac{\omega_o Q}{4}$$


$$\int_0^{\infty} \left| \frac{\frac{s}{\omega_o}}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \frac{\omega_o Q}{4}$$

Generalization in


A. Dastgheib and B. Murmann, "Calculation of Total Integrated Noise in Analog Circuits," IEEE TCAS1, vol. 55, no. 10, pp. 2988-2993, Oct. 2008.



Equipartition Theorem

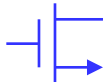

Equivalent Noise Bandwidth

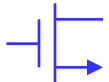

Advanced Analog Integrated Circuits


Noise–Power Tradeoff

Bernhard E. Boser


University of California, Berkeley

boser@eecs.berkeley.edu



Copyright © 2016 by Bernhard Boser

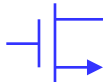

Analog versus Digital SNR

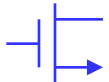


Representative Circuit

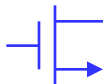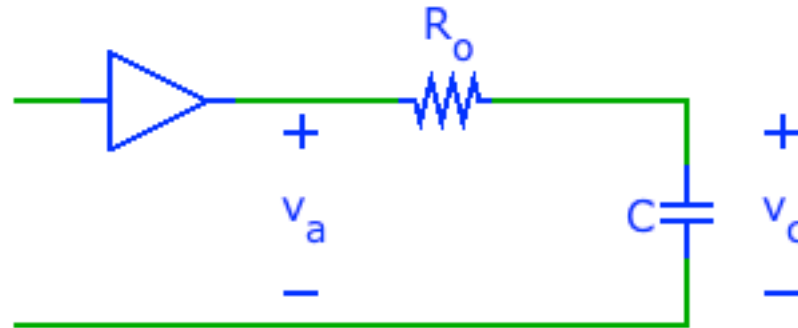


Peak SNR versus Capacitance

- SNR versus C for 1-V sinusoidal signal at 100°C

Bits	SNR [dB]	C	
3.0	20	4.1 aF	
6.3	40	412 aF	
9.7	60	41 fF	
13.0	80	4.1 pF	
16.3	100	412 pF	
19.6	120	41 nF	
23.0	140	4.1 μ F	

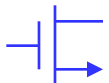

Aside: Oversampling

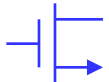

Noise-Power Tradeoff



Advanced Analog Integrated Circuits


Noise Representations

Bernhard E. Boser


University of California, Berkeley

boser@eecs.berkeley.edu

Copyright © 2016 by Bernhard Boser

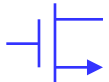


Noise Representations

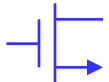

Output and Input Referred Noise


Output

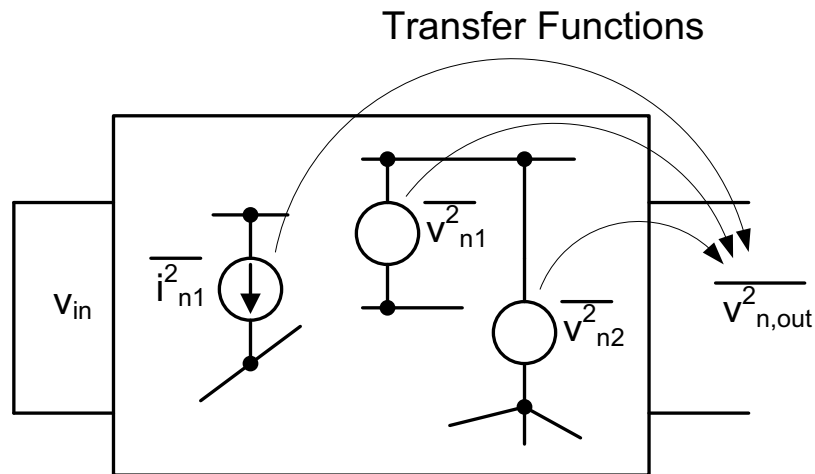

$$v_{out} = H_i \cdot S_{n,i}$$


$$\overline{v_{n,out}^2} = \sum_i |H_i|^2 \overline{S_{n,i}^2}$$

Input

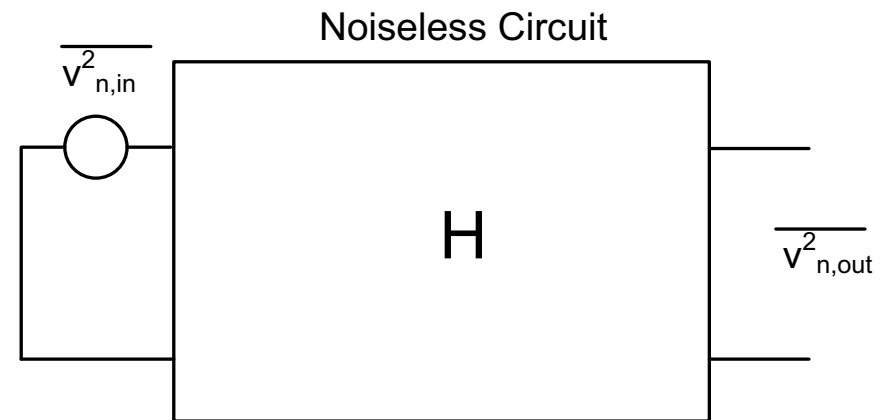


$$v_{out} = H \cdot v_{in}$$


$$\overline{v_{n,in}^2(\omega)} = \frac{\overline{v_{n,out}^2(\omega)}}{|H|^2}$$

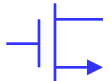


Minimum Detectable Signal

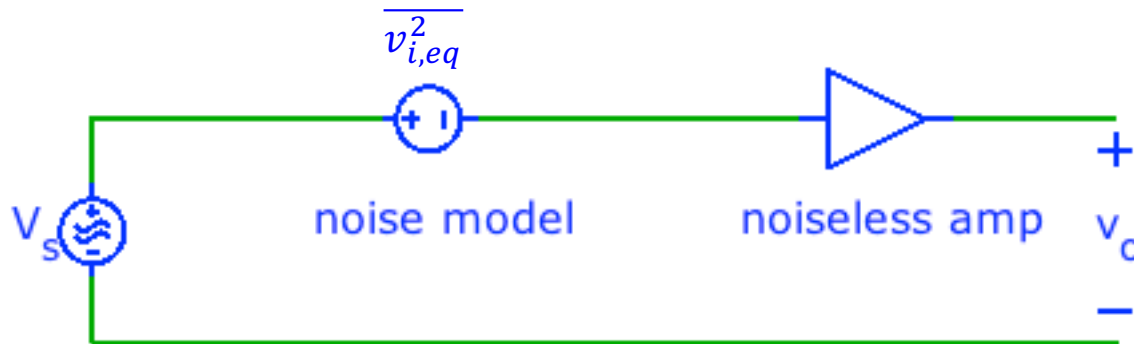


Source Impedance

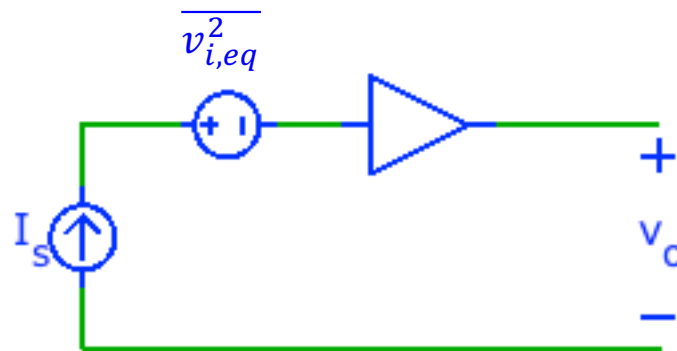

Equivalent Input Current Noise

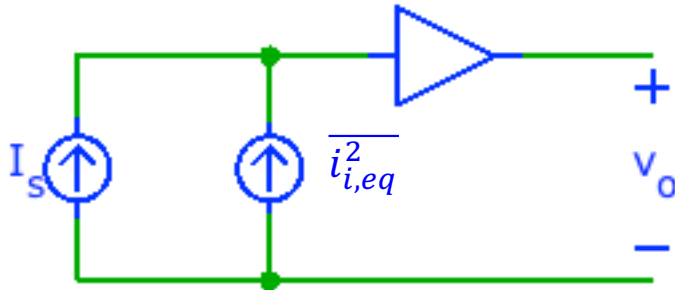


Input Voltage and Current Noise Sources

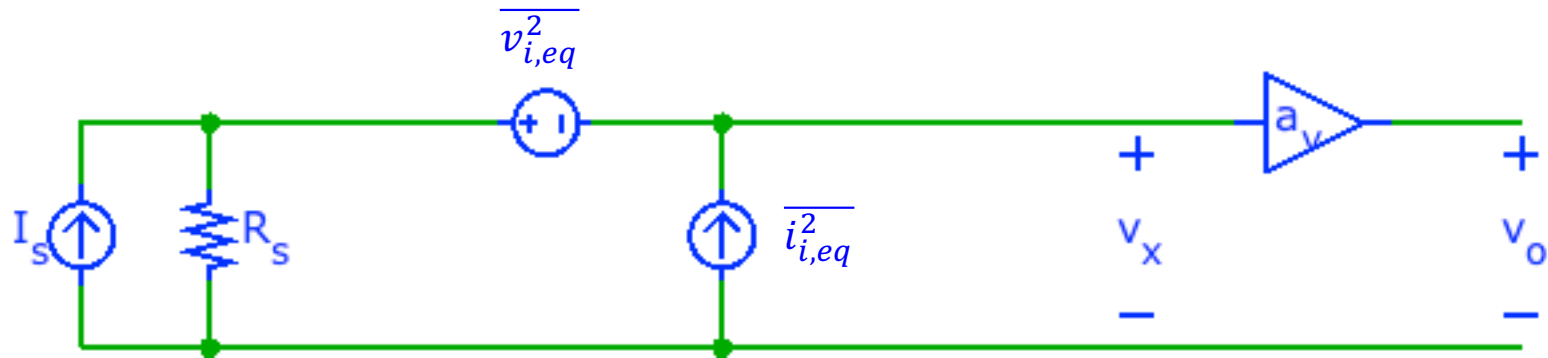

Correlated Noise

- Counting some of noise twice
 - When noise sources are correlated
 - And both noise sources matter (i.e. contribute similarly to the noise at the output of the circuit)
- Situations:
 - a) Custom circuit with known R_S :
Represent input referred noise with one source for a specific R_S
 - b) General purpose circuit (e.g. opamp)
Need to consider correlation in noise calculations *if* both sources matter (rare)

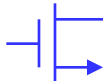

Examples

BJT Opamp

LT1115 - Ultra-Low Noise

Input Noise Voltage Density	$f_0 = 10\text{Hz}$	1.0	1.2	$\text{nV}/\sqrt{\text{Hz}}$
	$f_0 = 1000\text{Hz}$	0.9		$\text{nV}/\sqrt{\text{Hz}}$
Wideband Noise	DC to 20kHz	120		nV_{RMS}
Corresponding Voltage Level re 0.775V		-136		dB
Input Noise Current Density (Note 3)	$f_0 = 10\text{Hz}$	4.7	2.2	$\text{pA}/\sqrt{\text{Hz}}$
	$f_0 = 1000\text{Hz}$	1.2		$\text{pA}/\sqrt{\text{Hz}}$

JFET Opamp

OPA827

Input Voltage Noise:

$f = 0.1\text{Hz to } 10\text{Hz}$ 250 nV_{PP}


Input Voltage Noise Density:

$f = 1\text{kHz}$ 4 $\text{nV}/\sqrt{\text{Hz}}$



$f = 10\text{kHz}$ 3.8 $\text{nV}/\sqrt{\text{Hz}}$

Input Current Noise Density:

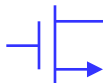$f = 1\text{kHz}$ 2.2 $\text{fA}/\sqrt{\text{Hz}}$



Source Resistance

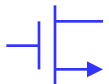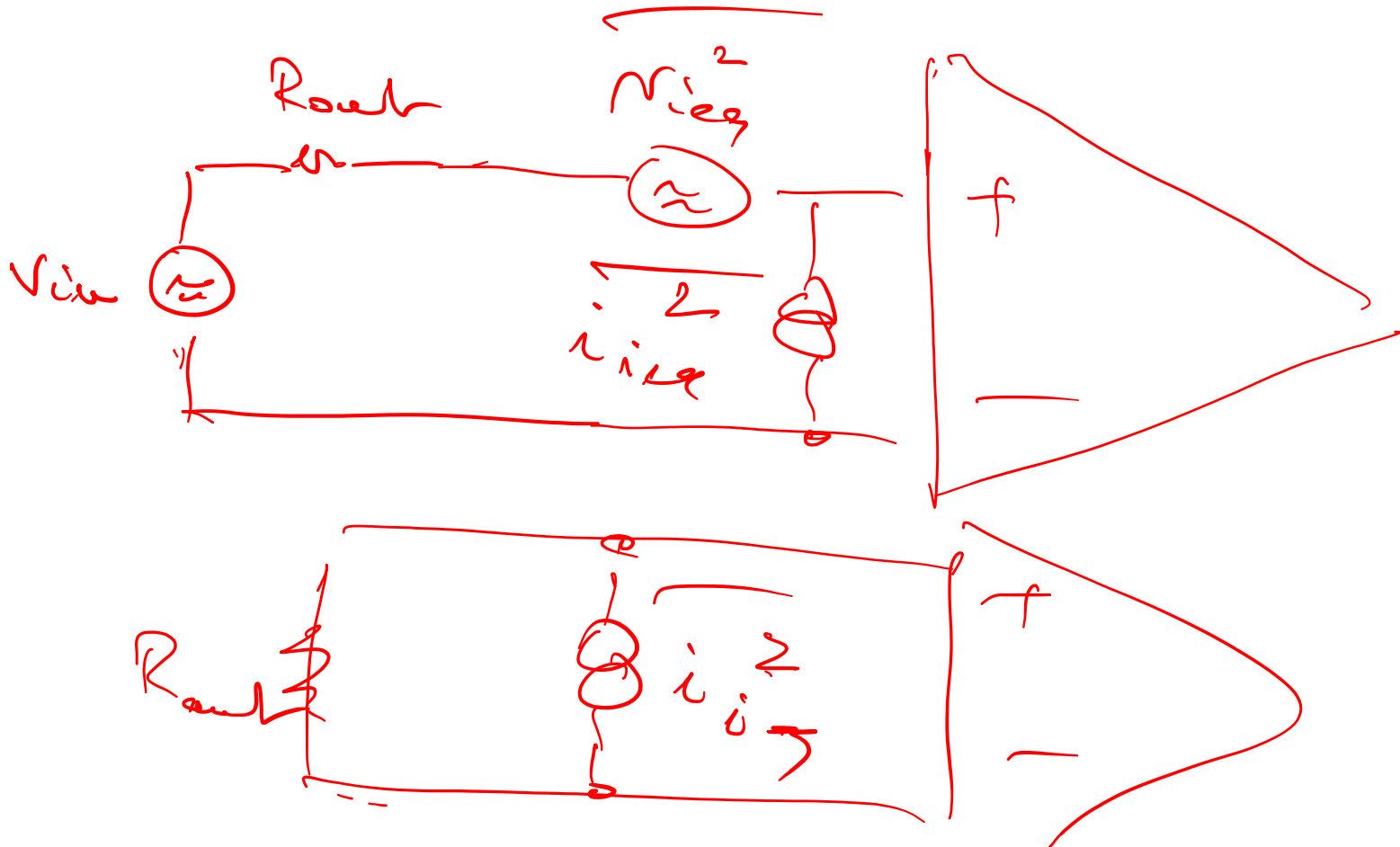

Advanced Analog Integrated Circuits


Noise Calculations – Example

Bernhard E. Boser


University of California, Berkeley

boser@eecs.berkeley.edu

Copyright © 2016 by Bernhard Boser

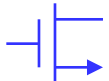

Example: Negative Feedback Amplifier

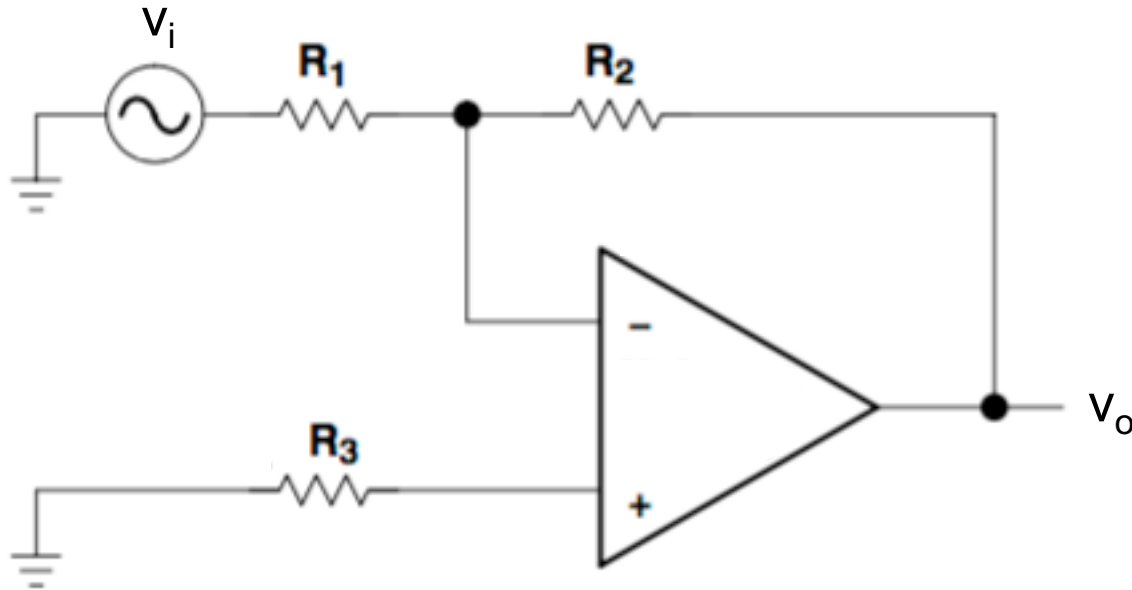


$$v_o = -v_i \frac{R_2}{R_1} = -a_v v_i$$


<http://www.ti.com/lit/an/slva043b/slva043b.pdf>

Noise Model


Opamp

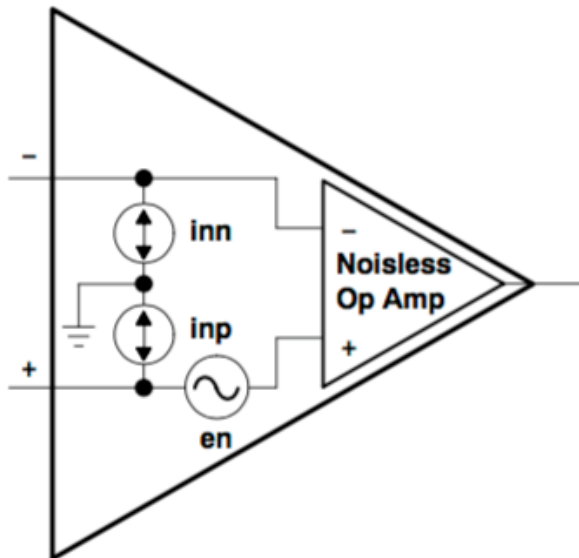

Circuit

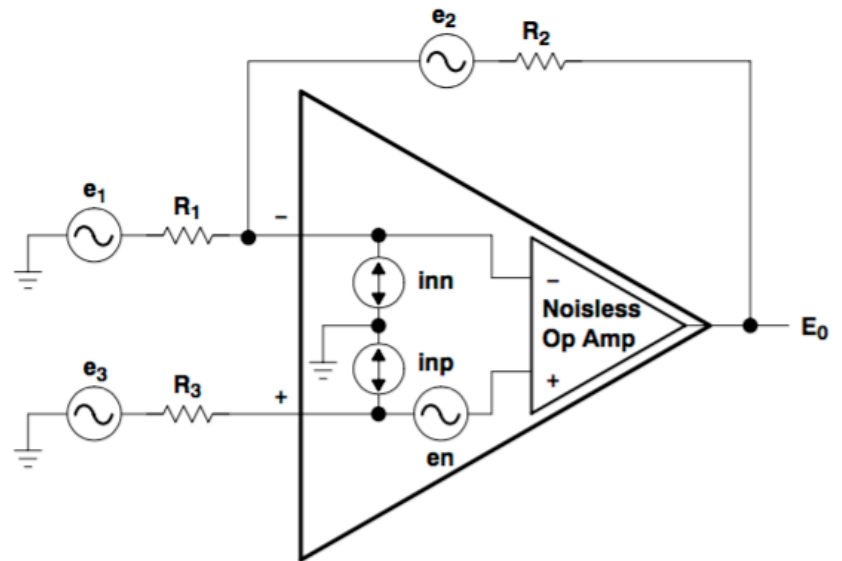


6 noise sources!

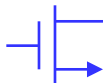

Noise Calculation


- One noise source at a time (linear superposition)

1) Noise at Output from R_1

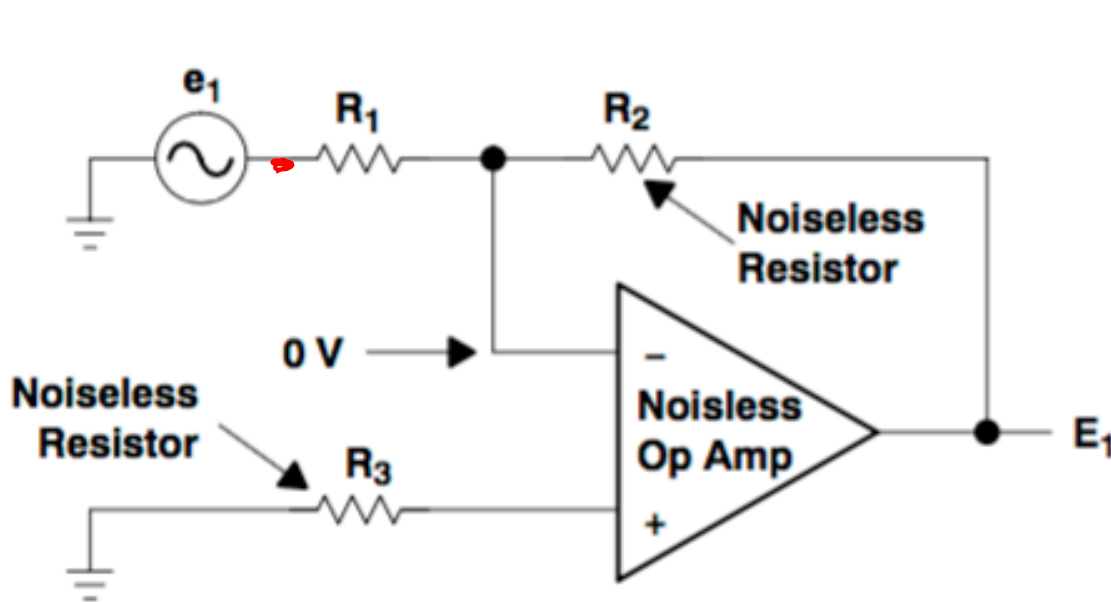



$$\overline{e_{1,o}^2} = \left(\frac{R_2}{R_1} \right)^2 \overline{e_1^2}$$

2) Noise at Output from R_2

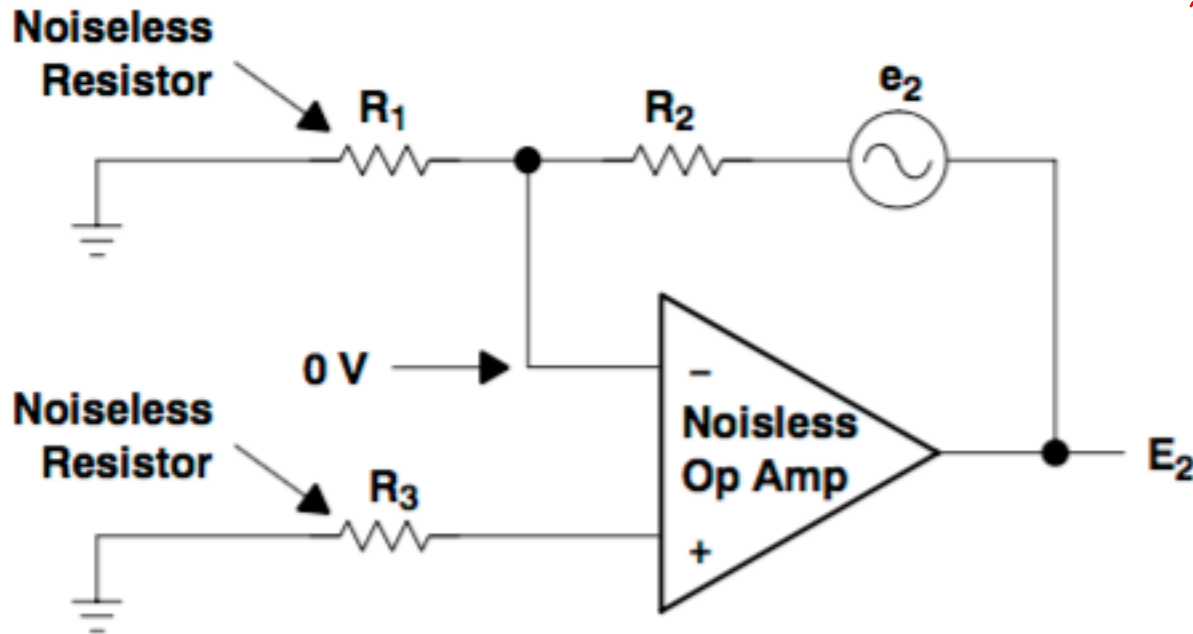

$$e_{2,0}^2 = e_2^2$$


3) Noise at Output from R_3

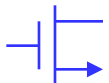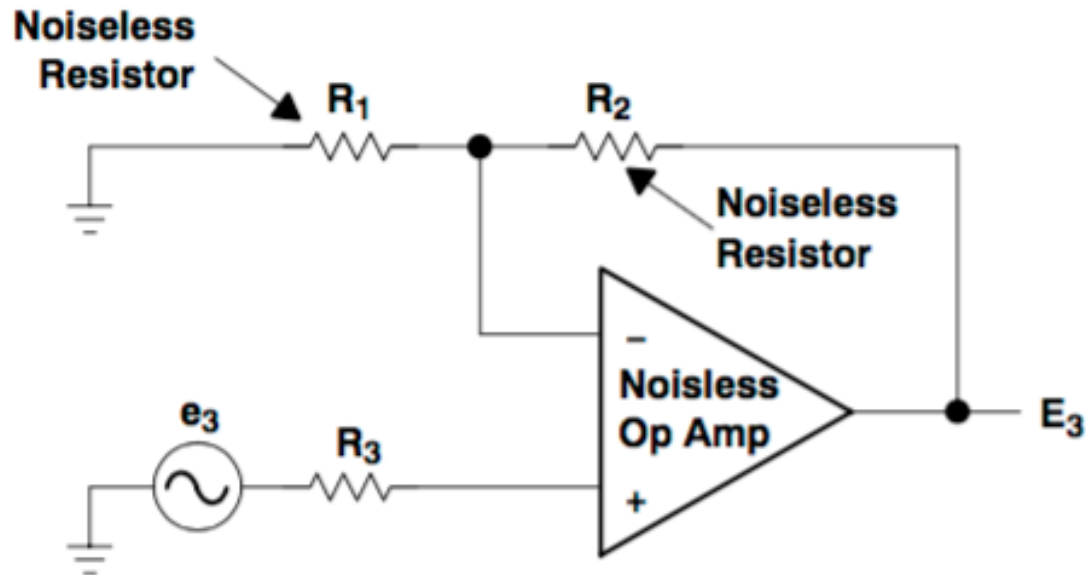


Output Noise from Feedback Network





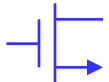
Input Referred Noise from Feedback Network



4) Noise from Opamp Voltage Noise

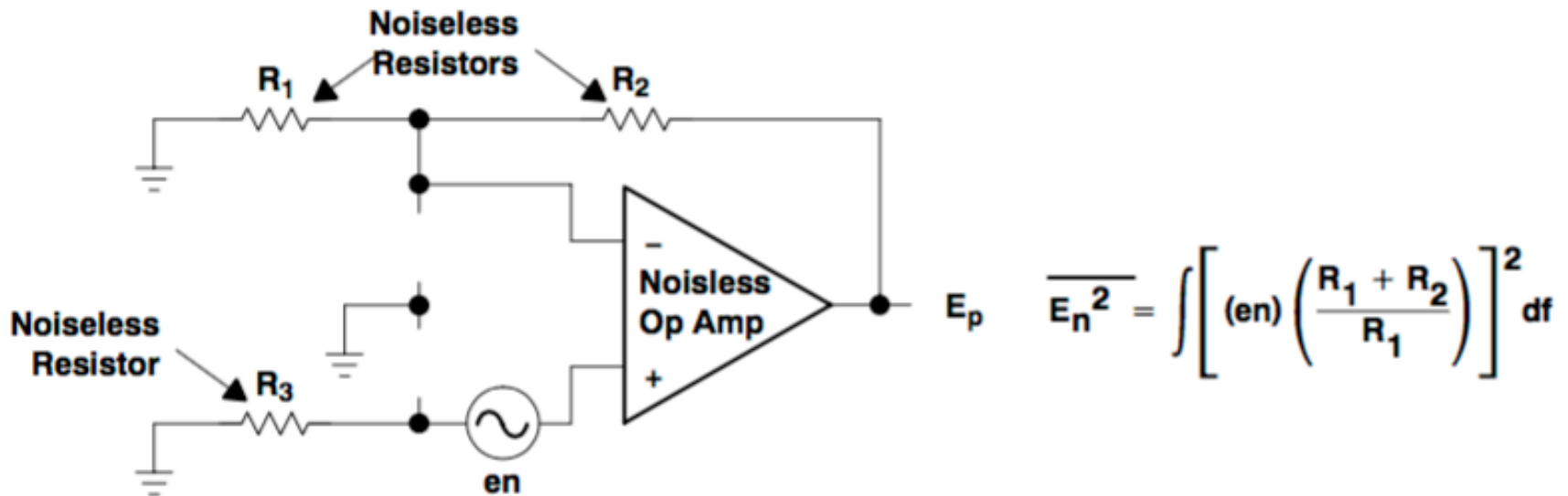


5) Noise from Opamp Current Noise

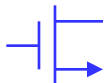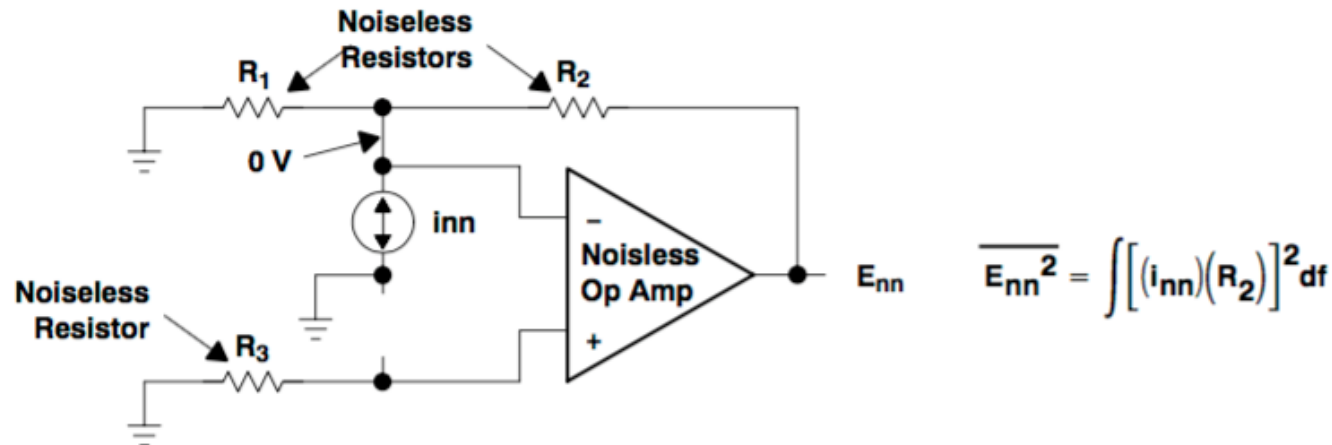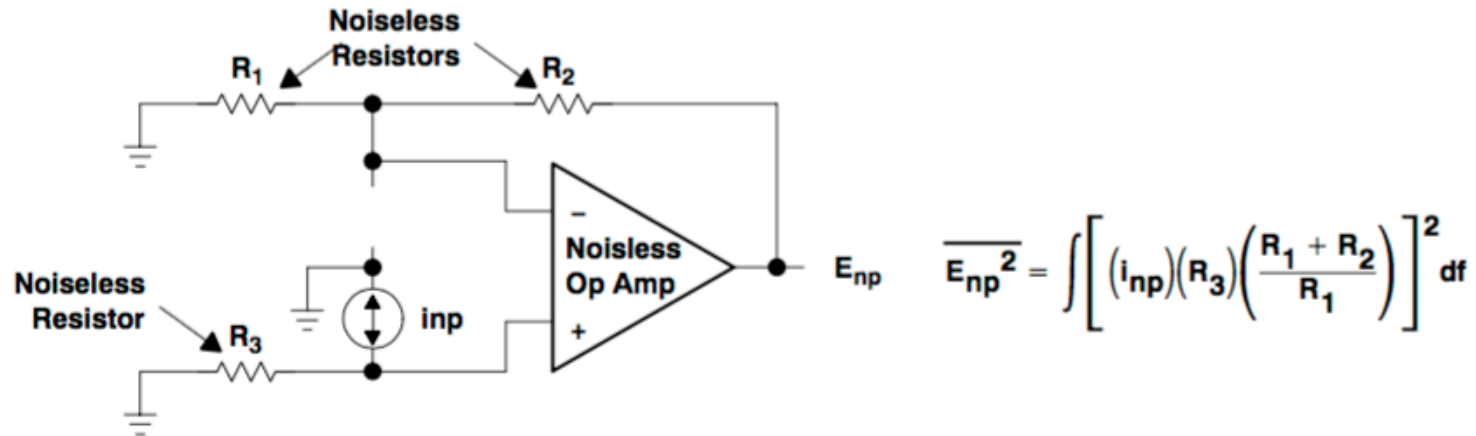

Noise from Opamp

$$\overline{v_{oa,n}^2} = \overline{v_{v,n}^2} \left(\frac{R_1 + R_2}{R_1} \right)^2 + \overline{i_{in,n}^2} R_2^2 \quad \text{for } R_3=0$$
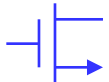
$$\begin{aligned} \overline{v_{if,eq}^2} &= \overline{v_{v,n}^2} \left(\frac{1 + a_v}{a_v} \right)^2 + \overline{i_{in,n}^2} \frac{R_2^2}{a_v^2} \\ &= \overline{v_{v,n}^2} \left(1 + \frac{1}{a_v} \right)^2 + \underbrace{\overline{i_{i,n}^2} R_1^2}_{\text{significant for high } R_s, R_1} \end{aligned}$$



Total Input Referred Noise

$$\overline{v_{i,eq}^2} = \overline{v_{R1,n}^2} \left(1 + \frac{1}{a_v}\right) + \overline{v_{v,n}^2} \left(1 + \frac{1}{a_v}\right)^2 + \overline{i_{i,n}^2} R_1^2$$

Source and feedback resistor Amplifier voltage noise Amplifier current noise

$$\overline{v_{v,n}^2} = 4 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$

$$\overline{i_{i,n}^2} = 1.2 \frac{\text{pA}}{\sqrt{\text{Hz}}} \quad (\text{uncorrelated})$$

a_v large

$$R_1 = 50\Omega$$

$\overline{v_{v,n}^2}$ dominates over $\overline{i_{i,n}^2}$, correlation no concern


$$R_1 = 1\text{M}\Omega$$

$$\frac{\overline{v_{i,eq}^2}}{\Delta f} = \sqrt{\left(0.9 \frac{\text{nV}}{\sqrt{\text{Hz}}}\right)^2 + \left(4 \frac{\text{nV}}{\sqrt{\text{Hz}}}\right)^2 + \left(0.06 \frac{\text{nV}}{\sqrt{\text{Hz}}}\right)^2}$$

$$\frac{\overline{v_{i,eq}^2}}{\Delta f} = \sqrt{\left(126 \frac{\text{nV}}{\sqrt{\text{Hz}}}\right)^2 + \left(4 \frac{\text{nV}}{\sqrt{\text{Hz}}}\right)^2 + \left(1200 \frac{\text{nV}}{\sqrt{\text{Hz}}}\right)^2}$$


Low source resistance:
Voltage noise dominates
Use BJT

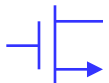High source resistance:
Current noise dominates
Use MOS



Additional Noise Topics

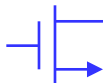- Later in EE 240B
 - Noise in sampled data systems
 - (Low) noise amplifier design ...
 - Flicker noise
- RF noise metrics (EE 242A)
 - Noise figure
 - Receiver sensitivity
 - Phase noise in oscillators
- Cyclostationary noise
 - Noise in circuits with high signal amplitude which modulates the noise power spectral densities
 - E.g. oscillators, mixers, comparators



Summary

- Thermal noise is fundamental
- Random, but accurately described by universal statistics
- Strong correlation between noise and power dissipation for high accuracy analog systems
 - Up to 4x power for each extra bit
- Noise representations
 - PSD at output
 - Total noise at output
 - PSD at input (depends on R_S)
 - Minimum detectable signal (MDS)
- Noise contributions for different R_S
 - High R_S : current noise dominates (FET advantageous)
 - Low R_S : voltage noise dominates (BJT advantageous)

