

Electronics for IoT

H-Bridge

Bernhard E. Boser

University of California, Berkeley

boser@eecs.berkeley.edu


DC Motor Speed (RPM) Control

- Objective: control
 - Direction of Rotation
 - Speed / Torque
- Forward:
 - Vary voltage to set speed
 - E.g. 6V → full speed, 3V → half speed
- Reverse:
 - Flip terminals: e.g. -6V
- Brake: Short terminals
- **Never:** open terminals
 - Why?




DC motor:
2 electrical terminals to apply power

H-Bridge

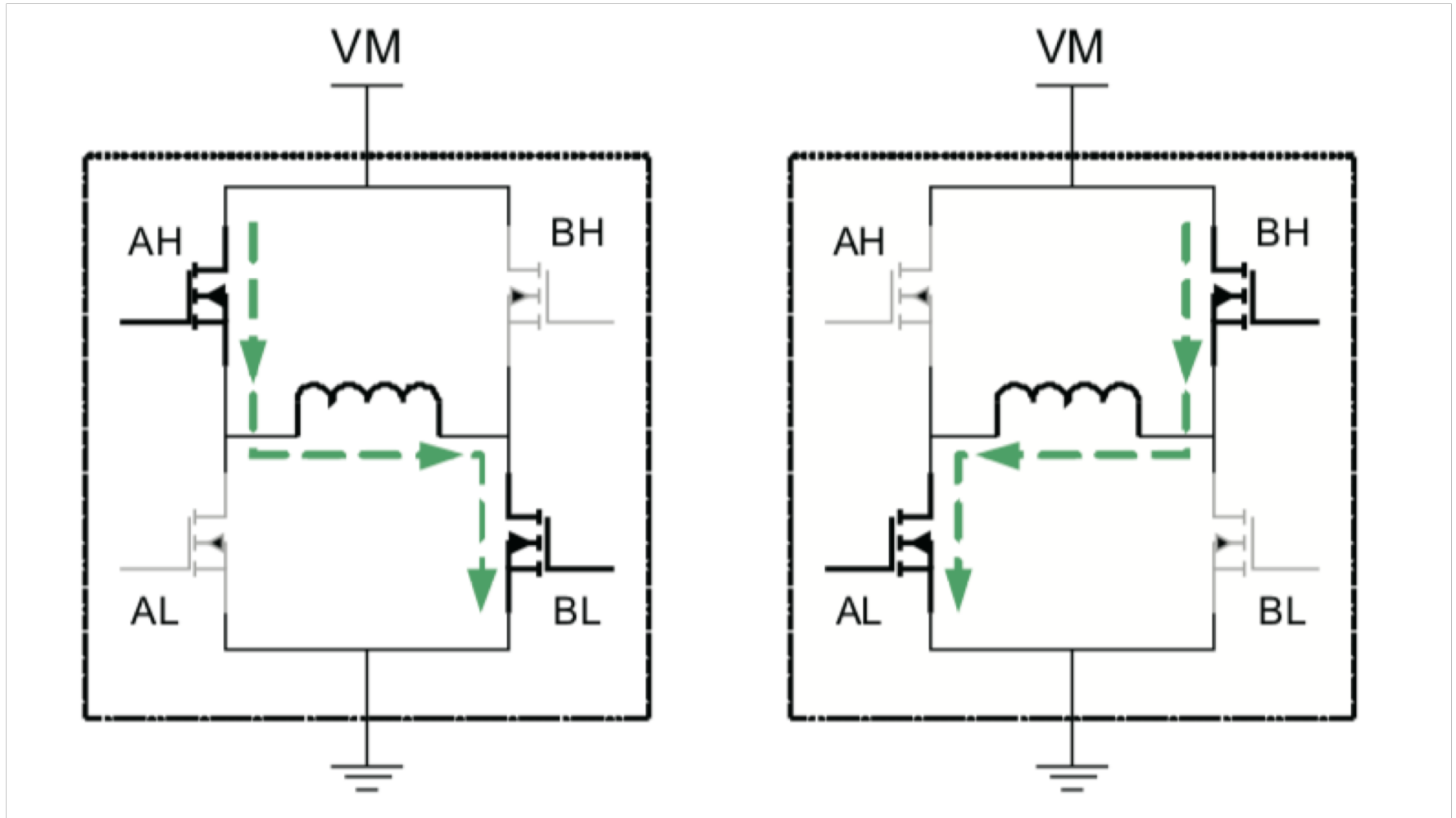


On-Off Control

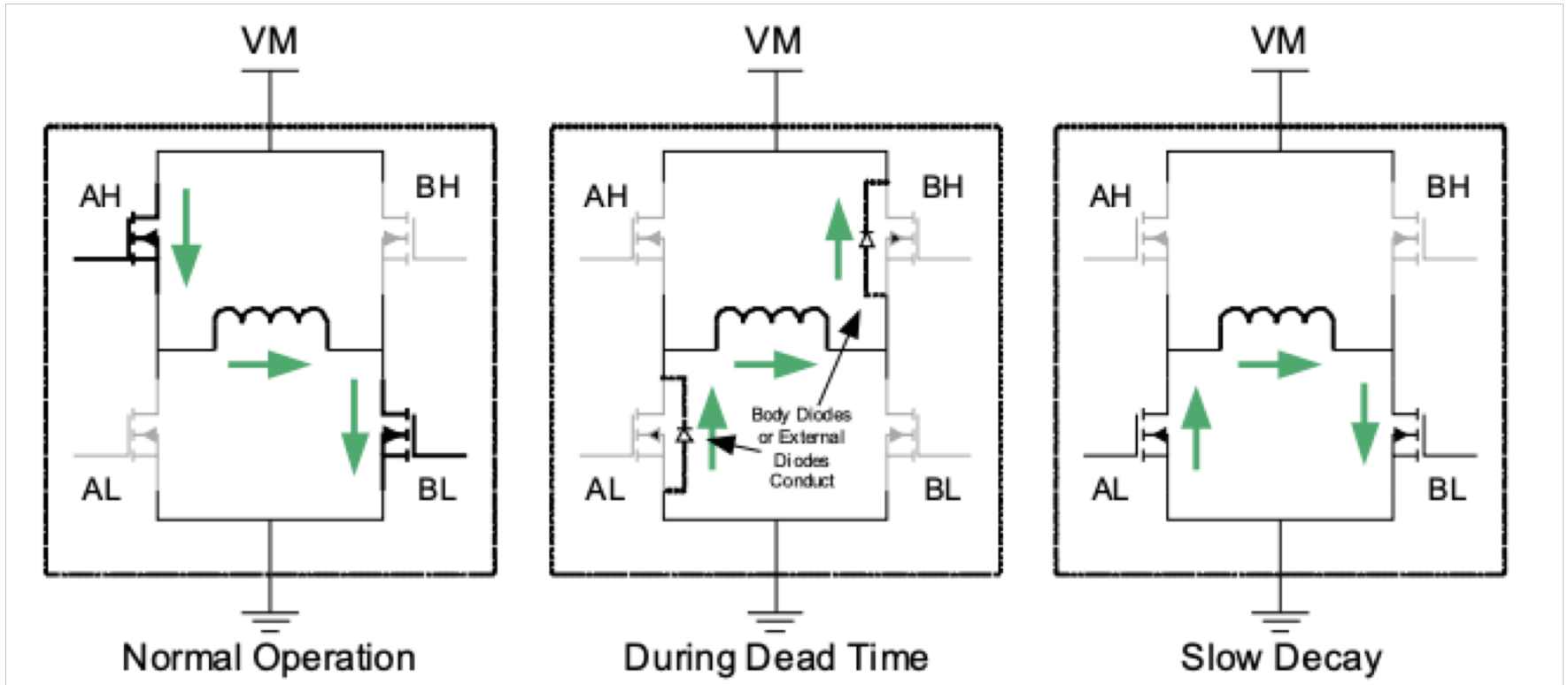

Inductance


Typical Brushed Motor in Cross-section

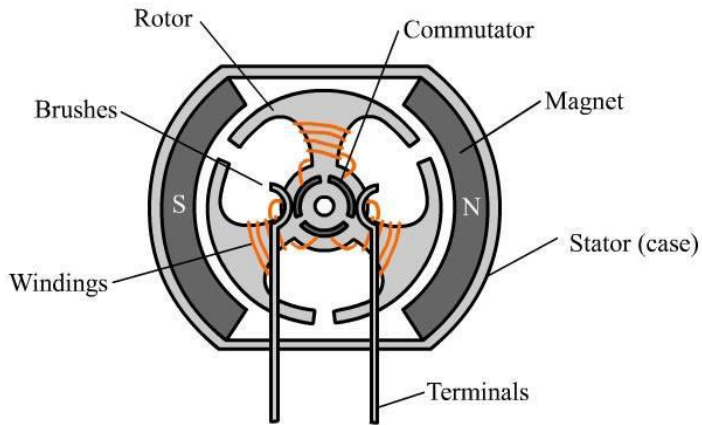

Calculate (just like inertia). E.g.

$$L = \frac{N^2 \mu A}{l}$$

$$\mu = \mu_r \mu_0$$

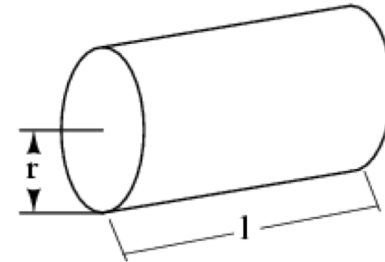

Where,

L = Inductance of coil in Henrys

N = Number of turns in wire coil (straight wire = 1)


μ = Permeability of core material (absolute, not relative)

μ_r = Relative permeability, dimensionless ($\mu_0=1$ for air)

$\mu_0 = 1.26 \times 10^{-6}$ T-m/At permeability of free space


A = Area of coil in square meters = πr^2

l = Average length of coil in meters

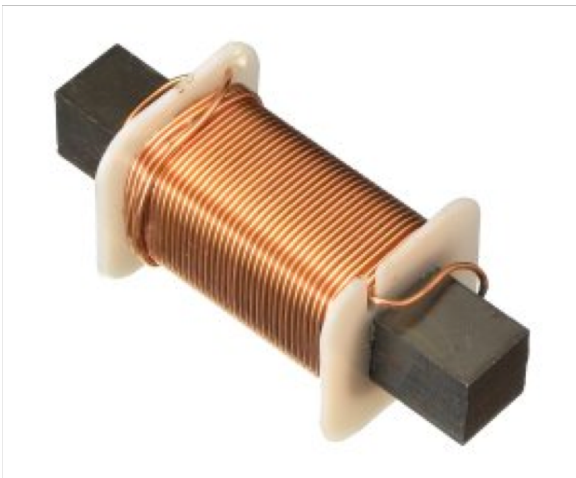


Finite element simulation for more complicated geometries

PWM Speed Control

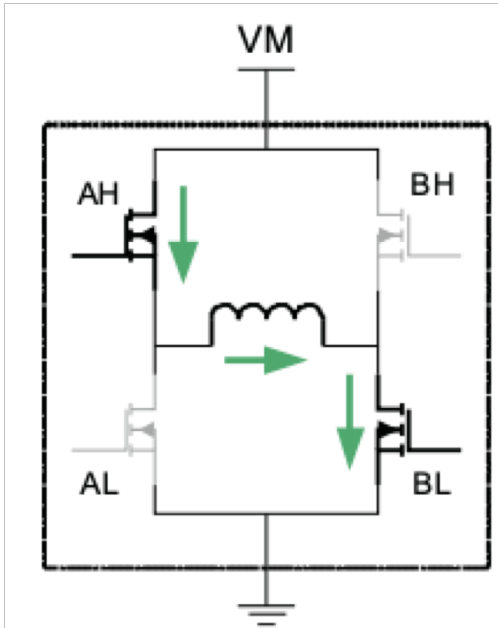

“ON”

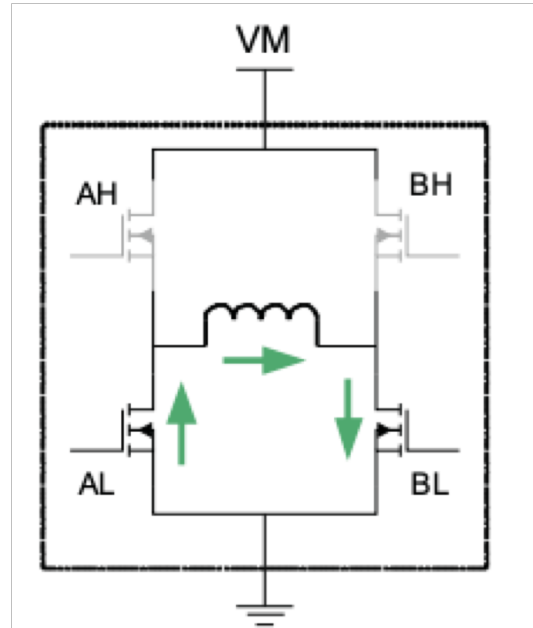

“OFF”

50% duty cycle



75% duty cycle



25% duty cycle



DRV8833 H-Bridge



DRV8833

SLVSAR1E – JANUARY 2011 – REVISED JULY 2015

DRV8833 Dual H-Bridge Motor Driver

1 Features

- Dual-H-Bridge Current-Control Motor Driver
 - Can Drive Two DC Motors or One Stepper Motor
 - Low MOSFET ON-Resistance: HS + LS 360 mΩ
- Output Current (at $V_M = 5\text{ V}$, 25°C)
 - 1.5-A RMS, 2-A Peak per H-Bridge in PWP and RTY Package Options
 - 500-mA RMS, 2-A Peak per H-Bridge in PW Package Option
- Outputs can be in Parallel for
 - 3-A RMS, 4-A Peak (PWP and RTY)
 - 1-A RMS, 4-A Peak (PW)
- Wide Power Supply Voltage Range: 2.7 to 10.8 V
- PWM Winding Current Regulation and Current Limiting
- Thermally Enhanced Surface-Mount Packages

3 Description

The DRV8833 device provides a dual bridge motor driver solution for toys, printers, and other mechatronic applications.


The device has two H-bridge drivers, and can drive two DC brush motors, a bipolar stepper motor, solenoids, or other inductive loads.

The output driver block of each H-bridge consists of N-channel power MOSFETs configured as an H-bridge to drive the motor windings. Each H-bridge includes circuitry to regulate or limit the winding current.

Internal shutdown functions with a fault output pin are provided for overcurrent protection, short-circuit protection, undervoltage lockout, and overtemperature. A low-power sleep mode is also provided.

The DRV8833 is packaged in a 16-pin WQFN package with PowerPAD™ (Eco-friendly: RoHS & no Sb/Br).

Block Diagram

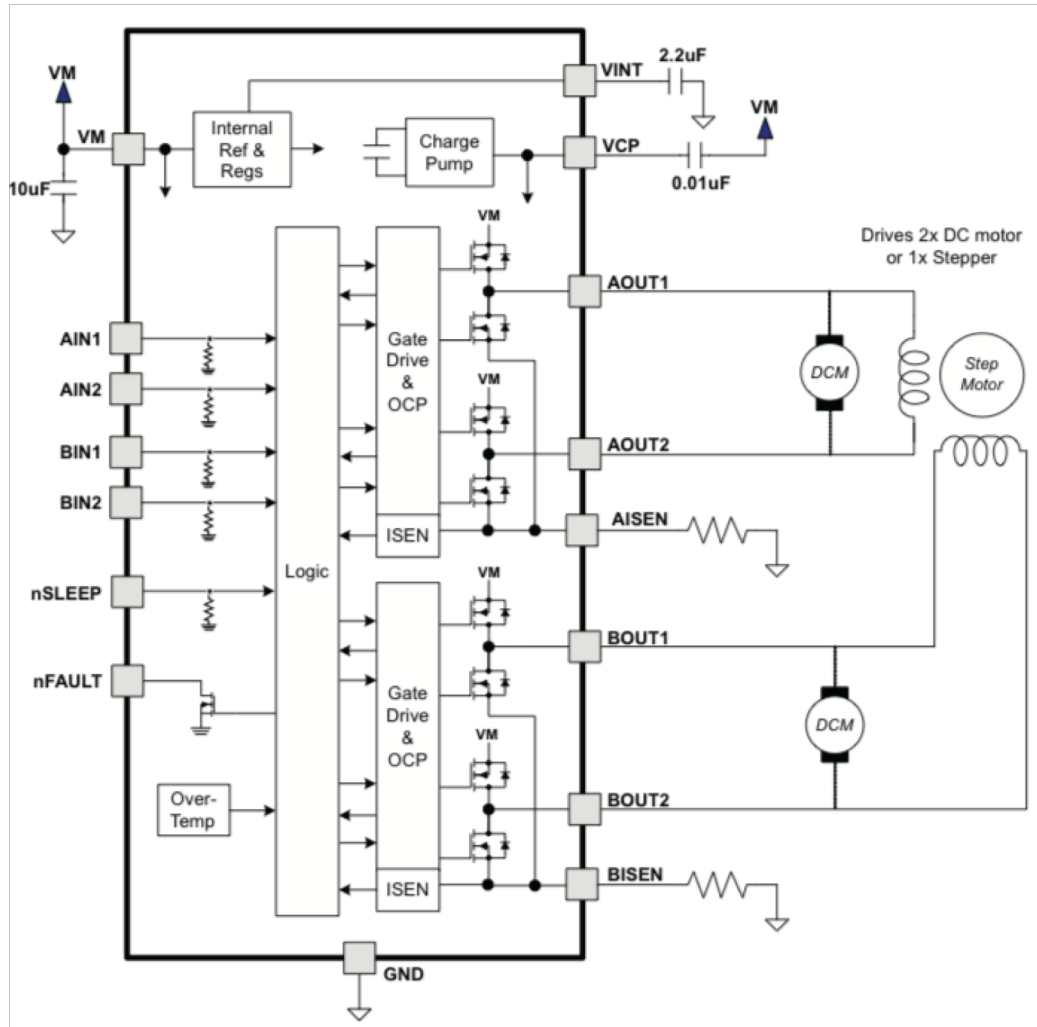

PWM Control

Table 2. PWM Control of Motor Speed

xIN1	xIN2	FUNCTION
PWM	0	Forward PWM, fast decay
1	PWM	Forward PWM, slow decay
0	PWM	Reverse PWM, fast decay
PWM	1	Reverse PWM, slow decay

Breakout Board Wiring

