

# Hambley Problems Problem Set 3

**P1.67.** The circuit shown in Figure P1.67 is the electrical model for an electronic megaphone, in which the  $8\text{-}\Omega$  resistance models a loudspeaker, the source  $V_x$  and the  $5\text{-k}\Omega$  resistance represent a microphone, and the remaining elements model an amplifier. Given that the power delivered to the  $8\text{-}\Omega$  resistance is  $8\text{ W}$ , determine the current circulating in the right-hand loop of the circuit. Also, determine the value of the microphone voltage  $V_x$ .

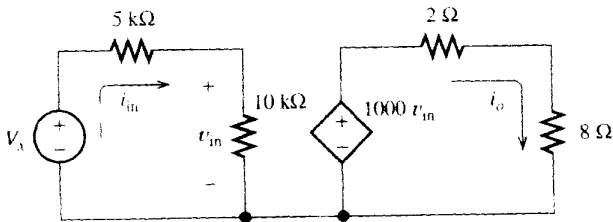


Figure P1.67

**\*P14.32.** Consider the amplifier shown in Figure P14.32. Find an expression for the output current  $i_o$ . What is the input impedance? What is the output impedance seen by  $R_L$ ?

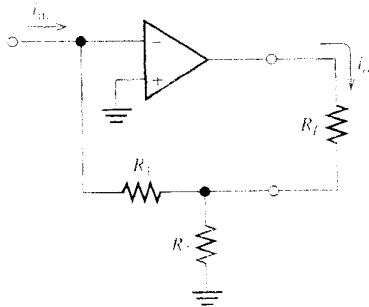


Figure P14.32

**P2.80.** An automotive battery has an open-circuit voltage of  $12.6\text{ V}$  and supplies  $100\text{ A}$  when a  $0.1\text{-}\Omega$  resistance is connected across the battery terminals. Draw the Thévenin and Norton equivalent circuits, including values for the circuit parameters. What current can this battery deliver to a short circuit? Considering that the energy stored in the battery remains constant under open-circuit conditions, which of these equivalent circuits is more realistic? Explain.

**P14.12.** Consider the inverting amplifier shown in Figure P14.12, in which one of the resistors has been replaced with a diode. Assume an ideal op amp,  $v_{in}$  positive, and a diode current given by Equation 10.4, which states that  $i_D = I_s e^{v_D/V_T}$ .

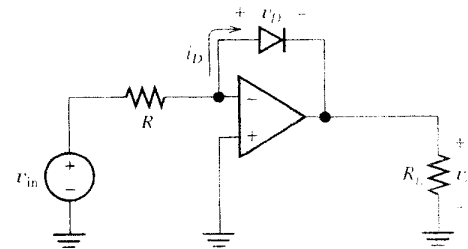


Figure P14.12

**P14.34.** The circuit shown in Figure P14.34 employs negative feedback. Use the summing-point constraint (for both op amps) to derive expressions for the voltage gains  $A_1 = v_{o1}/v_{in}$  and  $A_2 = v_{o2}/v_{o1}$ .

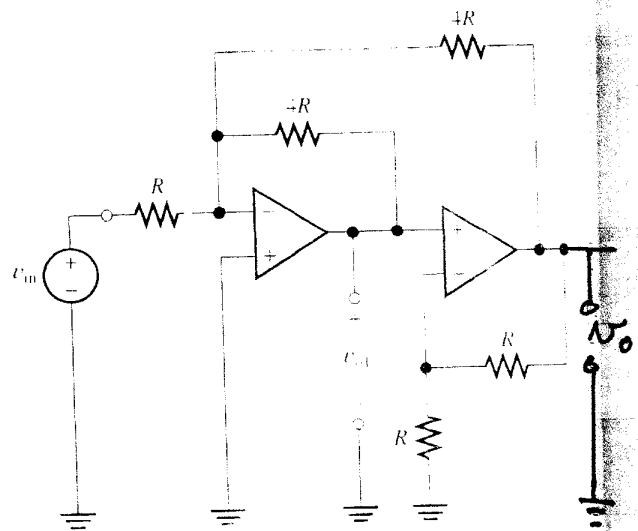


Figure P14.34