

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**

**EEEC100/42, Fall 2009**

**T. K. Gustafson**

NAME(PLEASE PRINT CLEARLY):

S.I.D. :

**Fall 2009**

Due : Oct 28 at lecture

Problem Set No. 4

Based upon Chapters 3-5 of Hambley, further use of LTSpice Basic MOSFET (12.1,12.2),  
Diode (10.4-10.7) ,and Transistor (13.1-13.4).

Problem Number one ) Given initial current find voltage!

- a) Hambley 3.11. In addition sketch the stored energy versus time.
- b) Hambley 4.45
- c) Hambley 3.71. Why do you get  $v(t) = 0$  for the answer?

Problem Number two ) Transient and Steady State Capacitors and inductors

- a) Hambley 4.27
- b) Hambley 4.11
- c) Hambley 4.49

Problem No 3) Transient and Steady State Sinusoidal Excitation of an R-L Circuit  
Hambley 4.48

Problem No 4) Transient and Steady State Sinusoidal Excitation of a series resonant circuit

- a) Hambley 4.64 Do this any way you wish.
- b) Verify the result of a) using LTSpice by plotting the amplitude (lg-lg) (and phase) of  $v_c(t)$  over a frequency range of 1 Hz to 1 kHz. What is the slope of the line beyond 100 Hz (dB/decade). (Note LTSpice does this automatically when you ask it to plot  $v_c(t)$ ).

Problem No 5) Basic Amplifier Parameters

Problem 11.7 of Hambley

Problem No 6) Field Effect Transistor

- a) Problem 12.2 of Hambley
- b) Using LTSpice obtain the drain characteristics of the Infineon BSS145 n-channel FET (its listed). To do this place voltage sources between the gate and ground (source) and between

the drain and ground (source). Do a d. c. sweep of the 1st voltage source (drain-source ) between 0 and 5 volts. Use an increment of .01. Also ask for a sweep of the 2nd voltage source (drain-source) between 2 and 5 volts with an increment of .5 V. Then simulate-run and finally under "view" click Id(M1)

Problem No 7) Diode Circuit

Problem 10.71 of Hambley. If you wish to simulate it, a frequency of 1000 rad / sec , C values of .001 F and R= 1k will show the results. A transient analysis out to 10 ms. is sufficient