

UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering
and Computer Sciences

EEEC100/42, Fall 2009

T. K. Gustafson

NAME(PLEASE PRINT CLEARLY):

S.I.D. :

Fall 2009

Due : Nov 13 at lecture

Problem Set No. 5

Based upon Chapters 3-5 of Hambley, Basic MOSFET (12.1,12.2), Diode (10.4-10.7) ,and Transistor (13.1-13.4) and digital concepts. Three problems are basically review

Problem Number one) Transient and Steady State RLC Circuit (Review)

a) Hambley 4.22 .


b) Also, what are the initial currents just after the switch is closed.

c) Also solve for the steady-state current i_1 if the source voltage is $100\cos(\omega t)$ for $\omega = 100$ rad/sec.

d) Use LTSpice to plot i_3 as a function of ω for $1 < \omega < 10000$

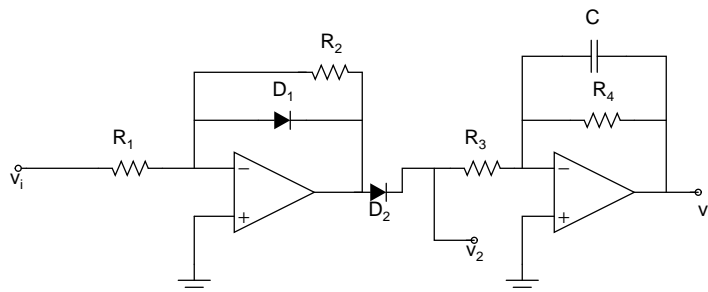Problem Number two) Voltmeter (Op Amps and Ideal Diodes) (Review)

The following circuit is a basic a.c. voltmeter.



Treat the diodes as ideal.

If the input is a sinusoid having a peak amplitude V_p , sketch the voltage waveform v_2 (Hint it is a rectified sine or cosine). Calculate the average value of v_2 in terms of R_1 , R_2 and V_p . Obtain an expression for the dc output voltage v_3 in terms of V_p and the resistors R_1 to R_4 . Assume $R_4 C$ is much greater than the period of the sinusoid so that only the average value of v_2 is not grounded by the capacitor.

If you wish to simulate this circuit, you can use $1k$ resistors, the generic diode, and LT1001A Op Amps with 12 volt plus and minus bias voltages. A $50 \mu\text{F}$ capacitor is sufficient. Increasing it shows the effect even more. Do a transient analysis for a sinusoid input at 60 Hz for 24 periods. Carry out the analysis from 0 to 400 ms. This should verify the analytical result.

Problem No 3) Load Line Analysis and bipolar characteristics

- a) Hambley 12.20 . I believe you only have to concern yourself with the saturation region of the FET.
- b) Hambley 13.29
- c) Hambley 13.19

Problem No 4) Binary -decimal representation, Boolean concepts

- a) Hambley 7.8 (Do this on a calculator if you wish!)
- b) Hambley 7.27
- c) Hambley 7.46 (Should also look at 7.47)

Problem No 5) Karnaugh Maps, SOP and POS

Hambley Problem 7.54

Problem No 6) Ideal Op-Amp Review

Hambley Problem 14.25

Problem No 7) Multi frequency component signal

Hambley Problem 6.24