

Solution Hambley 11.7 Problem 5 Problem Set 4 ①



$$R_i = 1 \text{ M}\Omega$$

$$R_o = 1 \text{ k}\Omega$$

$$A_{voc} = -10^4$$

$$R_L = 1 \text{ k}\Omega$$

Equivalent Circuit

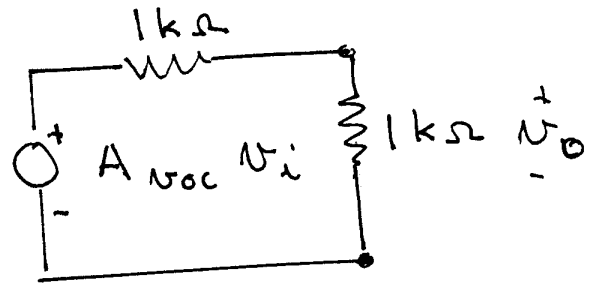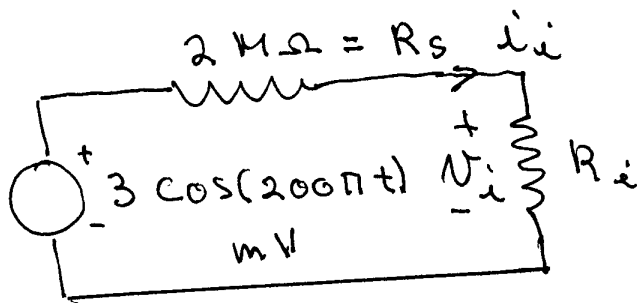

$$V_o = -A_{voc} V_i \times \frac{R_L}{R_L + R_o}$$

$$V_i = \frac{R_i}{R_i + R_s} \times 3 \cos(200\pi t) = \cos(200\pi t)$$

Source voltage gain = $\frac{V_o}{3 \cos(200\pi t)} = -A_{voc} \times$

$$\left(\frac{R_L}{R_L + R_o} \right) \left(\frac{R_i}{R_i + R_s} \right) = A_{vs}$$

$$\begin{aligned} A_{vs} &= -10^4 \times \frac{1}{1+1} \times \frac{1}{1+2} = -\frac{10^4}{6} = -1.66 \dots \times 10^3 \\ &= -20(\log_{10} 1.66 + 3) \\ &= -20(3.22) \\ &= -64.4 \text{ dB} \end{aligned}$$

Thus $V_o(t) = -(1.66 \times 10^3) \times 3 \cos(200\pi t) \text{ mV}$
 $= -4 \cos(200\pi t) \text{ V}$

Power Gain

$$\text{Power to load (time Avg)} = \frac{1}{2} \frac{V_L^2}{1k\Omega} \quad V_L = 3 \frac{R_L}{R_L + R_o} \times \frac{R_i}{R_i + R_s}$$

$$\text{Power from source (time Avg)} = \frac{3^2}{2} \times \left(\frac{1}{3M\Omega} \right)$$

∴ Power gain for amp is generally the power to load / power into amplifier input (Not Power from Source)

$$= \left(\frac{1}{2} \frac{V_L^2}{1k\Omega} \right) \div \frac{V_i I_i}{2} \leftarrow \text{time Avg}$$

$$= \frac{1}{2} \frac{V_L^2}{R_L} \div \frac{1}{\frac{R_i}{R_i + R_s} \times 3 \times \frac{3}{R_i + R_s} \times \frac{1}{2}} \leftarrow \text{RMS}$$

$$= \frac{A_{vdc}^2 R_L}{R_L (R_L + R_o)^2} \times \frac{R_i^2}{(R_i + R_s)^2} \times \frac{1}{\frac{R_i}{(R_i + R_s)^2} \times \frac{1}{2}}$$

$$G = \frac{A_{vdc}^2 R_L R_i}{(R_L + R_o)^2} = \frac{10^8 \times 1k\Omega \times 1000k\Omega}{(2k\Omega)^2} \quad \text{Note}$$

$$= \frac{10^{11}}{4} = 2.5 \times 10^{10} \rightarrow 10(\ln \frac{1}{4} + 9) \text{ dB}$$

$$= 10(-.60 + 9) = (-6 + 90)$$

Check

$$\check{G} = A_{vs}^2 \frac{(R_i + R_s)^2}{R_i R_L} = \frac{10^8}{36} \times \frac{10^{12}}{10^9} = \frac{1}{4} \times 10^{11} = \underline{\underline{84 \text{ dB}}}$$