
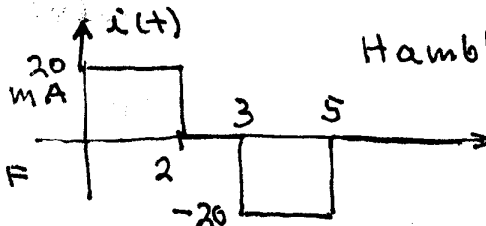


Solutions

Problem 1


a)

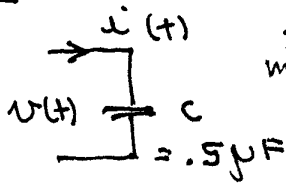

Hambley 3.11

$$i = C \frac{dv}{dt}$$

$$v = \int \frac{i}{C} dt$$

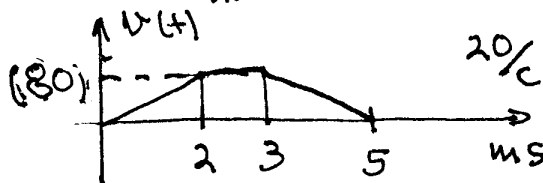


$$\frac{20}{C} = \frac{20 \text{ mA}}{0.5 \times 10^{-6} \text{ F}} = 40 \times 10^3 \text{ V/s}$$

At 2 msec

$$V = 80 \text{ V}$$

Energy

$$1.6 \text{ mJ}$$

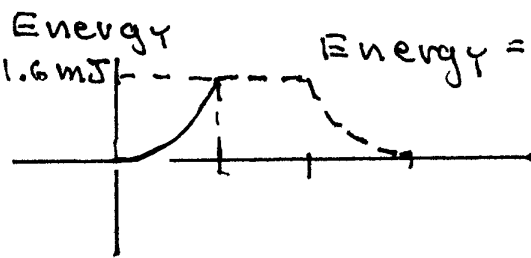


$$\text{Energy} = \frac{1}{2} C v^2$$

$$\text{Peak} = \frac{1}{2} \times \frac{1}{2} \times 10^{-6} (80)^2$$


$$= \frac{1}{4} \times 10^{-6} \times 64 \times 10^2$$

$$= 16 \times 10^{-4} \text{ J}$$

b)

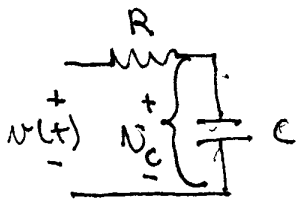

Hambley 4.45

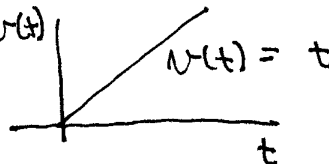

$$v_c(t) = \frac{\frac{1}{pC}}{\frac{1}{pC} + R} v(t) = \frac{1}{1 + pCR} t$$

$$= \left(\frac{1}{pCR}\right) \left(\frac{1}{1 + \frac{1}{pCR}}\right) t$$

$$= \frac{1}{pCR} \left(1 - \frac{1}{pCR} + \left(\frac{1}{pCR}\right)^2 - \left(\frac{1}{pCR}\right)^3 + \dots\right) t$$

$$= \frac{1}{CR} \left(\frac{t^2}{2} - \frac{1}{CR} \frac{t^3}{3!} + \frac{1}{(CR)^2} \frac{t^4}{4!} + \dots\right)$$

$$= RC \left(-1 + \frac{t}{RC} + e^{-t/RC}\right)$$

Problem No. 1c

Hambley 3.71

$$LC = 500 \times 10^{-6} \times 2 \times 10^{-3} = 10^{-6} \therefore \frac{1}{\sqrt{LC}} = \omega_0 = 1000$$

$$V_c(t) = 10 \sin(1000t)$$

$$i = C \frac{dV_c}{dt} = 500 \times 10^{-6} \times 10 \times 1000 \cos(1000t) = 5 \cos(\omega_0 t)$$


$$V_L(t) = L \frac{di}{dt} = -2 \times 10^{-3} \times 5 \omega_0 \sin(\omega_0 t) = -10 \sin \omega_0 t$$

$$V(t) = 0$$

Problem No. 2

a) Hambley 4.27

Inductor is short
Capacitor is open

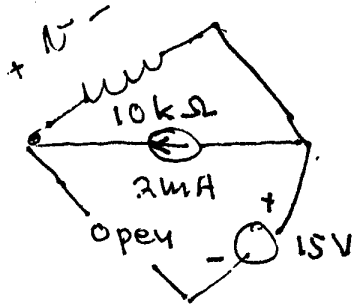


$$V = 2 \text{ mA} \times 10 \text{ k}\Omega = 20 \text{ V}$$

$$i_R = 2 \text{ mA}$$

$$V_c = 20 + 15 = \underline{35 \text{ V}}$$

b) Hambley 4.11

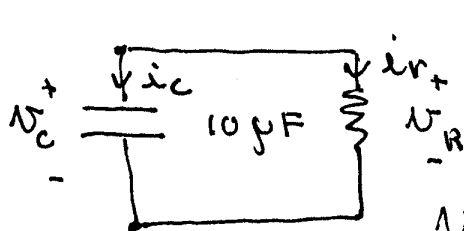

$$i_c + i_R = 0$$

$$\left(\frac{1}{pC} + R\right)V = 0$$

$$V_R = V_c = V$$

$$\frac{1}{C} V(t) + pRV = 0$$

Note: if you use integrals note that $\frac{1}{p}$ can involve a constant

$$\frac{dV}{dt} + R(p)V = 0$$

$$\int \frac{dV}{dt} dt + R \int \frac{dV}{dt} dt = 0$$

$$- \int \frac{dV}{dt} dt + R(V(t) - V(0)) = 0$$

Solution to Differential Equation $V(t) = A e^{st}$ $V(0) = A$

$$\frac{1}{C} A e^{st} + s R A e^{st} = 0$$


$$\therefore s = -RC \quad A = 50 \text{ V}$$

$$t = 30 \text{ sec} \quad V(t) = 50 e^{-30/RC} = 25 \text{ V}$$

$$\therefore -30/RC = \ln \frac{25}{50} = -\ln 2 = .69$$

$$R = \frac{30}{.69C} = \frac{50}{3 \cdot .69} \text{ M}\Omega = 4.34 \text{ M}\Omega$$

Problem 4, 49

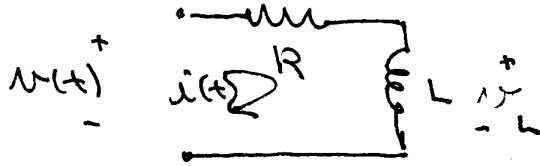

$$v(t) = (R + Lp) i(t)$$

$$i(t) = \left(\frac{1}{R + Lp} \right) v(t)$$

$$= \frac{1}{Lp} \left(\frac{1}{1 + \frac{R}{Lp}} \right) i(t)$$

$$= \frac{1}{Lp} \left(1 - \frac{R}{L} \frac{1}{p} + \left(\frac{R}{L} \frac{1}{p} \right)^2 + \dots \right) v(t)$$

$$= \frac{1}{R} \left(\frac{R}{Lp} - \left(\frac{R}{Lp} \right)^2 + \left(\frac{R}{Lp} \right)^3 + \dots \right) v(t)$$

$$= \frac{1}{R} \left(\frac{1}{2} \frac{R}{L} t^2 - \left(\frac{R}{L} \right)^2 \frac{t^3}{3!} + \left(\frac{R}{L} \right)^3 \frac{t^4}{4!} + \dots \right)$$

$$= \frac{1}{R^2} \left(\frac{1}{2} \left(\frac{Rt}{L} \right)^2 - \frac{1}{3!} \left(\frac{Rt}{L} \right)^3 + \dots \right)$$

$$= -\frac{1}{R^2} + \frac{1}{R} t + \frac{1}{R^2} \left(1 - \frac{Rt}{L} + \frac{1}{2} \left(\frac{Rt}{L} \right)^2 - \dots \right)$$

$$= -\frac{1}{R^2} + \frac{t}{R} + \frac{1}{R^2} e^{-Rt/L}$$

transient solution

Note

$$v_L = L \frac{di}{dt}$$

$\therefore i$ can't change instantaneously unless $v_L \rightarrow \infty$

$$\left. \frac{di}{dt} \right|_{t=0} = \frac{1}{R} - \frac{R}{L} \frac{1}{R^2} = 0$$

No. 3

$$t = 0 \quad 10 \sin(300t)$$

$$\overline{v(t)} = \overline{Ri} + L \frac{di}{dt}$$

Multiply both sides by $e^{R/L t}$

$$(10 \sin(300t) e^{R/L t}) = L \left(\frac{d}{dt} [e^{R/L t} i(t)] \right)$$

$$\textcircled{1} \quad \int_{0^+}^t \frac{10}{L} \sin(300t) e^{R/L t} dt = e^{R/L t} i(t) - i(0^+)$$

We can do this this way

$$2 \operatorname{Re} \int_{0^+}^t \frac{10}{L} \frac{e^{300jt} e^{R/L t}}{2j} dt$$

$$= \operatorname{Re} \frac{10}{Lj} \left[\frac{1}{300j + R/L} (e^{300jt + R/L t} - 1) \right]$$

$$= \frac{10}{L} \operatorname{Re} \left[\frac{1}{-300 + R/Lj} e^{300jt + R/L t} - \frac{1}{-300 + R/Lj} \right]$$

$$= \frac{10}{L} \operatorname{Re} \left[\frac{-300 - R/Lj}{(300)^2 + (R/L)^2} e^{300jt + R/L t} + \frac{300}{(300)^2 + (R/L)^2} \right]$$

$$= \frac{10}{L} \operatorname{Re} \left[\frac{-1}{\sqrt{(300)^2 + (R/L)^2}} e^{300jt + R/L t} + j \tan^{-1} \left(\frac{R/L}{300} \right) \right] + \frac{3000}{(300)^2 + (R/L)^2}$$

$$= -\frac{10}{L} \frac{\cos(300t + \tan^{-1}(1))}{300\sqrt{2}} e^{R/L t} + \frac{10}{300(2)}$$


$i(0^+) = 0$ so (1) results in

$$i(t) = -\frac{10}{300\sqrt{2}} \cos(300t + \pi/4) + \frac{10}{300 \times 2} e^{-R/L t}$$

Steady-State
Response

Natural Response
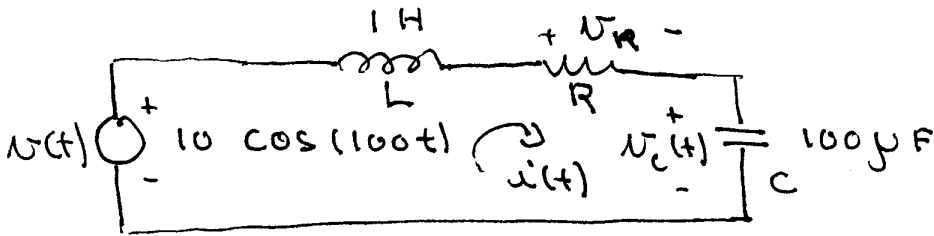
$$\text{check } i(t=0) = -\frac{10}{300\sqrt{2}} \underbrace{\cos \frac{\pi}{4}}_{= \frac{1}{\sqrt{2}}} + \frac{10}{600} = 0$$



Steady state

$$i(t) = \frac{1}{R + j\omega L + \frac{1}{j\omega C}} v(t)$$

$$\begin{aligned} \therefore i(t) &= \operatorname{Re} \left[\frac{1}{R + j\omega L + \frac{1}{j\omega C}} 10 e^{j100t} \right] \\ &= \operatorname{Re} \left[\frac{1}{R + j(\omega L - \frac{1}{\omega C})} 10 e^{j100t} \right] \\ &= \operatorname{Re} \left[\frac{10}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} e^{-j \tan^{-1} \left[\frac{(\omega L - \frac{1}{\omega C})}{R} \right] + j100t} \right] \\ &= \frac{10}{(R^2 + (\omega L - \frac{1}{\omega C})^2)^{\frac{1}{2}}} \cos \left(100t - \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right) \right) \end{aligned}$$

$\omega = 100 \text{ rad/sec}$

Transient Solution $i(t) \neq 0$ when $v(t) = 0$ for

$$R + pL + \frac{1}{pC} = 0$$

$$R + p^2 LC + 1 = 0$$

$$p^2 + p \frac{R}{L} + \frac{1}{LC} = 0$$

$$p = -\frac{1}{2} \frac{R}{L} \pm j \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$\therefore i_t(t) = e^{-\frac{R}{2L}t} [A e^{j\omega_1 t} + B e^{-j\omega_1 t}]$$

$$i_{\text{Total}} = i_t(t) + i(t) = 0 \text{ at } t=0$$

$$(1) \quad \therefore A + B = - \left[\frac{10}{(R^2 + (\omega L - \frac{1}{\omega C})^2)^{\frac{1}{2}}} \cos \left(\tan^{-1} \left[\frac{(\omega L - \frac{1}{\omega C})}{R} \right] \right) \right]$$

Also $i = C \frac{dv_C}{dt}$ $v_L = L \frac{di}{dt}$ v_C can't change instantaneously
 i can't change

so $i = 0$ at $t=0^+$ $v_C = 0$ at 0^+ $v_R = 0$ at 0^+

so by KVL $v_L = 0$ at 0^+ implying $\frac{di}{dt} = 0$ at 0^+

Thus

$$(2) \quad j\omega_1 [A - B] = \frac{1000}{(R^2 + (\omega L - \frac{1}{\omega C})^2)^{1/2}} \sin(\tan^{-1}(\frac{\omega L - \frac{1}{\omega C}}{R}))$$

parameters

$$\omega L - \frac{1}{\omega C} = 100 - \frac{1}{10^7 \times 10^{-6}} = 0$$

so the circuit is resonant. It just acts as a resistor for the S.F.S.F.


$$i(t) = \frac{10}{R} \cos(100t)$$


Transient

$$\begin{aligned} A + B &= -\frac{10}{R} \\ A - B &= 0 \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} \rightarrow B = A = -\frac{5}{R}$$


$$\begin{aligned} i_{\text{Total}}(t) &= \frac{10}{R} \cos(100t) - \frac{10}{R} e^{-R/L t} \\ &= 200 (\cos(100t) - e^{-R/L t}) \end{aligned}$$
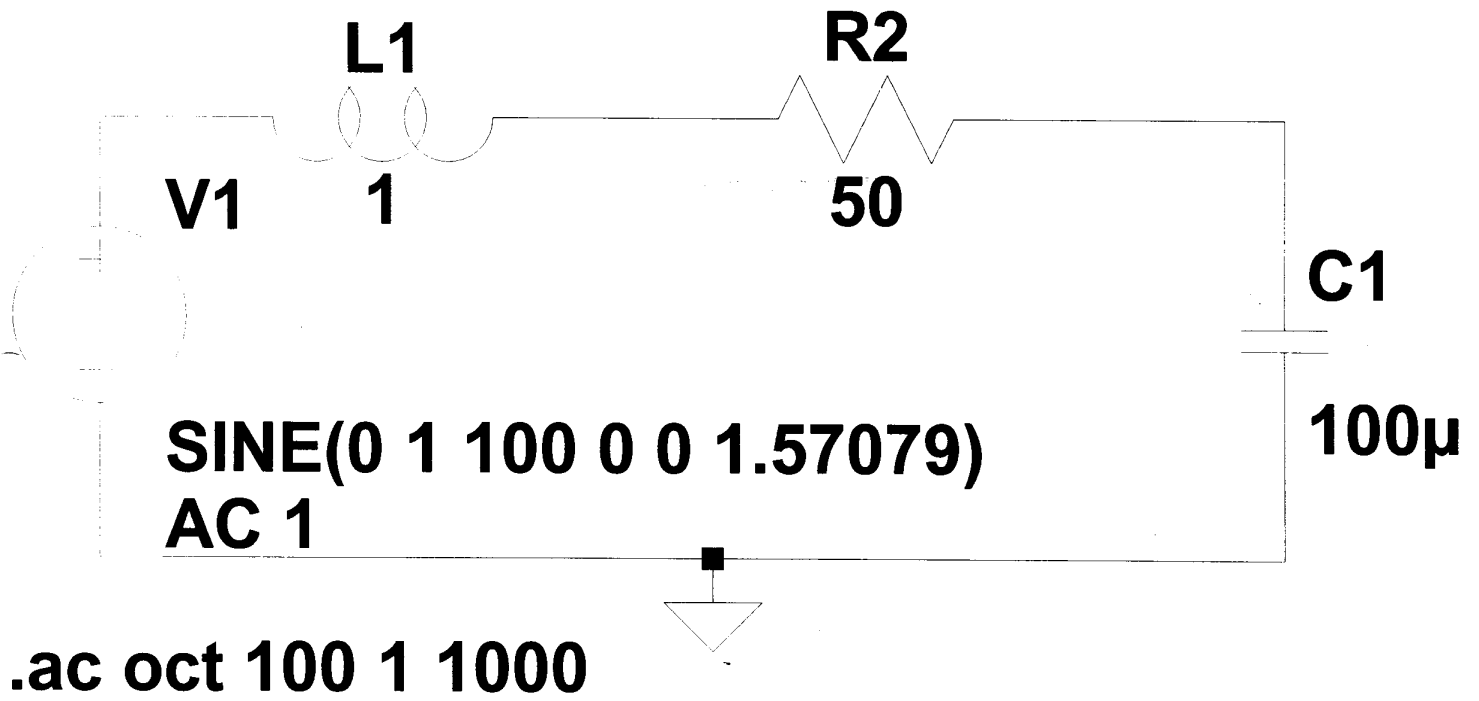
$$\frac{R}{L} = \frac{50}{1} = 50 \text{ sec}^{-1}; \quad L/R = 20 \text{ msec}$$




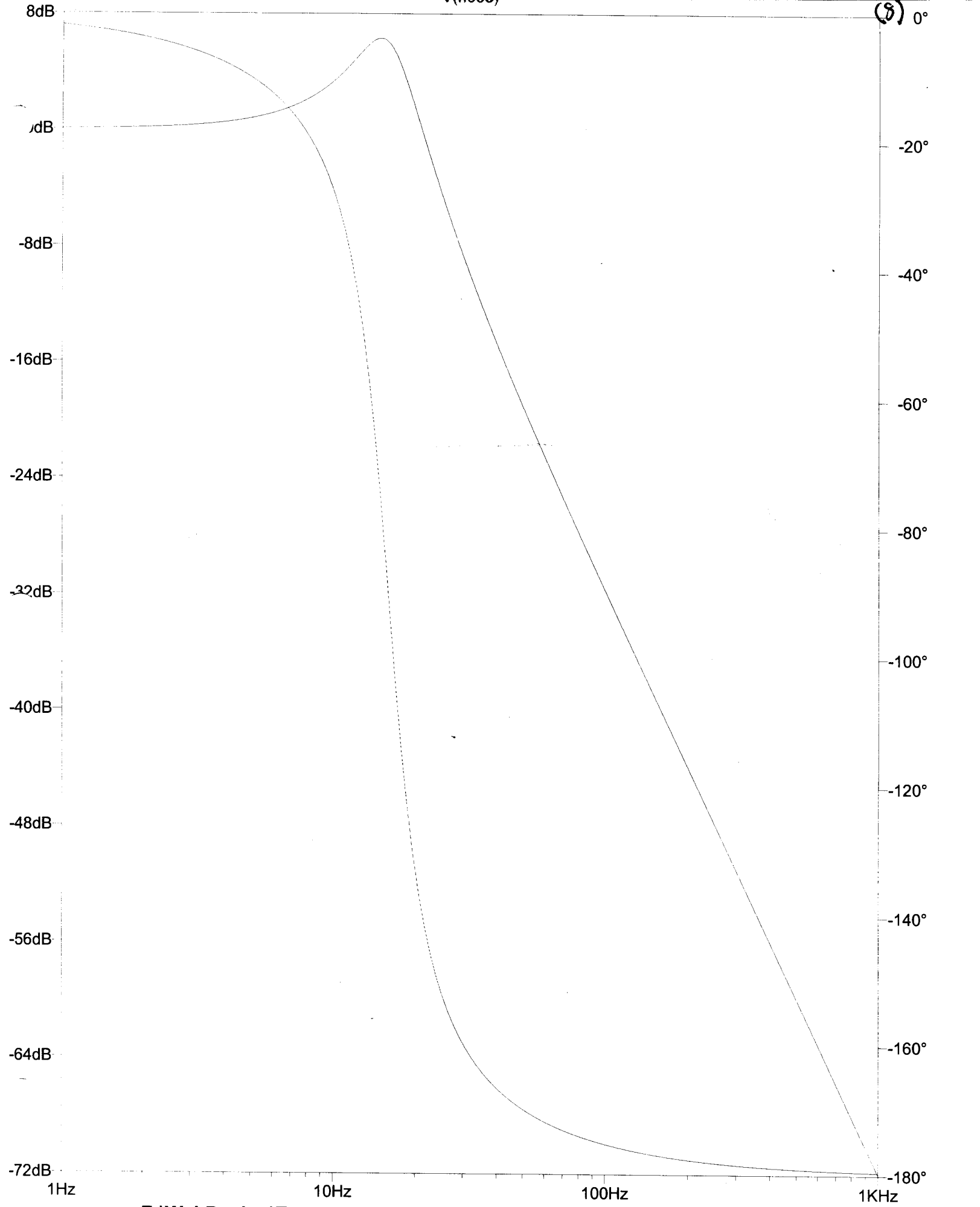


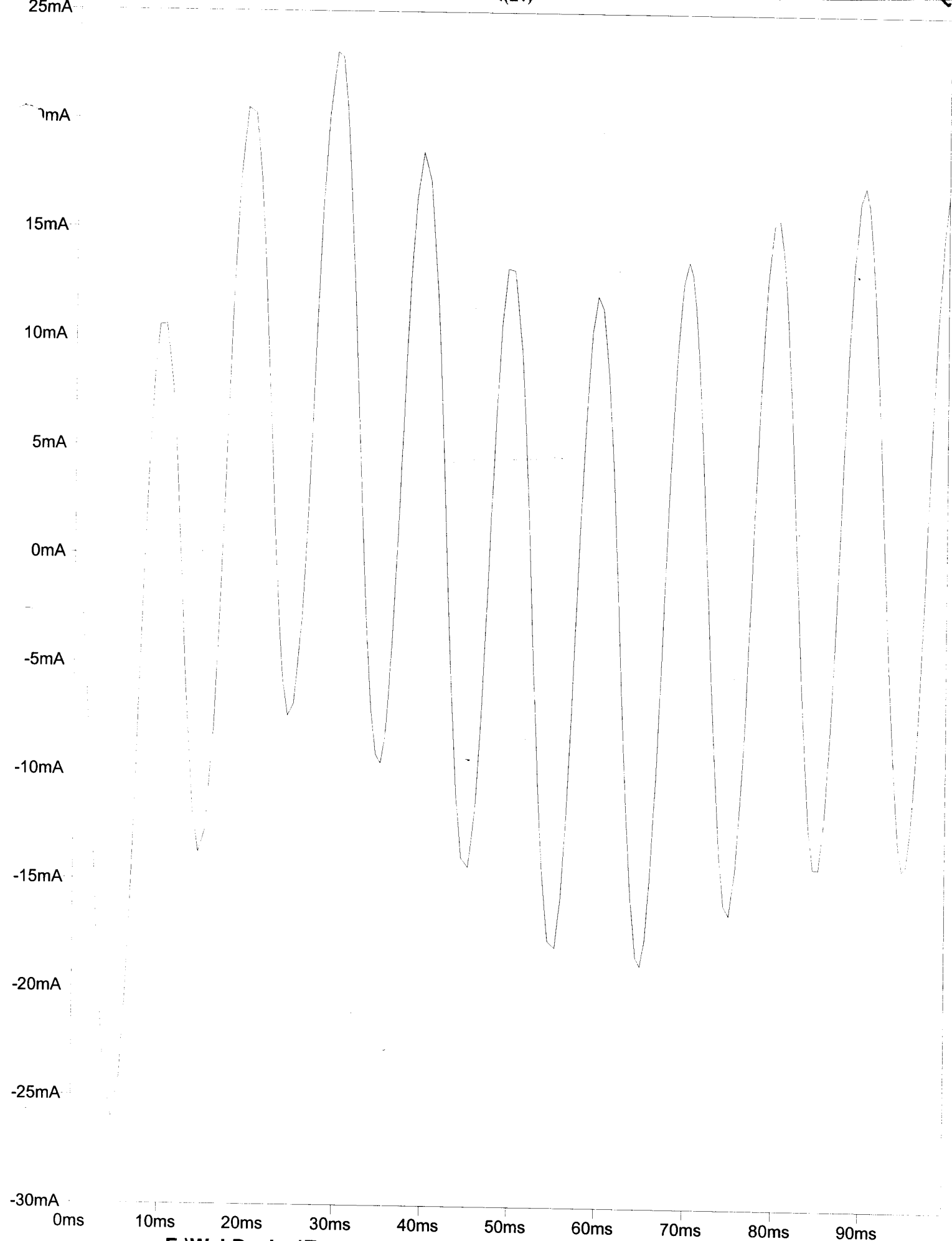--- E:\WebDesign\Templates\Documents\Simulations\Prob4_PS4_RLC.raw ---




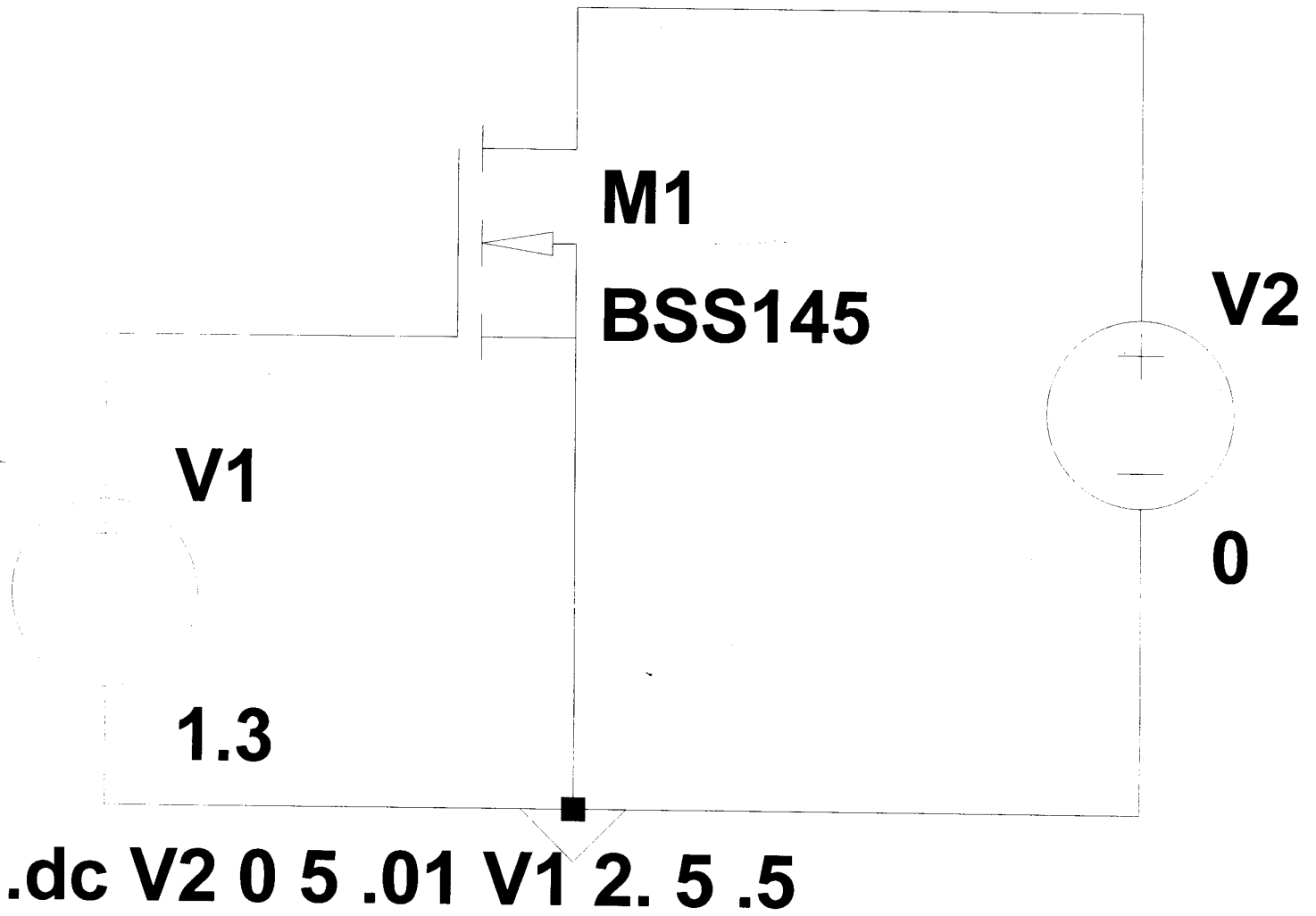--- E:\WebDesign\Templates\Documents\Simulations\Prob4_PS4_RLC.raw ---



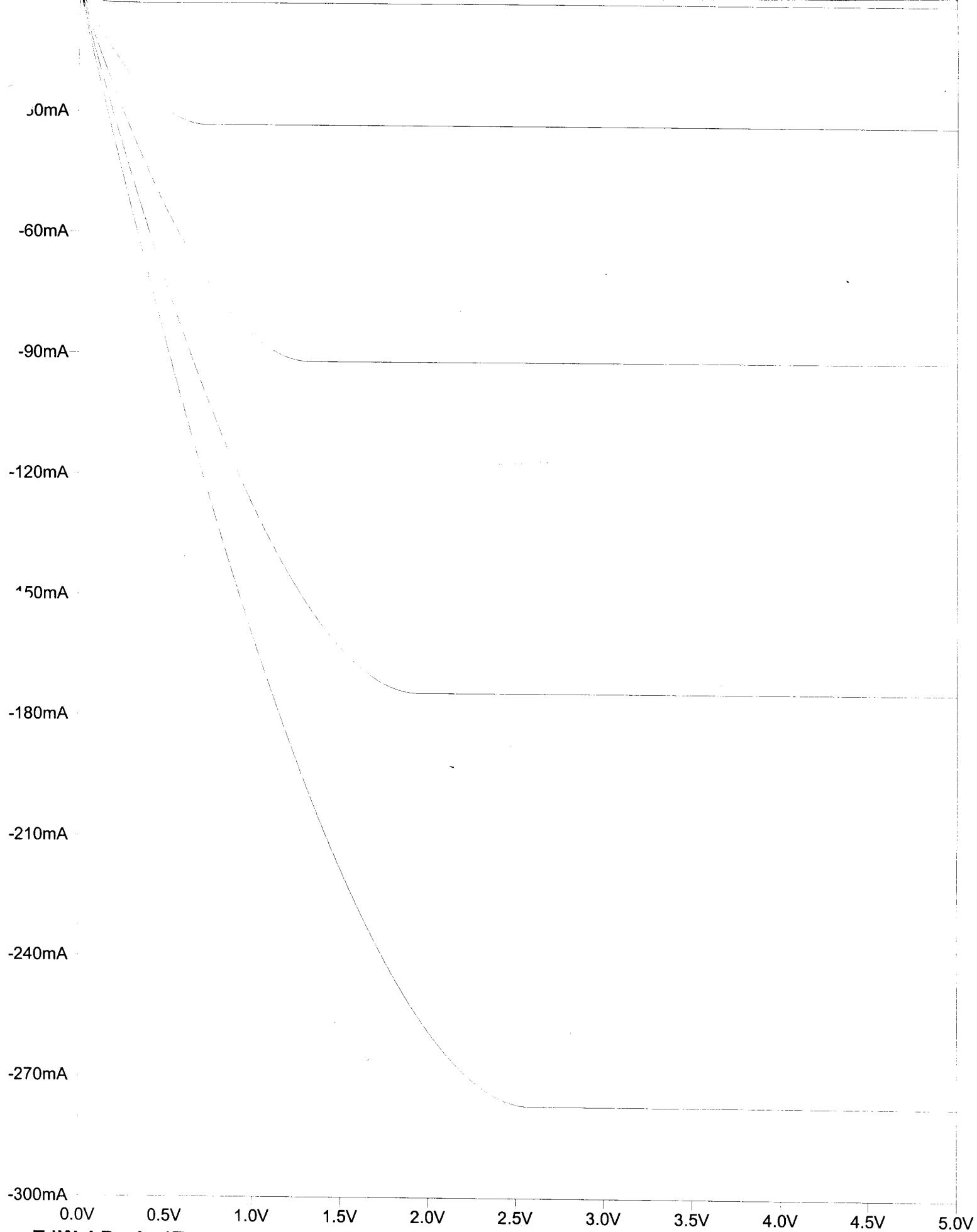

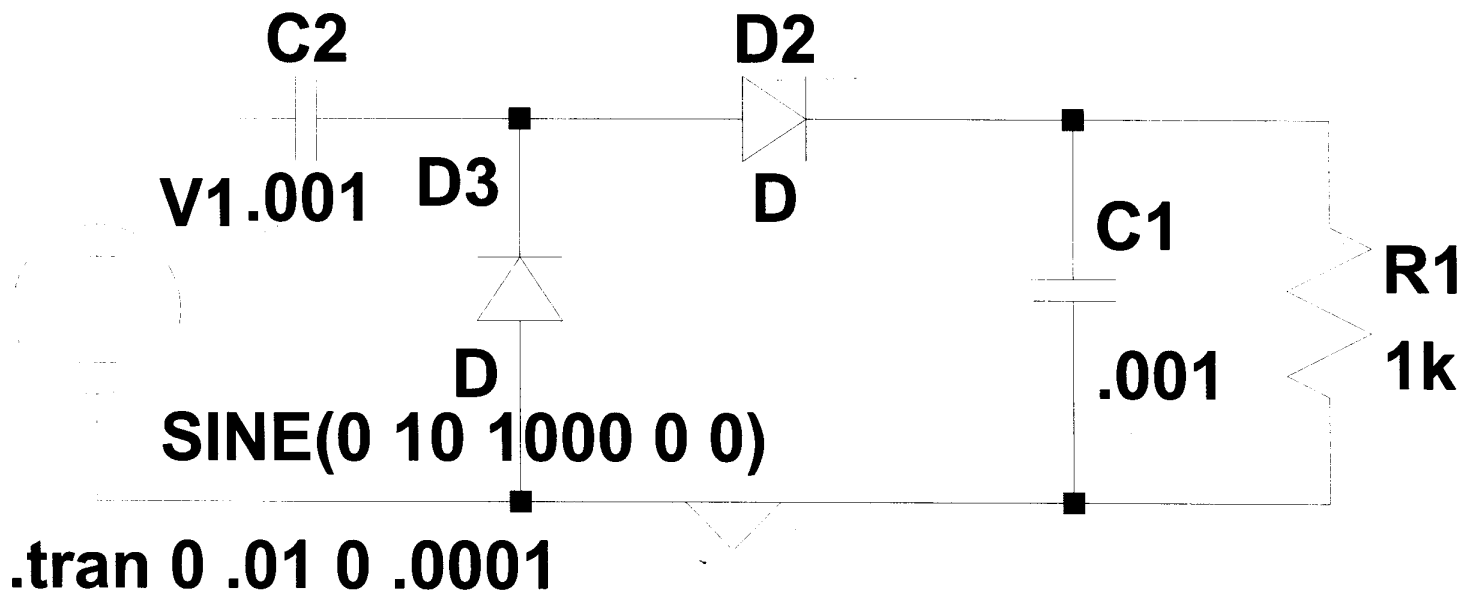
-- E:\WebDesign\Templates\Documents\Assignments\Problem_Sets\Problem_Set_4\Mosfet_Id_Vds.r



V(1002)

V(1003)

V(1004)

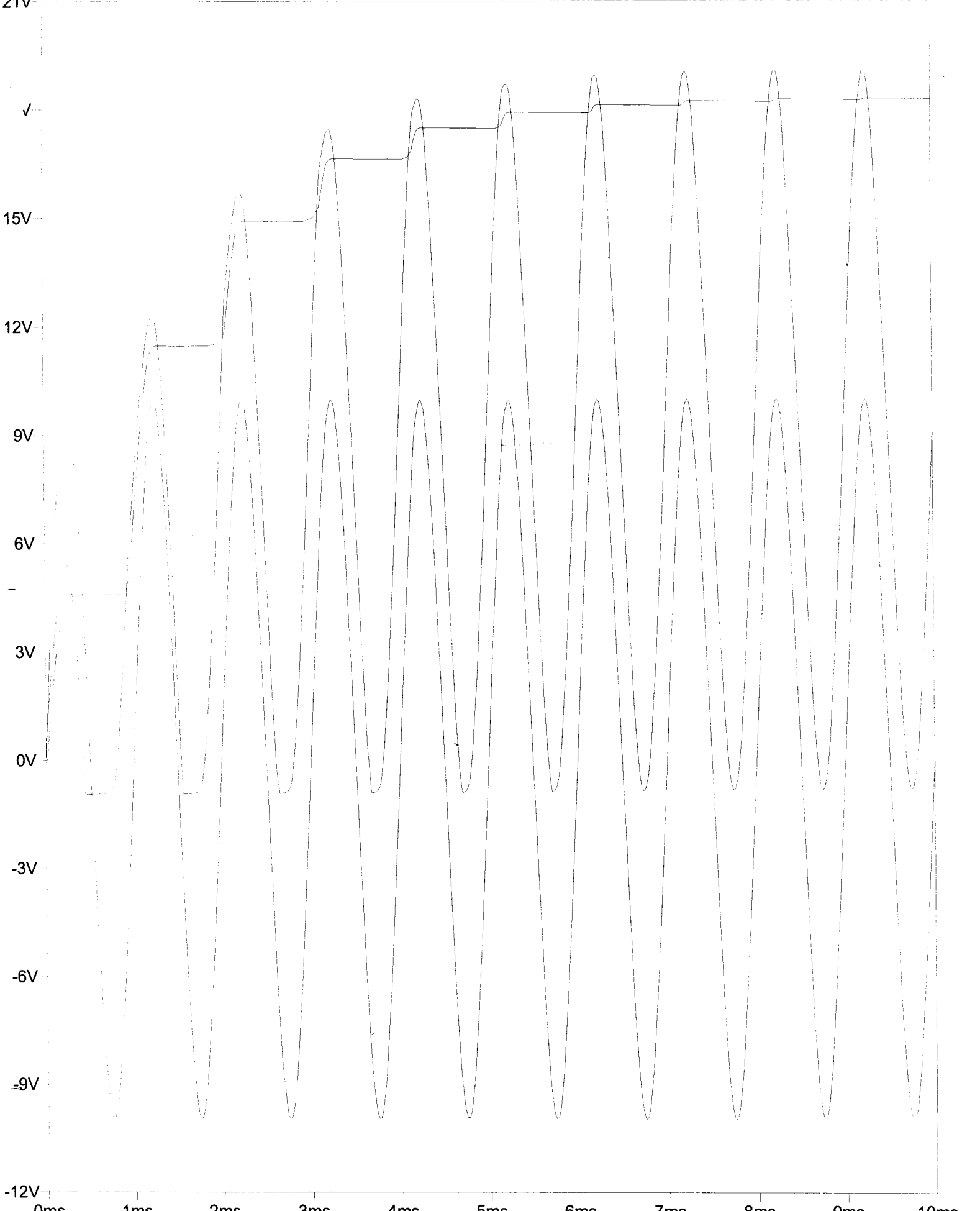

0ms 1ms 2ms 3ms 4ms 5ms 6ms 7ms 8ms 9ms 10ms

E:\WebDesign\Templates\Documents\Assignments\Problem_Sets\Problem_Set_4Voltage_Double.ra