

a) $i_2 = \frac{100}{10^3} = .1 \text{ Amp}$ (Inductor short, cap open)

$i_3 = 0$ (100 μF open); $i_4 = i_2 = .1 \text{ Amp}$

b) Initial current $i_1 = .2 \text{ Amps}$ (Inductor open, Capacitor short)

Thus $i_1 = 100/500 + 100/1000 = .3 \text{ Amps}$

c) $100 \cos 10^2 t$ $\omega = 10^2 \text{ rad/sec}$

For the steady-state

$$Z(\omega) = (100j + 1000) \parallel ((500 - j100) \parallel 1000)$$

$$= (100j + 1000) \parallel \left(\frac{(500 - j100)1000}{1500 - j100} \right)$$

$$= \frac{(100j + 1000)(500 - j100)1000}{100j + 1000 + (500 - j100)(1000)}$$

$$= \frac{100(j + 10)(5 - j)10}{(15 - j)}$$

$$= \frac{100(1 + 50j - 5j)10}{(15j + 1 + 150 - 10j + 50 - 10j)}$$

$$= \frac{100(1 + 50j - 5j)10}{-5j + 201}$$

$$= \frac{100(51 - 5j)(201 + 5j)10}{(201)^2 + 25}$$


$$= \frac{1000(51 \times 201 + 25 - j(5)(201 - 51))}{(201)^2 + 25}$$

$$= \frac{1000(10276 - j750)}{40426}$$

$$= 1000(.2542 - j.0186)$$

$$= 255 e^{-j.073}$$

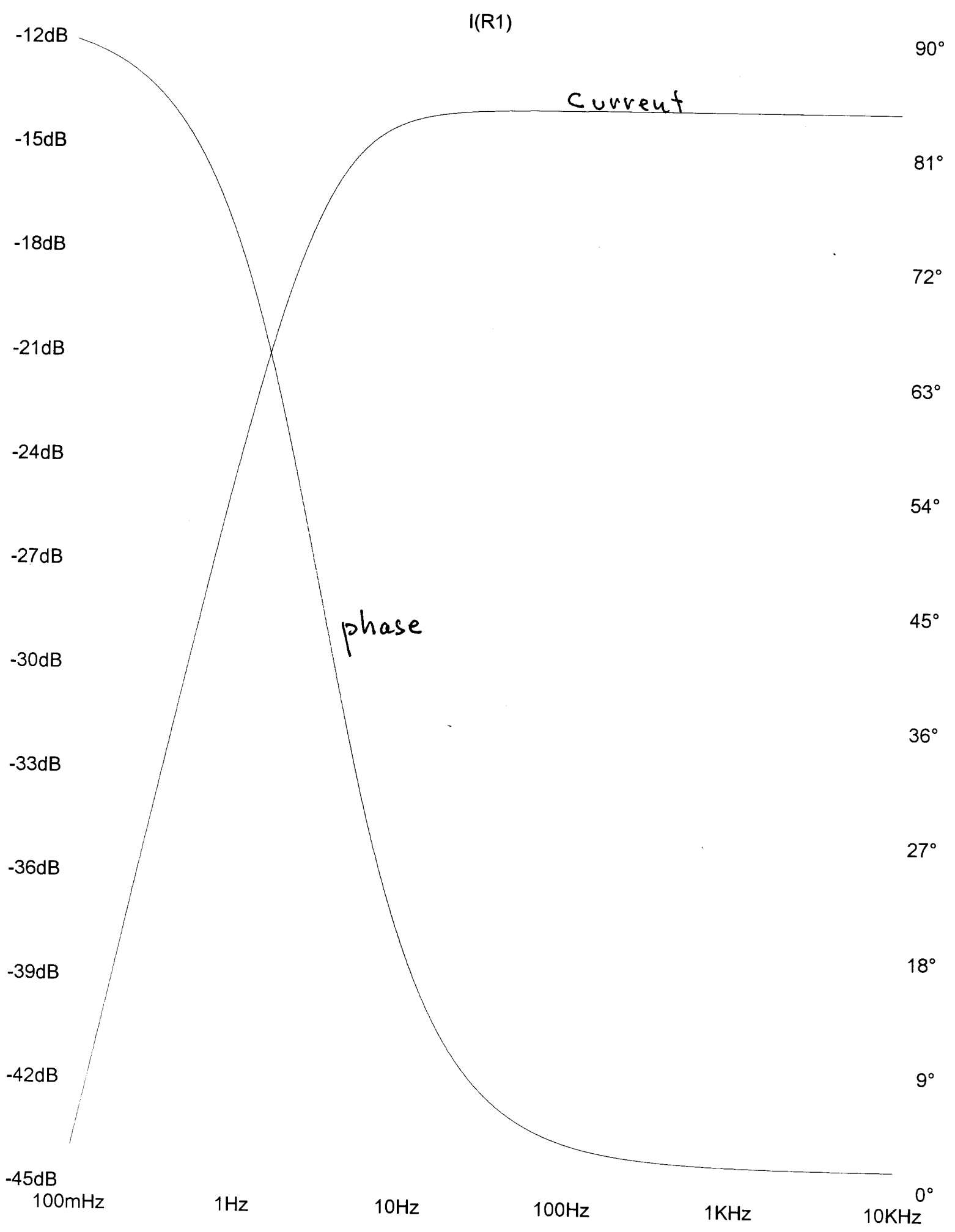
Thus $i_1(t) = \frac{100}{255} \cos(100t + .073)$ (Almost Resonant)



Problem No 2: (Reference Sedra/Smith page 1020)

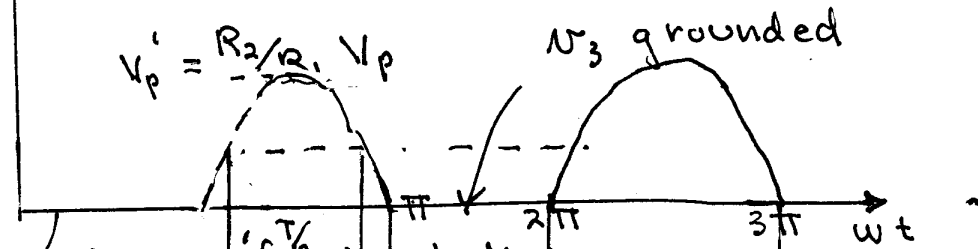Problem Set 5/

$v_1(t)$ (output after second diode) (before filter)




$$\text{Avg} = \frac{1}{T} \int_0^{T/2} v_p' \sin \omega t \, dt$$

Diodes on
so v_3 is
grounded

$$= \frac{v_p'}{T} \int_0^{\pi} \sin \alpha \, d\alpha = v_p' \frac{2}{\omega T} = \frac{v_p'}{\pi}$$

$v_2(t)$ (output after RC filtering)

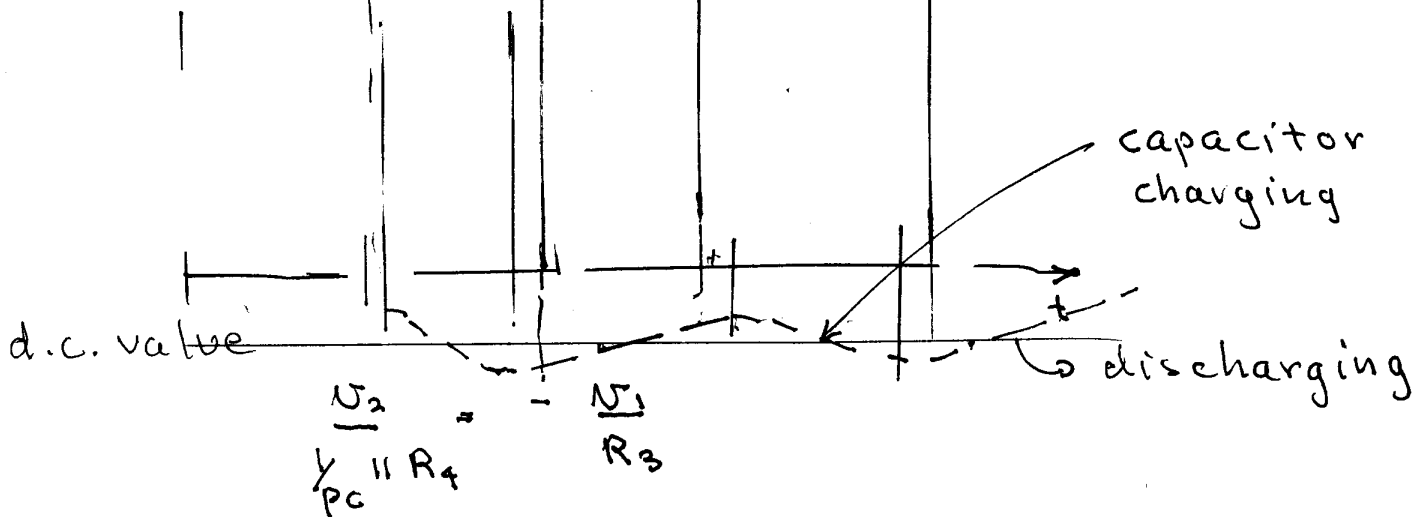

$$\therefore v_2 = - \frac{R_4}{1 + R_4 P C} \frac{v_1}{R_3} \quad R_4 C \text{ is large}$$

Governing D.E.

$$(1 + R_4 P C) v_2 = - \frac{R_4}{R_3} v_1$$

$$\left(\frac{1}{R_4 C} + \frac{d}{dt} \right) v_2 = - \frac{1}{R_3 C} v_1$$

$$\frac{d}{dt} (v_2 e^{t/R_4 C}) = - \frac{1}{R_3 C} e^{t/R_4 C}$$


Consider signal $v_1(t)$ above

The average of the signal $V_1(t)$

$$= V_p \int_0^{T/2} \sin \omega t \, dt \times \frac{1}{T} \times \frac{R_2}{R_1} = V_p \frac{R_2}{R_1} \times \frac{1}{T} \times \frac{1}{\omega} \times \frac{2\pi}{\omega} = V_p \frac{R_2}{R_1} \times \frac{1}{\pi}$$

This is the d.c. component.
which gets filtered out

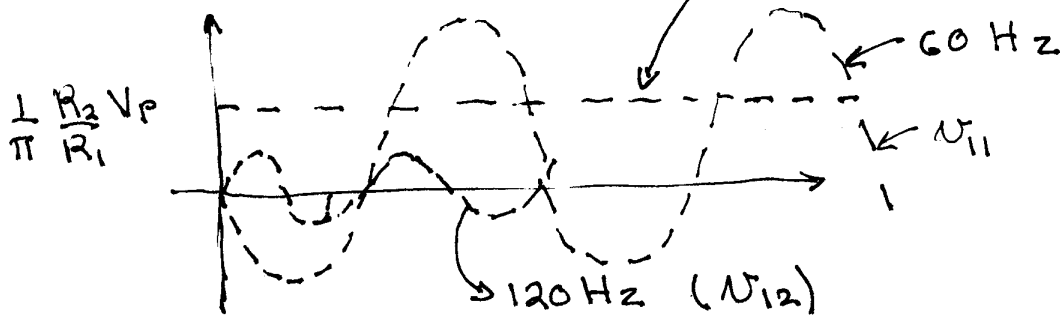model $V_1(t)$ as d.c. V_{10} $V_{10} + V_{11} + V_{12} + \dots$



Now look at V_2 for each of these

$p=0$ for d.c.

$$V_{20} = -\frac{R_4}{R_3} V_{10} = -\frac{R_4}{R_3} \frac{R_2}{R_1} \times \frac{1}{\pi}$$

$$V_{21} = -\frac{R_4}{1 + R_4 j\omega C} \frac{V_{11}}{R_3} \quad \text{for } 60 \text{ Hz } \omega = 2\pi \times 60$$

$$\approx -\frac{1}{j\omega C} \frac{V_{11}}{R_3} = -\frac{R_4}{R_3} \frac{R_2}{R_1} \frac{1}{j(\omega C R_4)}$$


$$\omega C R_4 \gg \pi$$

Thus V_{21} is small. (example $1 \text{ k}\Omega \times 50 \mu\text{F}$
 $\times 60 \text{ Hz}$) $= 50 \times 10^{-3} \times 2\pi \times 60 = 6\pi$


And output is close to a constant V_{20}

$$V_{20} = -\frac{R_4}{R_3} \frac{R_2}{R_1} \times \frac{1}{\pi}$$

LT Spice Problem 2 a.c. voltmeter

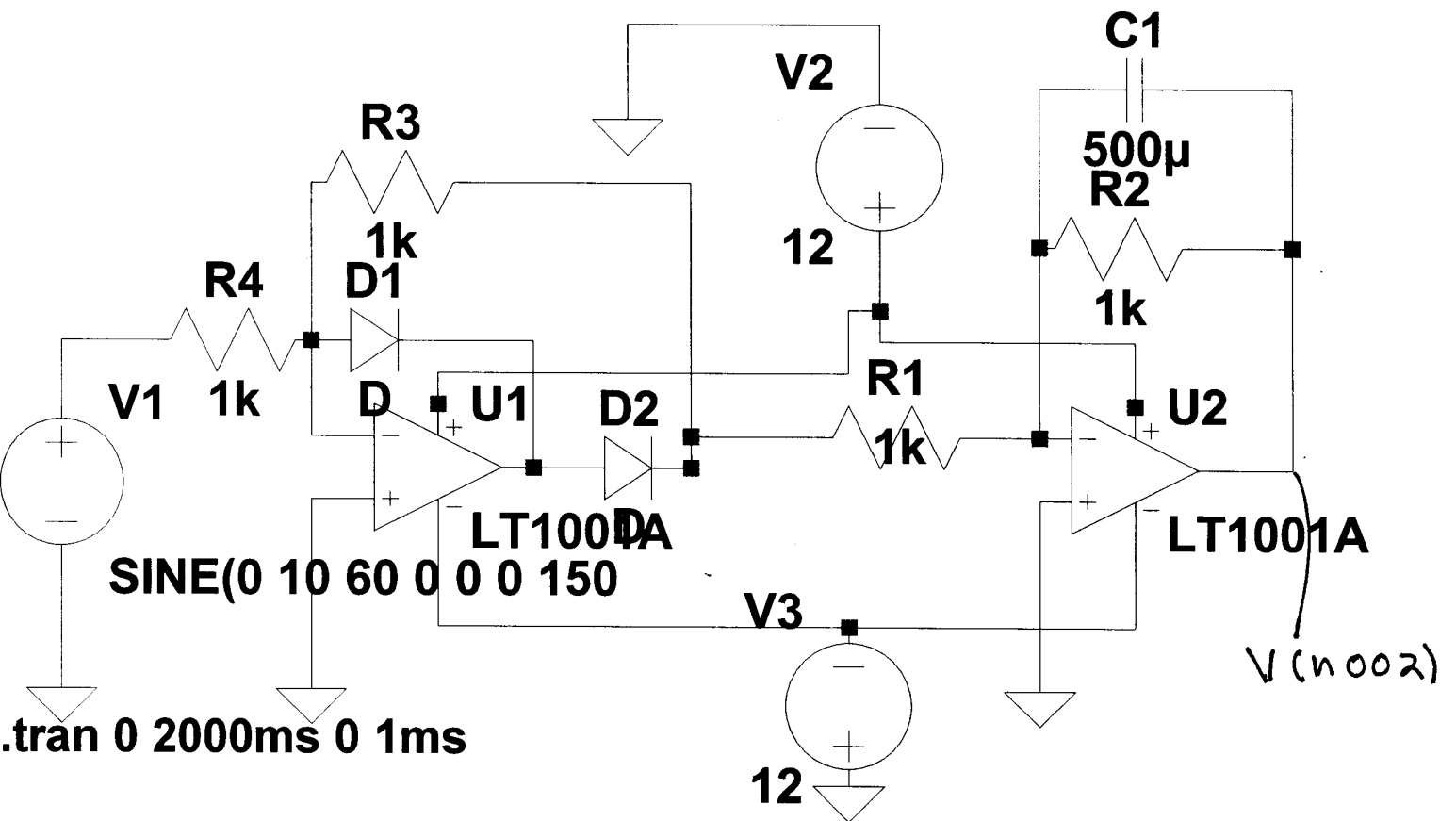

V(n002)

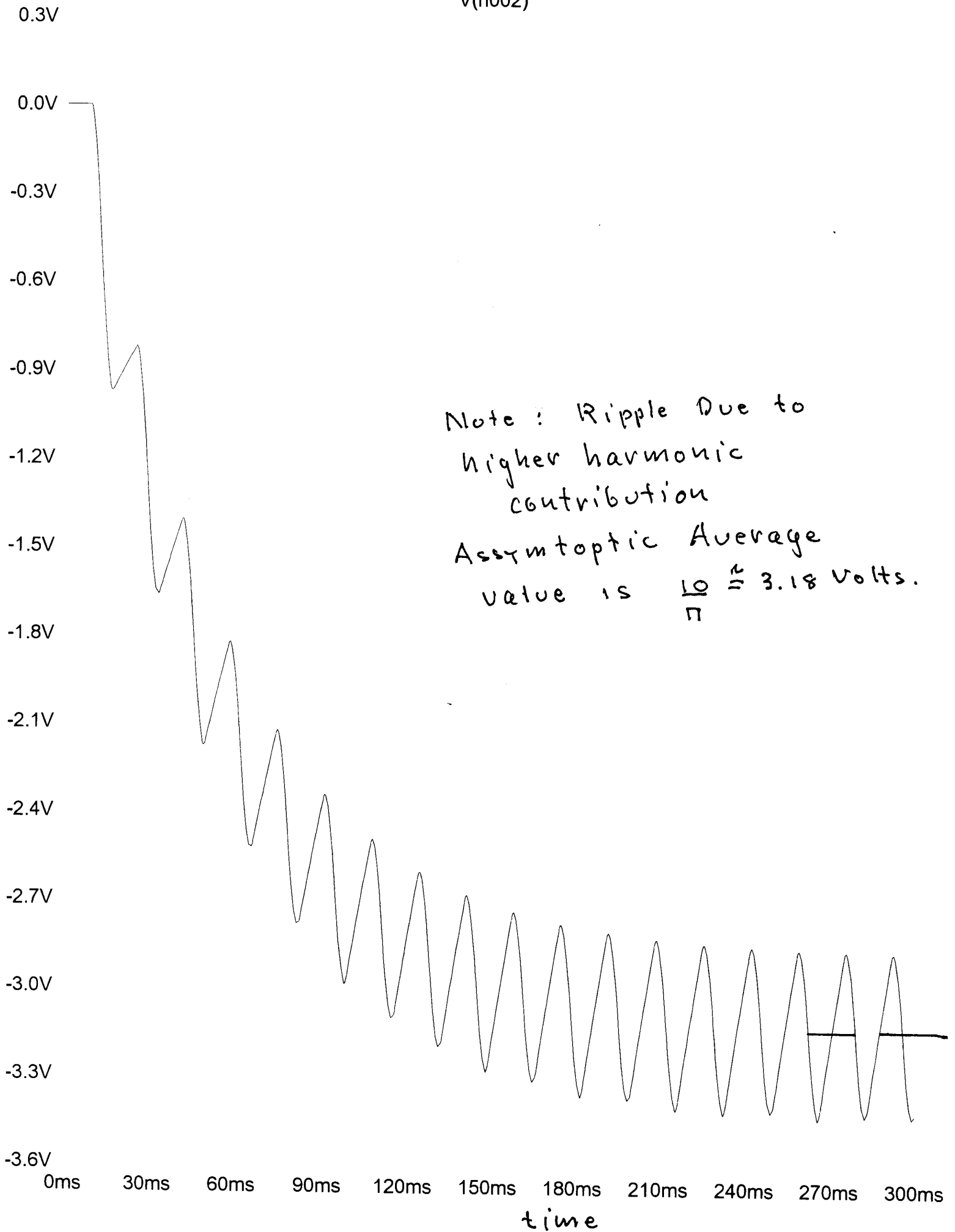


Problem No. 3 Hambley 12.20

FET $V_{t0} = 1V$ $K = .5 \text{ mA/V}^2$

$$i_D = K (V_{GS} - V_{T0})^2 = .5 (V_{GS} - 1)^2$$

$$= .5 (V_{GS} - 1)^2$$

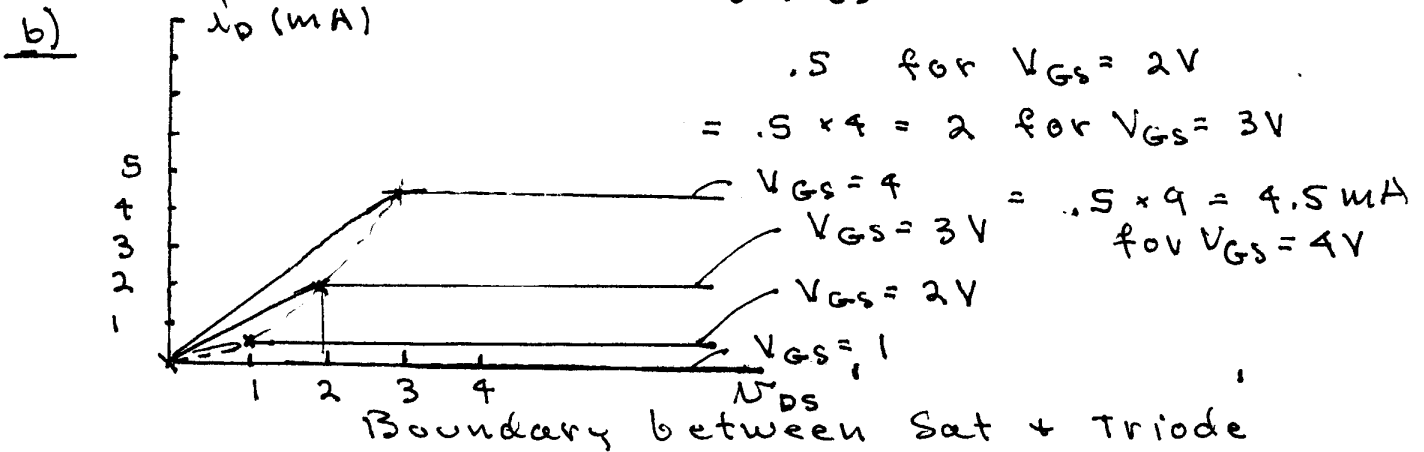
.5 for $V_{GS} = 2V$
 $= .5 \times 4 = 2$ for $V_{GS} = 3V$
 $= .5 \times 9 = 4.5 \text{ mA}$ for $V_{GS} = 4V$



$$V_{DS} = V_{GS} - V_T$$

$$= V_{GS} - 1$$

D.C. Load Line

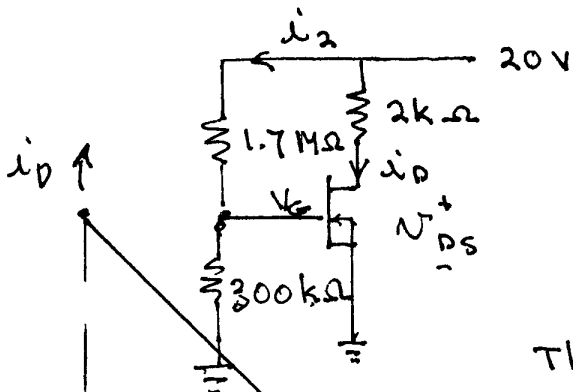


Volt divider for D.C.

$$V_G = 20 \frac{.3}{1.7+.3} \approx 20 \times \frac{.3}{2.0} = 3V$$

Thus

a) $V_{GS}(t) = 3 + \sin(20000\pi t)$

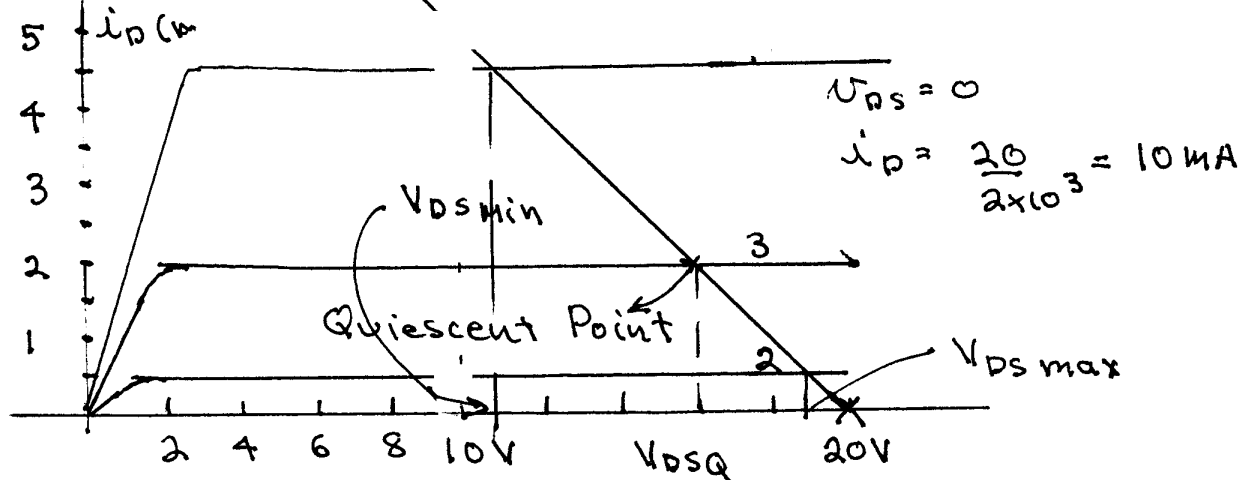c) Load line $V_{DS} = -2k\Omega i_D + 20$



$$V_{DS} = -2 \times 10^3 (K)(V_{GS} - V_{T0})^2 + 20$$

$$= -2 \times 10^3 \times 0.5 (V_{GS} - 1)^2 + 20$$

$$V_{GS \text{ min}} = 2 \text{ V}$$


$$\therefore V_{DS \text{ max}} = -1 + 20 = 19 \text{ V} \rightarrow$$

$$V_{DS \text{ min}} \text{ for } V_{GS \text{ max}} = 4 \text{ V}$$

$$= - (3)^2 + 20$$

$$= 11 \text{ V} \rightarrow$$

b Hambley 13.29

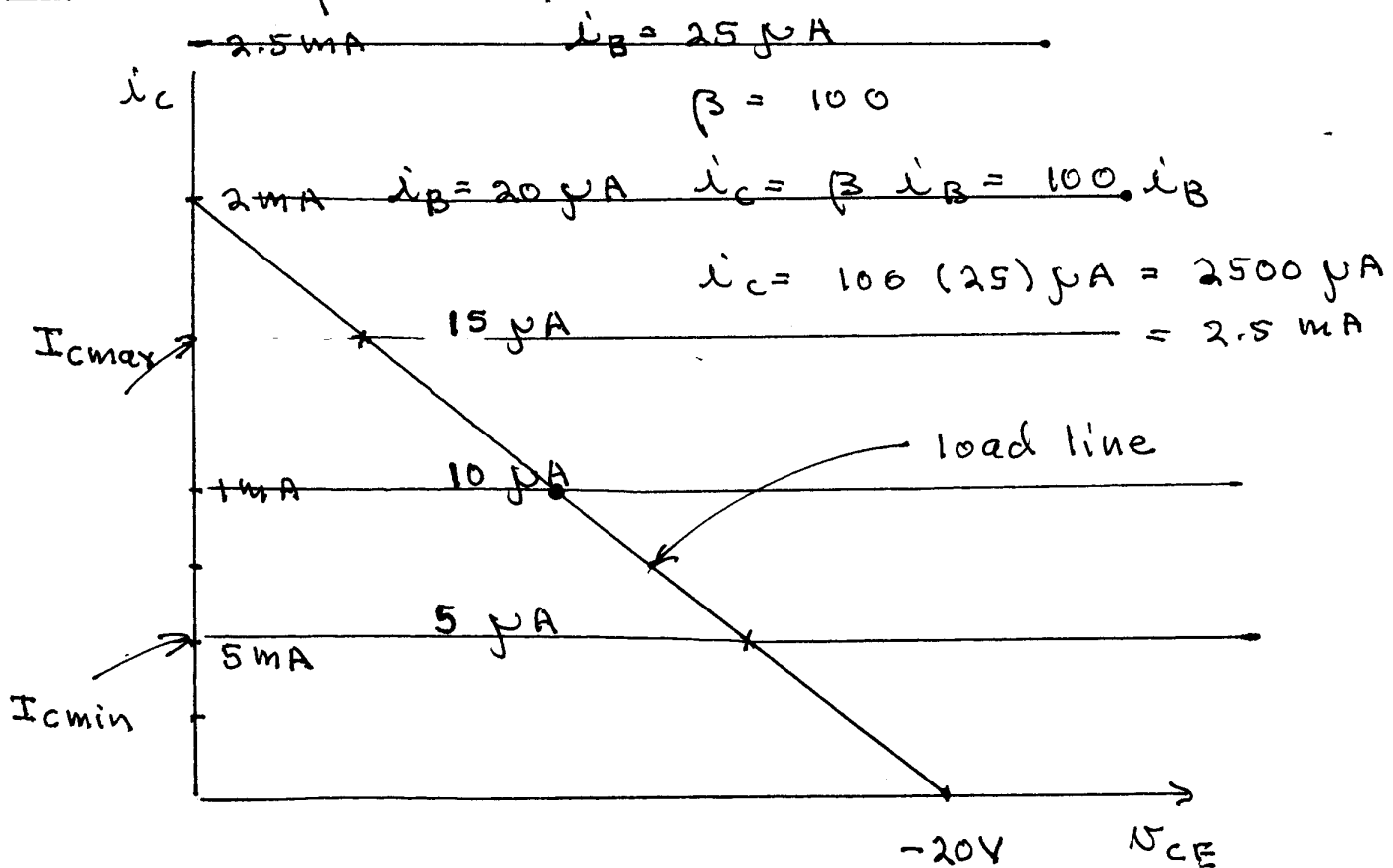

For case e) During the positive cycle the transistor is saturated so $I_C = 2 \text{ mA}$
 $I_{C \text{ min}}$ occurs for $I_B = 15 \mu\text{A}$ ($I_C = 1.5 \text{ mA}$)

Hambley 13.19

Note $i_c = 10 \text{ mA}$ for $i_B = 25 \mu\text{A}$

$$\beta = \frac{i_c}{i_B} = \frac{10}{.025} = 40$$

$$\beta = \frac{\alpha}{1-\alpha} \quad \text{or} \quad \alpha = \frac{\beta}{1+\beta} = \frac{40}{41}$$

Problem No. 4 Hambley 7.8

Binary $2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0$

64 | 32 | 16 | 8 | 4 | 2 | 1 → sum is 63
sum is 127

So 7 bits needed for 100

128 8th sum is 255
256 9th sum is 511

So 10 bits needed for 1000

512 10th
1024 11th
2048 12th
4096 → 8191
8192 14th
16384 15th
32768 16th

Large Number Law

$$2^n = 100 \quad n = 6.64 \rightarrow 7$$

Using large Number law

$$2^n = 1000 \quad n = 9.965 \rightarrow 10$$

12 bits

14 bits

15 bits

→ 16 bits

→ 17 bits

→ 18 bits

→ 19 bits

262154 19th

so 20 bits are needed

$$2^{20} = 2(262154) = 524308$$

Note Short Way

$$\sum_{i=0}^{n-1} 2^i \approx 2^n$$

Law of large numbers

We want this to be 10^6 so $2^n \approx 10^6 \Rightarrow n = \log_2 10^6 = 19.931 \rightarrow 20$

b) Hambley 7.27

a) $F = (A+B)\bar{C}$


b) $F = (A+B) + \bar{B}\bar{C}$

c) $F = AB + \bar{B}\bar{C} + D$

c) Hambley 7.46

$F = AB + CD$


$= \overline{\overline{AB} \overline{CD}}$

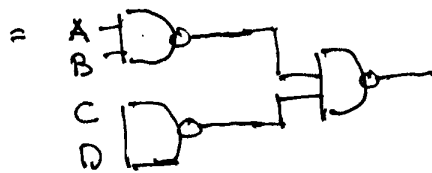

Hambley 7.47

$= \overline{\overline{(A+B)} + \overline{C+D}}$

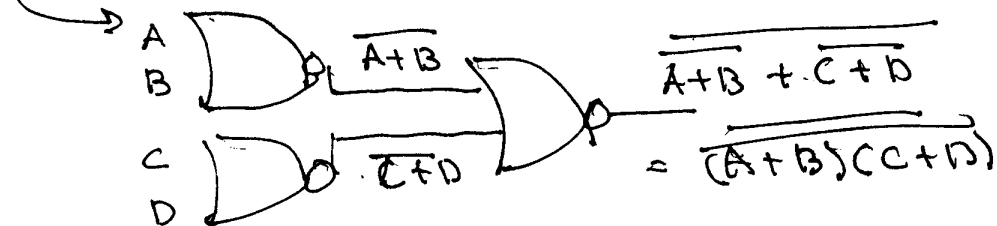since $\overline{A+B} + \overline{C+D} = \overline{(A+B)(C+D)}$



Problem No. 5 Hambley 7.54

Inputs A, B, C

$$D = \sum m(0, 3, 4)$$

↑
these are the terms in truth table
which give 1 for output

A	B	C	F	
0	0	0	1	$\bar{A} \bar{B} \bar{C} = 0$
0	0	1	0	
0	1	0	0	$\bar{A} B \bar{C}$
0	1	1	1	$\bar{A} B C$
1	0	0	1	$A \bar{B} \bar{C}$
1	0	1	0	
1	1	0	0	
1	1	1	0	

		AB		C	
		0	1	0	1
0	0	0	0	0	0
0	1	0	1	0	1
1	0	0	0	1	0
1	1	0	1	0	1

b) $F = \bar{A} \bar{C} + \bar{B} \bar{C}$
minimum SOP

c) POS

$$D = \prod (1, 2, 5, 6, 7)$$

$$F = (A + B + \bar{C})(A + \bar{B} + C)(\bar{A} + B + \bar{C})$$

$$(\bar{A} + \bar{B} + C)(\bar{A} + \bar{B} + \bar{C})$$

or apply de Morgan's Theorem to

$$F = \bar{A} \bar{C} + \bar{B} \bar{C}$$

$$= \overline{\overline{\bar{A} \bar{C} + \bar{B} \bar{C}}}$$

$$= \overline{(A + C)(B + C)}$$

or use Karnaugh map for \bar{F}

C \ AB	00	10	11	01
0	0	0	1	0
1	1	1	1	1

$$\bar{F} = C + AB$$

$$F = \overline{C + AB}$$

$$= \bar{C} \overline{AB}$$

$$= \bar{C} (\bar{A} + \bar{B})$$

Problem No. 6

Hambley 14.25

$$a) \quad \frac{V_o - V_A}{R} - \frac{V_A}{R} + i_{in} = 0$$

V_- is grounded so

$$V_A = -i_{in} R$$

$$\therefore \frac{V_o}{R} + 2 i_{in} + i_{in} = 0$$

$$\therefore \boxed{V_o = 3 R i_{in}}$$

b) Looking in from V_o ($i_{in} = 0$) (input open)

$$i_{R_2} = \frac{V_o - V_A}{R} = \frac{V_o}{R}$$

\therefore output Resistance = R

c) Input resistance

$$V_{in} = 0 \quad \frac{V_{in}}{i_{in}} = 0 = R_{in}$$

d) Transimpedance Amplifier

Problem No. 7 - 6.24

$$V_{in} = 5 \cos(\omega_0 t) + 5 \cos \omega_2 t + 5 \cos \omega_4 t$$

$$\omega_0 = 500 \pi$$

$\omega_2 = 2\omega_0$
 $\omega_4 = 4\omega_0$

even order harmonics of the fundamental at ω_0

$$V_{out} = \frac{\frac{1}{p_c}}{\frac{1}{p_c} + R} V_{in}(t)$$

For $e^{+j\omega t}$ terms $\omega = \omega_0, 2\omega_0, 4\omega_0$

$$V_{out} = \frac{\frac{5}{2}}{1 + j\omega CR}$$

$$V_{out}(t) = 2 \operatorname{Re} \left(\sum_{m=1,2,4} \frac{\frac{5}{2}}{1 + j\omega_m CR} e^{j\omega_m t} \right)$$

$$\omega_0 RC = 318.3 \times 10^{-6} \cdot 500 \pi = .5$$

$$= 5 \operatorname{Re} \left[\frac{1}{1 + .5j} e^{j500\pi t} + \frac{1}{1 + j} e^{j1000\pi t} \right]$$

convert to polar (with calculator!)

$$+ \frac{1}{1 + 2j} e^{j2000\pi t}$$

$$= 5 \operatorname{Re} \left[\left(\frac{1}{1.12} e^{j.46} \right) e^{j500\pi t} + \frac{1}{\sqrt{2}} e^{j\pi/4} e^{j1000\pi t} \right]$$

note how it is decreasing the amplitude of higher harmonics. This is a low pass filter

$$= 5 \left[.89 \cos(500\pi t - .46) + .707 \cos(1000\pi t - \pi/4) + .447 \cos(2000\pi t - 1.11) \right]$$