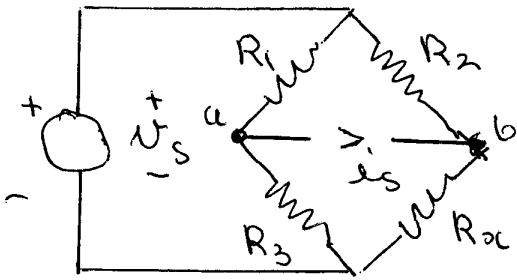


Problem 2.101 - Wheatstone Bridge



Balanced  
 $i_s = 0$  use voltage divider

$$V_{ab} = V_s \left( \frac{R_3}{R_1 + R_3} - \frac{R_2}{R_2 + R_x} \right)$$

$R_1 = 10k\Omega$ ,  $R_3 = 3419\Omega$ ,  $R_2 = 1k\Omega$

$$\frac{R_3}{R_1 + R_3} = \frac{R_2}{R_2 + R_x} \quad \text{solve for } R_x$$

Prob No. 1

Problem 2.102 Now the  $i_s \neq 0$

Problem suggests using Thevenin


$$V = V_{\text{open circuit}} + i R_{\text{eq}} \quad \left( \begin{array}{c} \text{Req} \\ \text{V}_{\text{open circuit}} \end{array} \right)$$

$$V_{\text{open circuit}} = V_s \left( \frac{R_3}{R_1 + R_3} - \frac{R_2}{R_2 + R_x} \right)$$

$$V_{\text{open circuit}} = V_s \left( \frac{R_3 R_x - R_2 R_1}{(R_1 + R_3)(R_2 + R_x)} \right) \quad \text{Eq (1)}$$


To find  $R_{\text{eq}}$  set  $V_{\text{open circuit}} = 0$

Equivalent is

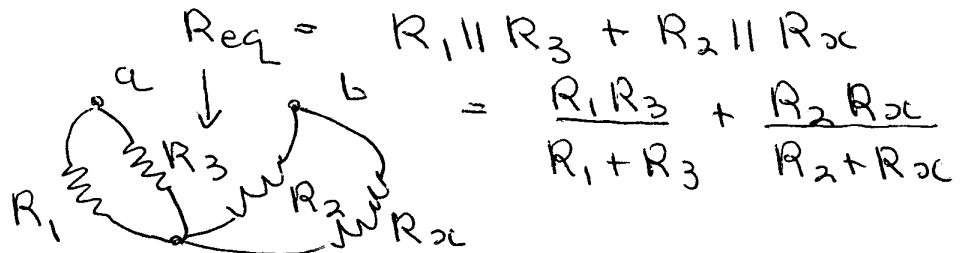


a) when bridge is balanced  $i_s = 0$   $V_{ab} = 0$   
So result above holds (Eq 1)

b)

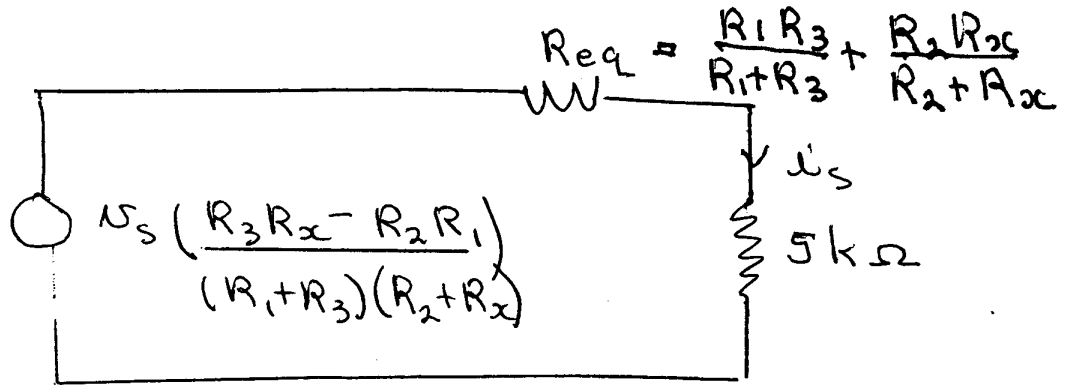
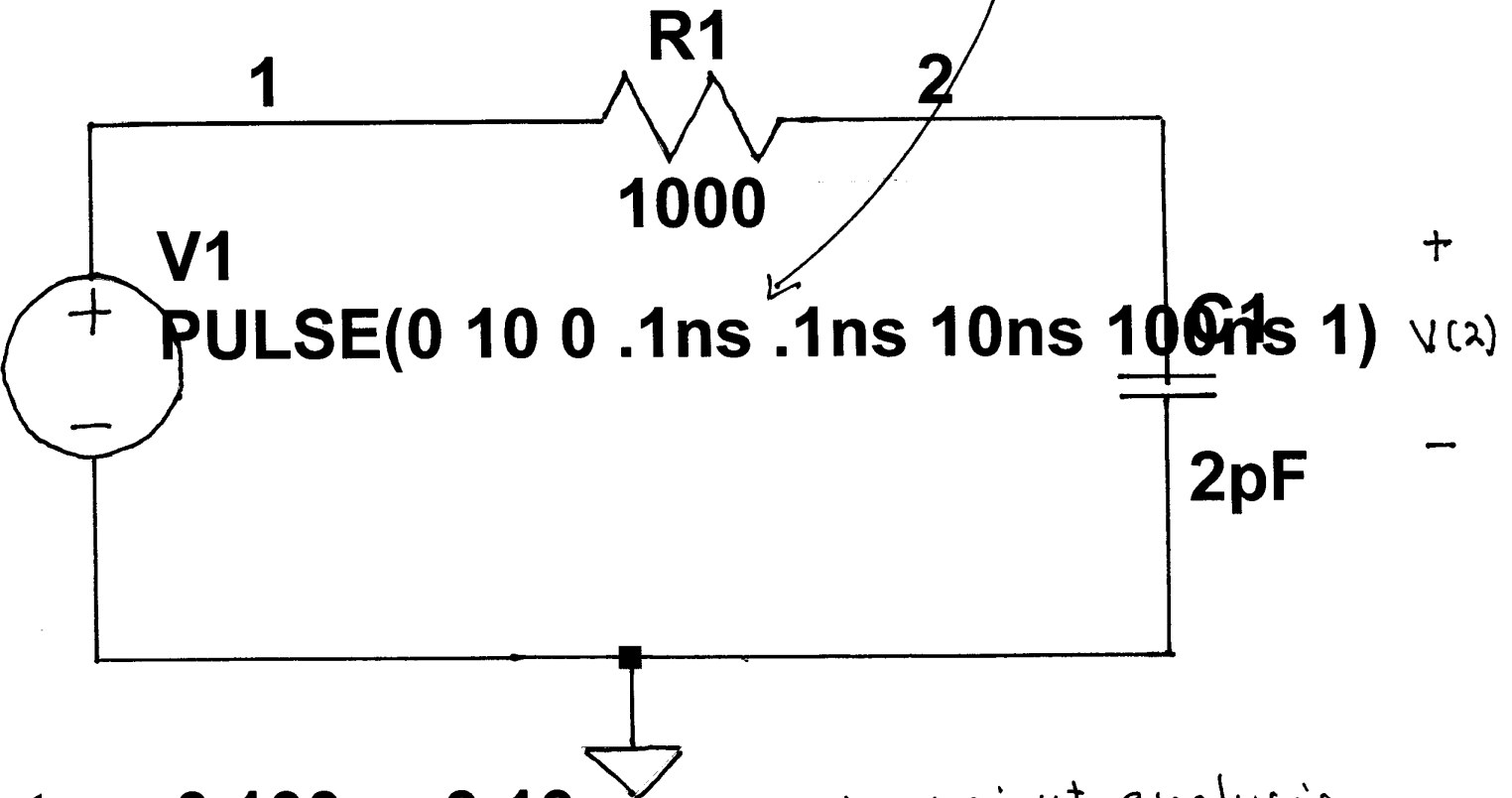
## Fun With LT Spice . (Problem 2)


Pulse starting at 0 Volts ramping up to 10 Volts with a rise-time .1nsec, fall time of .1nsec, 10nsec. in duration a period of 100nsec. 1 cycle plotted. This is the Spice netlist statement



**.tran 0 100ns 0 10ns** ← transient analysis  
from 0 to 100nsec for a pulse from 0  
to 10nsec

Result for V(2) next page

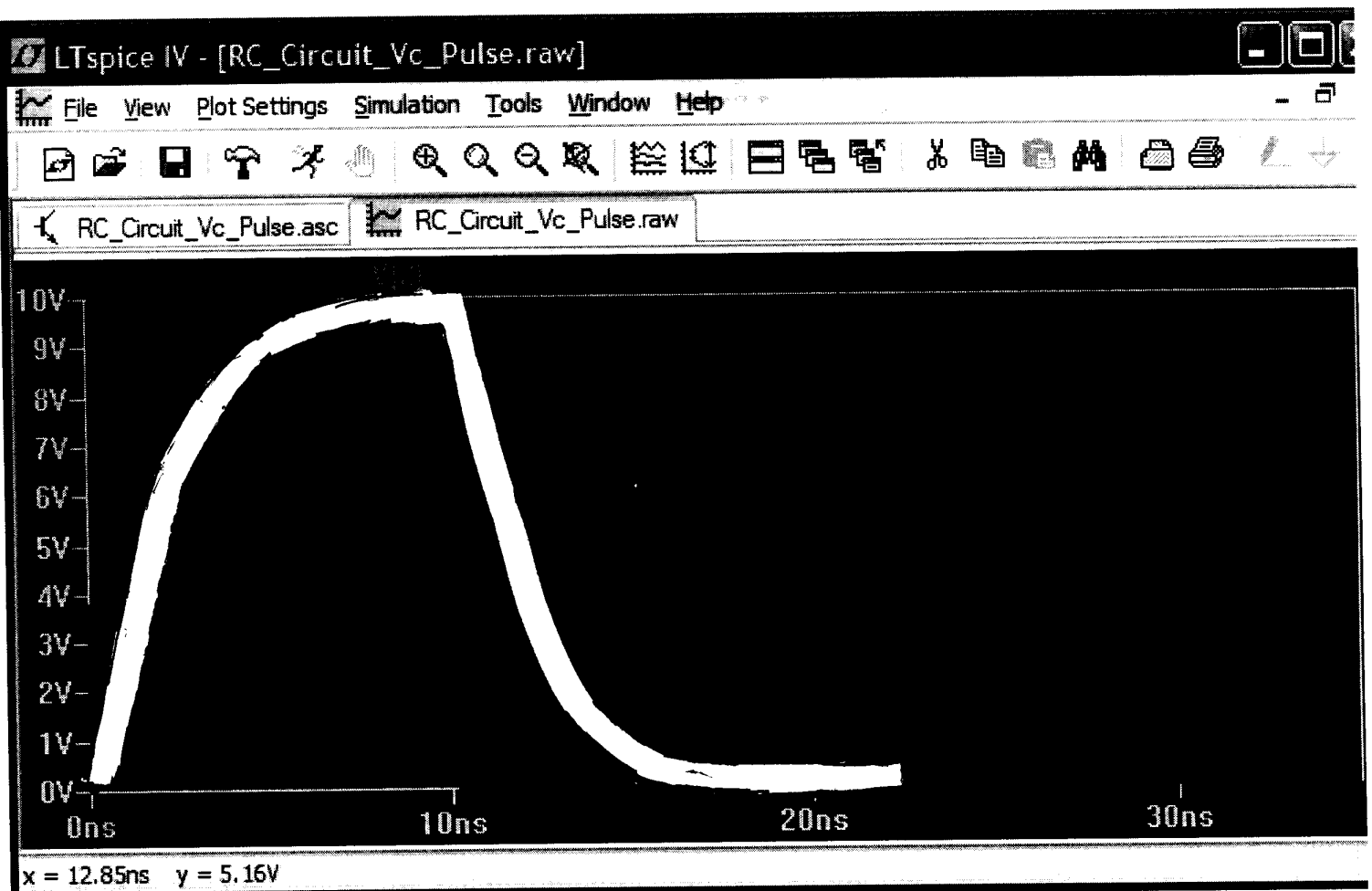
(Note your problem asked for a 4nsec delay  
Here it is taken as 0. Just shift these  
results by 4nsec to obtain the delay)



Can download LTspice from  
[www.linear.com](http://www.linear.com)

Getting started guide

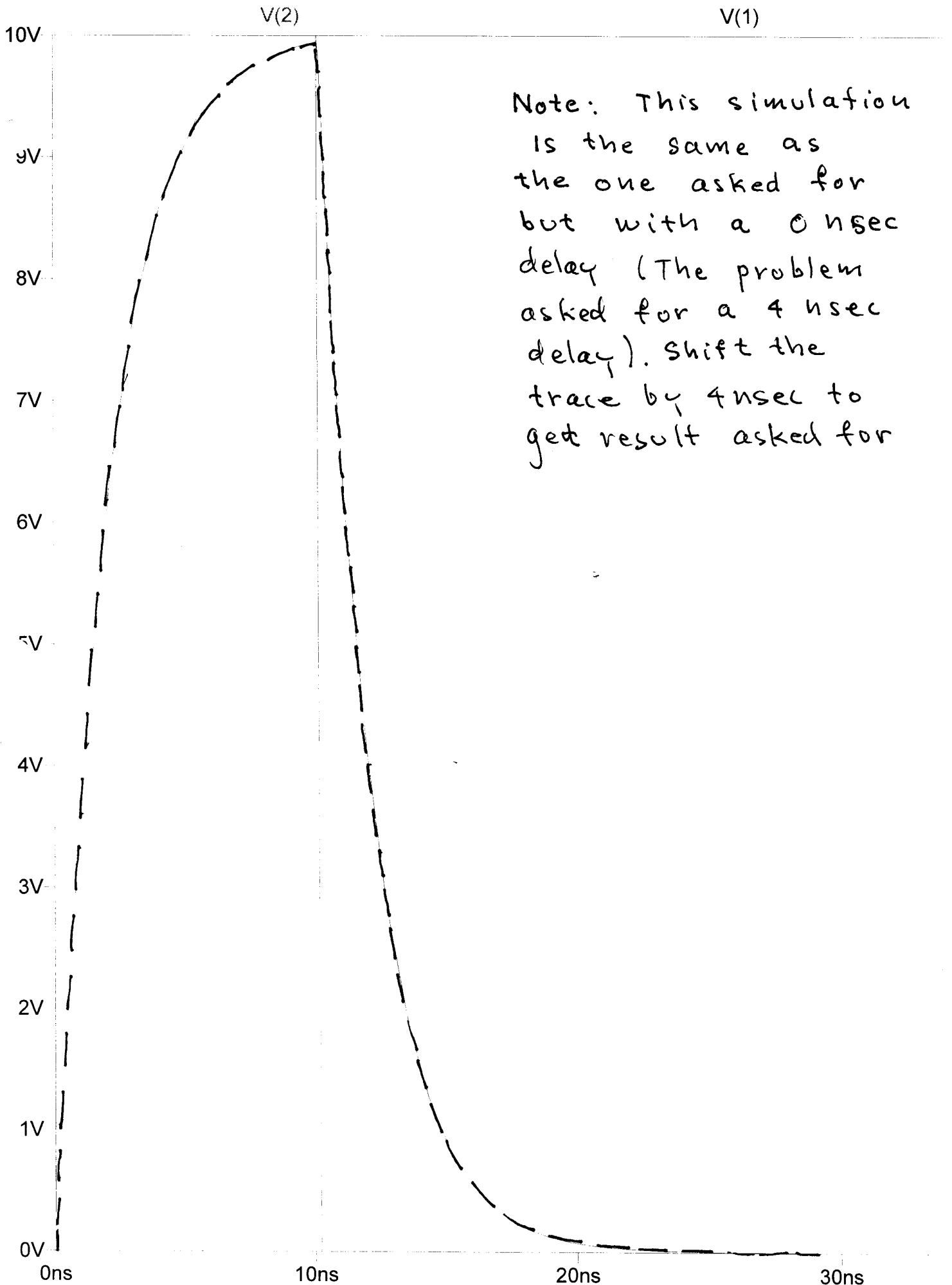[www.linear.com/designtools/software/  
LTspice Getting Started Guide.pdf](http://www.linear.com/designtools/software/LTspice%20Getting%20Started%20Guide.pdf)



Note: This simulation is the same as the one asked for but with a 0 nsec delay (The problem asked for a 4 nsec delay). Shift the trace by 4 nsec to get result asked for

Ans?  $V_o \approx -R_f i_s$  (7)  
 The sub-circuit disappears

Node ①

$$\textcircled{1} \quad V_i \left( \frac{1}{R_i} + \frac{1}{R_s} \right) + \frac{V_i - V_o}{R_f} = +i_s$$

Node ②

$$\textcircled{2} \quad \frac{V_o + A V_i}{R_o} + \frac{V_o - V_i}{R_f} = 0$$

$$\textcircled{1} \quad V_i \left( \frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f} \right) = +i_s + \frac{V_o}{R_f}$$

sub in ②

$$V_o \left( \frac{1}{R_o} + \frac{1}{R_f} \right) + \left( \frac{A}{R_o} - \frac{1}{R_f} \right) \left( +i_s + \frac{V_o}{R_f} \right)$$

$$\frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f}$$

= 0

$$V_o \left( \frac{1}{R_o} + \frac{1}{R_f} + \frac{1}{R_f} \left( \frac{A-1}{R_o R_f} \right) \frac{1}{\frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f}} \right) + \left( \frac{A-1}{R_o R_f} \right) \frac{i_s}{\left( \frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f} \right)} = 0$$

a)


so

$$V_o / i_s = \frac{- \left( A/R_o - 1/R_f \right)}{\left( \frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f} \right) \left( \frac{1}{R_o} + \frac{1}{R_f} + \frac{1}{R_f} \left( \frac{A-1}{R_o R_f} \right) \frac{1}{\left( \frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f} \right)} \right)}$$

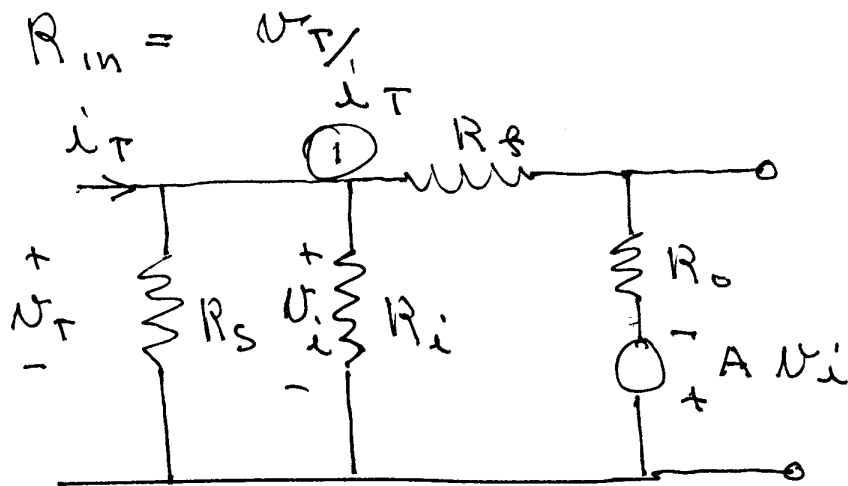b) Input Resistance - Resistance measured (8) when looking into terminals a) and b)

Note; Should specify condition of the output terminals. We shall assume them to be open

Approach Excite with a test voltage  $V_T$  and calculate current  $i_T$  then



observe  $V_i = V_T$      $A V_i = A V_T$

Use KCL at (1)


$$i_T = \frac{V_T}{R_s} + \frac{V_T}{R_i} + \frac{V_T - (-A V_T)}{R_o}$$

$$\text{Thus } \left| \frac{V_T}{i_T} = R_{in} = \frac{1}{\frac{1}{R_s} + \frac{1}{R_i} + \frac{(1+A)}{R_o}} \right.$$

c) When  $A \rightarrow \infty$

$$\left| \begin{array}{l} \text{a) } \rightarrow \frac{V_o}{i_s} = -R_f \text{ (as expected)} \\ \text{b) } \rightarrow R_{in} \rightarrow 0 \end{array} \right.$$

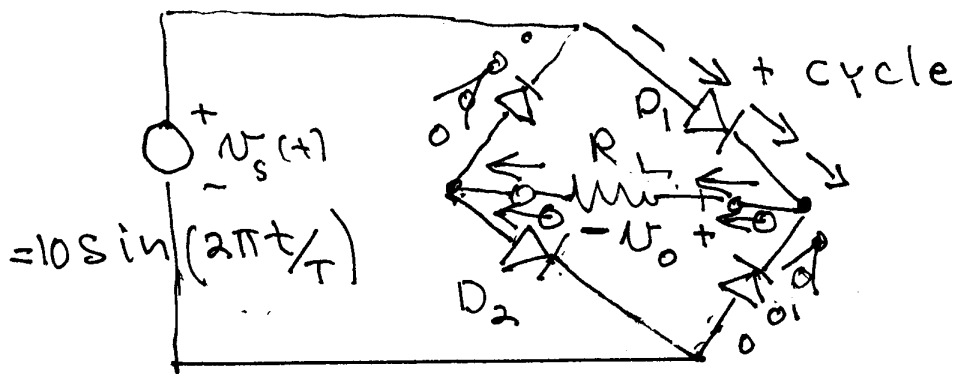Problem No 4 : The basic bridge rectifier (a)




Picture is clearer if we include a finite load resistance  $R_L$ .

During the positive cycle of  $\sin(2\pi t/T)$  the current follows the  $\rightarrow$ 's, since  $D_1$  and  $D_2$  are forward-biased and are thus shorts.

During the negative cycle  $D_1$  and  $D_2$  are open (reverse-biased) and the other two are forward-biased so shorted. The current then follows the  $\leftarrow$ 's,

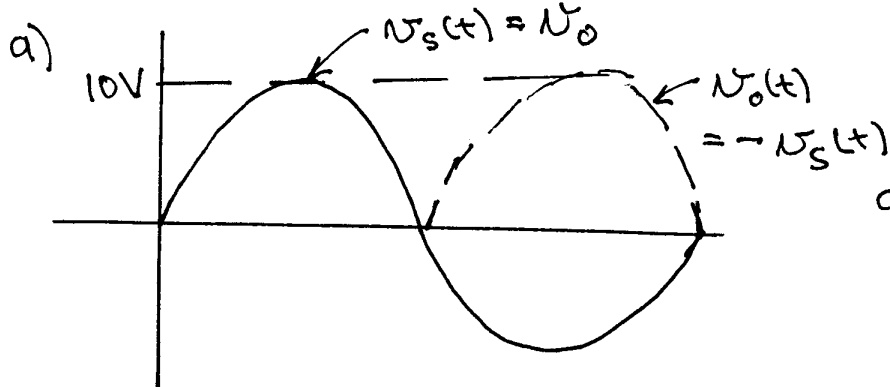
The current goes through the load resistor in the same direction regardless of the sign of  $V_s(t)$ . Thus



b)  $\int_0^T V_s(t) \frac{dt}{T} = 0$

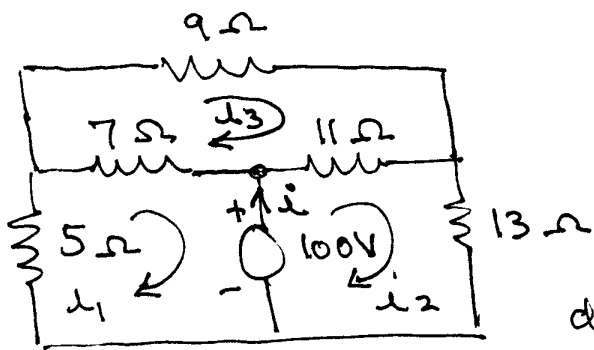c)  $\int_0^T U_o(t) \frac{dt}{T} = \int_0^{T/2} U_o(t) dt \frac{2}{T}$   
 $= \frac{20}{\pi}$





Power delivered  
 $= 100V \times i$   
 $= \text{sum of powers}$   
dissipated in the resistors

KVL for Meshes ① ② ③ in matrix form for  
 $i_2 + i_3$  in opposite directions

Symmetrical for this circuit (all resistors are reciprocal)

$$\begin{pmatrix} 5+7 & -7 & 0 \\ 0 & 11+13 & -11 \\ -7 & -11 & 11+7+9 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} -100 \\ 100 \\ 0 \end{pmatrix}$$

want to find  $i_1$  &  $i_2$

$$i_1 = \begin{pmatrix} -100 & 0 & -7 \\ 100 & 24 & -11 \\ 0 & -11 & 27 \end{pmatrix} = \frac{[-100(24 \times 27 - 11^2) - 7(100)(-11)]}{\Delta}$$

$$\Delta = 12(24 \times 27 - 11^2) - 7(7 \times 24)$$

$$i_2 = \begin{pmatrix} 12 & -100 & -7 \\ 0 & 100 & -11 \\ -7 & -11 & 27 \end{pmatrix} = \frac{[12(100 \times 27 - 11^2) - 7(100 \times 11 + 7 \times 100)]}{\Delta}$$

$i_1$  and  $i_2$  are  $-8.741$  and  $3.846$  amps respectively

$$i = (i_2 - i_1) = 12.597$$


$\therefore$  power consumed = 1259. Watts

# Flow graph soln

$$i_1 = \frac{7}{12} i_3 - \frac{100}{12}$$

$$i_2 = \frac{11}{24} i_3 + \frac{100}{24}$$
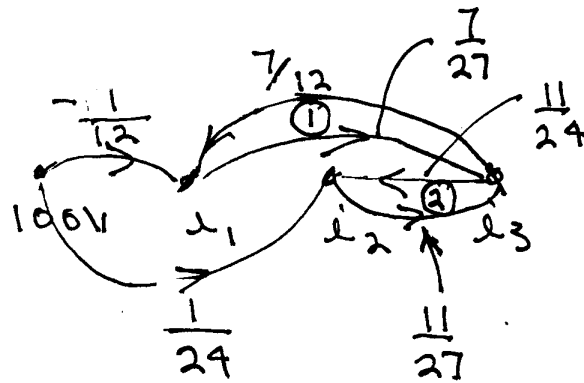
$$i_3 = \frac{11}{27} i_2 + \frac{7}{27} i_1$$



two loops ①  $\frac{7}{27} \times \frac{7}{12}$  ②  $\frac{(11)^2}{27 \times 24}$

$$\begin{aligned} \therefore \det &= 1 - \frac{49}{27(12)} - \frac{(11)^2}{27 \times 24} \\ &= 1 - \frac{1}{27(24)} \left( \frac{49 \times 2}{98} + 121 \right) \\ &= 1 - \frac{1}{27(24)} (219) = \frac{27 \times 24 - 219}{27 \times 24} \\ &= \frac{429}{648} = \frac{143}{216} \end{aligned}$$

$$i_1 = 100 \left( \underbrace{-\frac{1}{12} \left( 1 - \frac{11 \times 11}{27 \times 24} \right)}_{\substack{\text{New term} \\ \text{Sum of Loops that} \\ \text{do not touch} \\ \text{this path}}} + \frac{1}{24} \times \frac{11}{27} \times \frac{7}{12} \right) \frac{216}{143}$$

1 - "Sum of Loops"

$$= 100 \left( -\frac{2}{24} + \frac{1}{12 \times 27 \times 24} (11) \times 18 \right) \frac{216}{143}$$

$$= \frac{100}{18} \left( -2 + \frac{2}{36} \times 11 \right) \left( \frac{9}{143} \right)$$

$$i_1 = -100 \left( \frac{25}{18} \right) \frac{9}{143} = -8.741$$

$$i_2 = 100 \left( \frac{1}{24} \left( 1 - \frac{7}{27} \times \frac{7}{12} \right) - \frac{1}{12} \times \frac{7}{27} \times \frac{11}{24} \right) \times \frac{216}{143}$$


(1 - sum of Non Touching Loops)

$$= 100 \left( 1 - \frac{7 \times 18}{12 \times 27} \right) \times \frac{9}{143}$$

$$= 100 \left( \frac{18 - 7}{18} \right) \times \frac{9}{143} = \frac{100 \times 11}{2} \times \frac{1}{143}$$

$$= 3.846 \text{ amps.}$$

Problem No. 6 2-89 Hambley

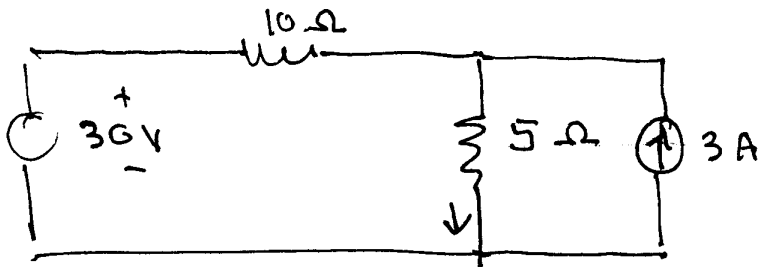

$$i = i_1 + i_2$$

$\uparrow$   
 due to  
 30V  
 source  
 with 3A set to 0 (open)

$\rightarrow$  due to 3A source with  
 30V set to 0 (short it)

$$\therefore i_1 = \frac{30V}{(5+10)\Omega} = \frac{30}{15} = 2A$$

$$i_2 = 3A \rightarrow$$

$$\therefore \boxed{i = 5A}$$

