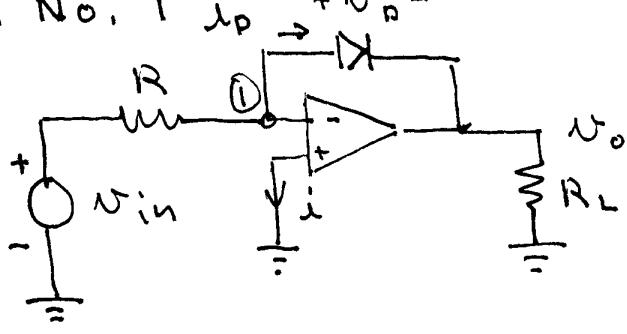


Problem No. 1



$$i_o = I_s e^{(V_o/nV_T)}$$

Ideal OP-Amp. $V_- = V_+ = 0$; $i = 0$

KCL at ①

$$\begin{aligned} \frac{V_{in}}{R} &= i_o = I_s e^{\frac{V_o}{nV_T}} \\ &= I_s e^{-\frac{V_o}{nV_T}} \text{ since} \end{aligned}$$

$$V_o = -V_o$$

$$\therefore V_o = -\left\{ \ln \left(\frac{i_o}{I_s} \right) \right\} (nV_T) = -\left(\ln \frac{V_{in}}{R I_s} \right) V_T n$$

Note V_o negative ($V_{in} > 0$)

$$= -(\ln V_{in}) (V_T n) + (\ln R I_s) V_T$$

Thus $V_T n$ is the slope of the line

V_o versus $\ln V_{in}$

$$R = 1k\Omega \quad V_{in} = 60 \text{ mV} \quad nV_T = 47.43 \text{ mV}$$


$$V_o = -455 \text{ mV}$$

$$\text{Thus } -455 = -\left(\ln \frac{60}{10^3 I_s} \right) 47.43$$

$$\frac{10^3 I_s}{60} = e^{-455/47.43}$$

$$\begin{aligned} I_s &= 6 \times 10^{-2} \times 6.8 \times 10^{-5} \text{ mA} \\ &= 40.8 \times 10^{-11} \text{ Amps} \end{aligned}$$

(1b) Logarithmic Amplifier

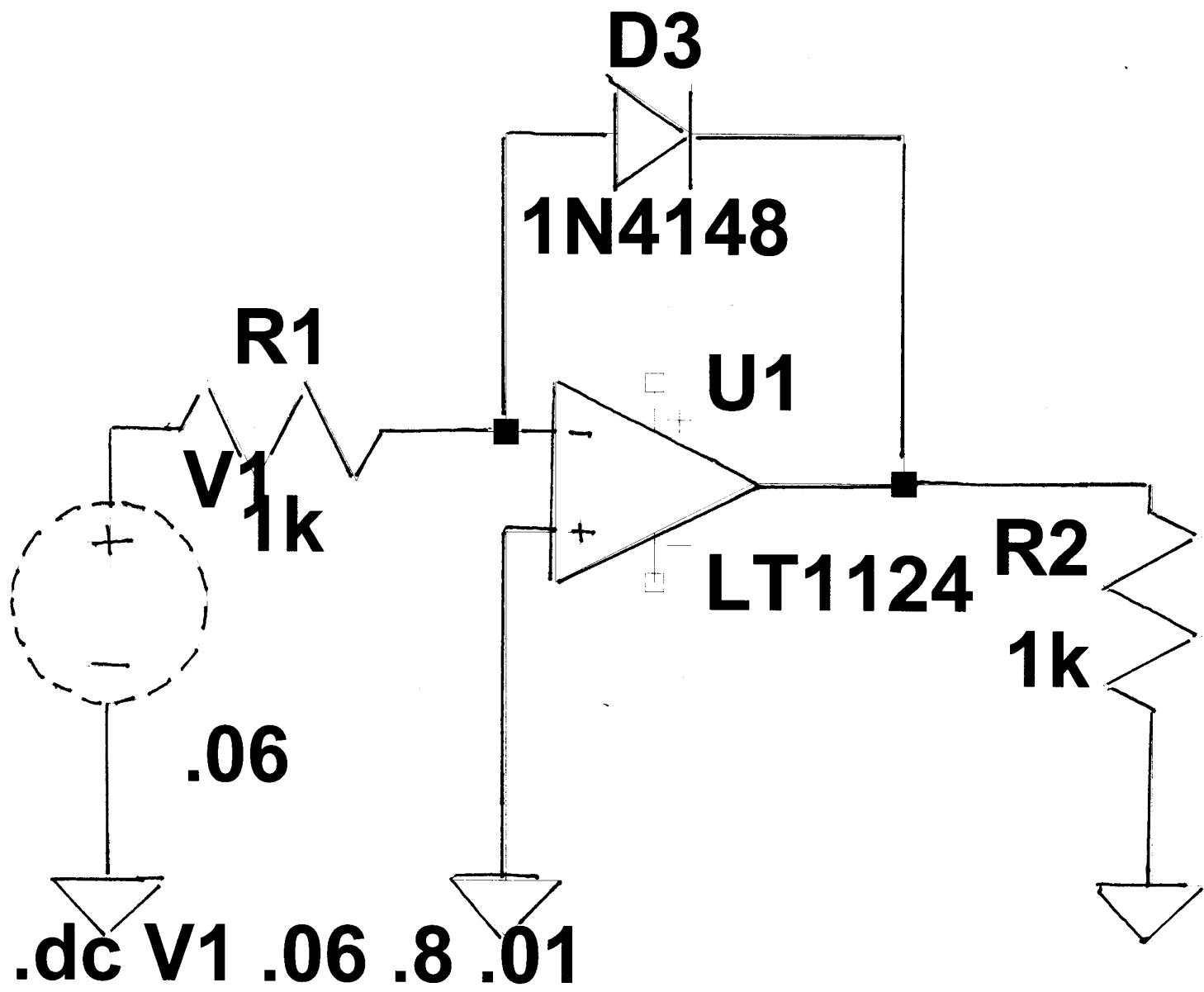

-450mV

-460mV

-470mV

-480mV

-490mV

-500mV

-510mV

-520mV

-530mV

-540mV

-550mV

-560mV

-570mV

-580mV

60mV

130mV

200mV

270mV

340mV


480mV

620mV

760mV


measured slope = $nV_T = 47.43 \text{ mV}$
at 300°K $V_T \approx 26 \text{ mV}$
so $n = 1.82$

Measuring Voltage Offset With Comparator

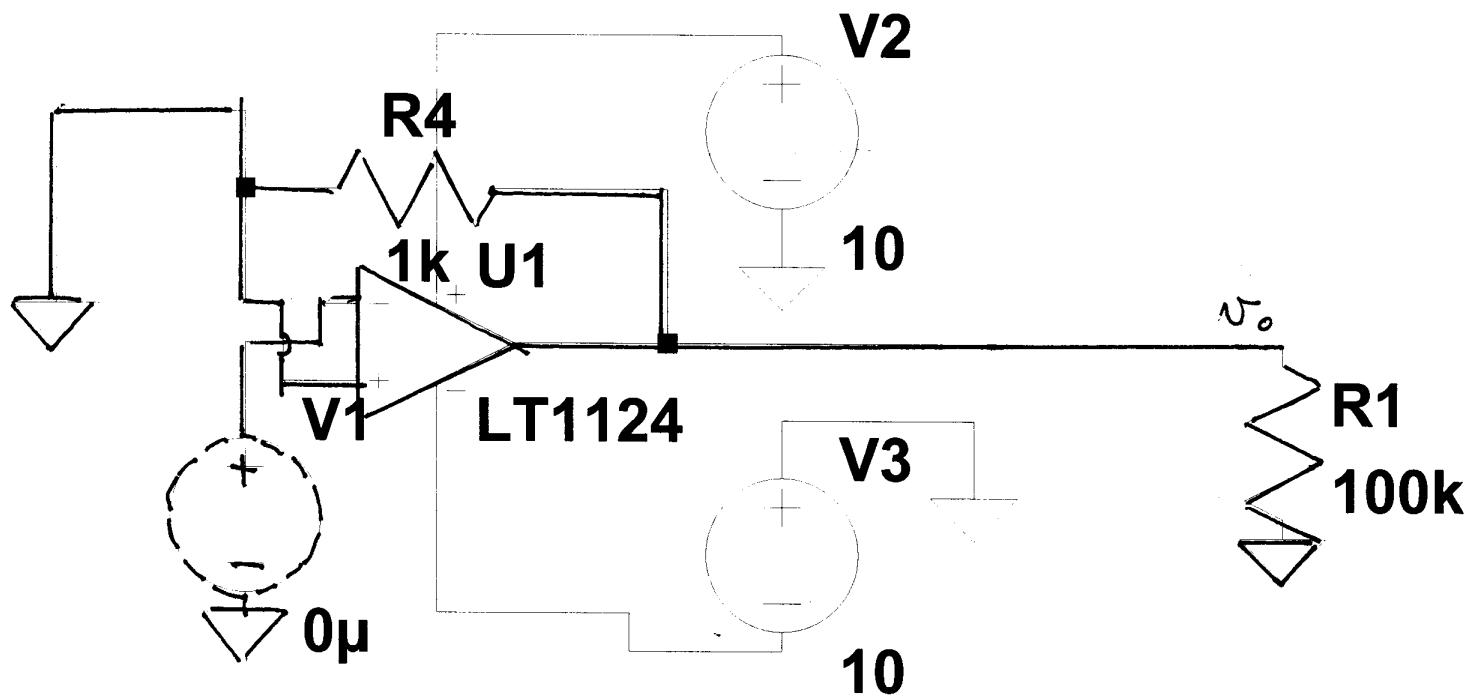


.dc V1 -50u 50u 1u


Saturation N_o versus V_I

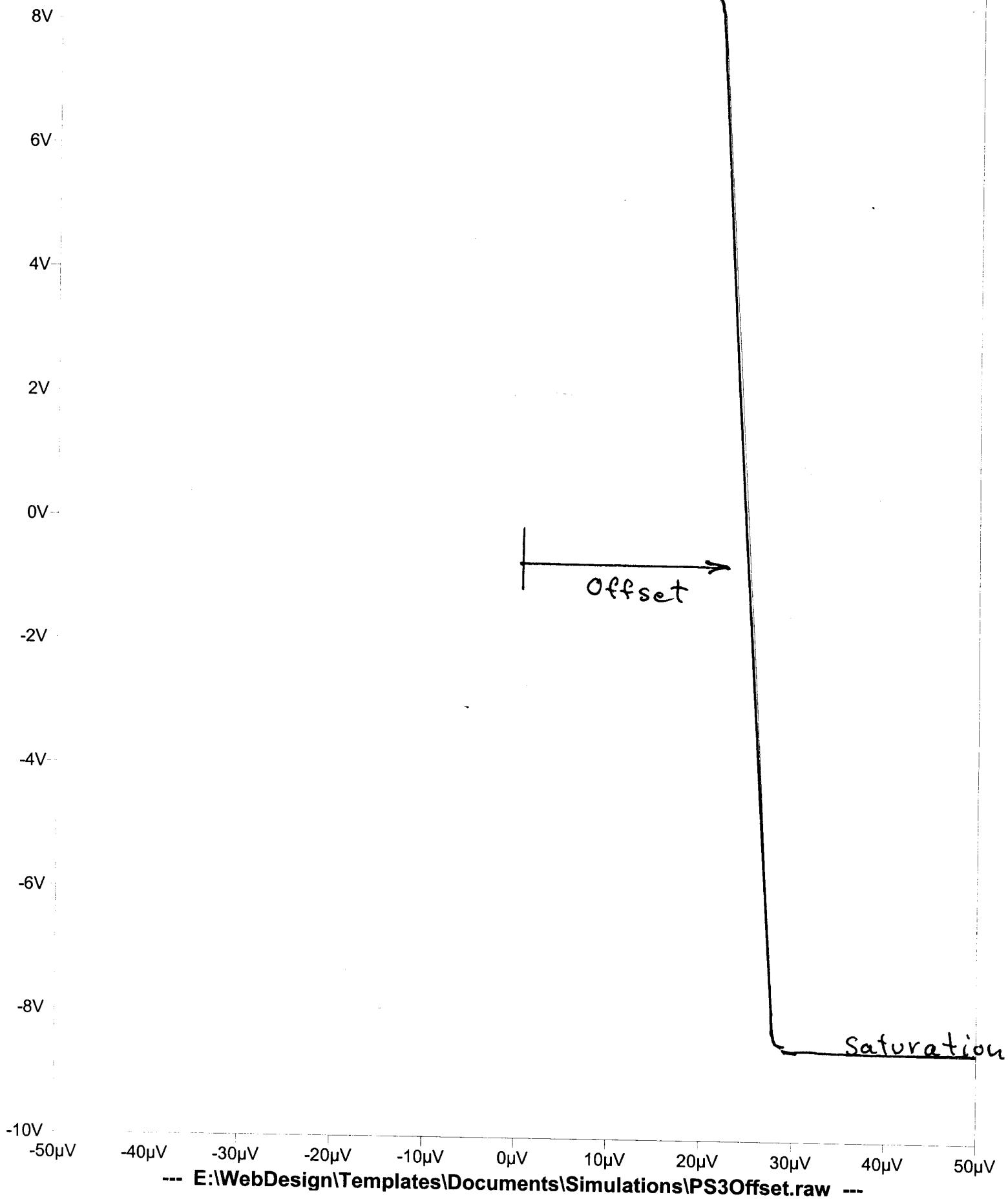

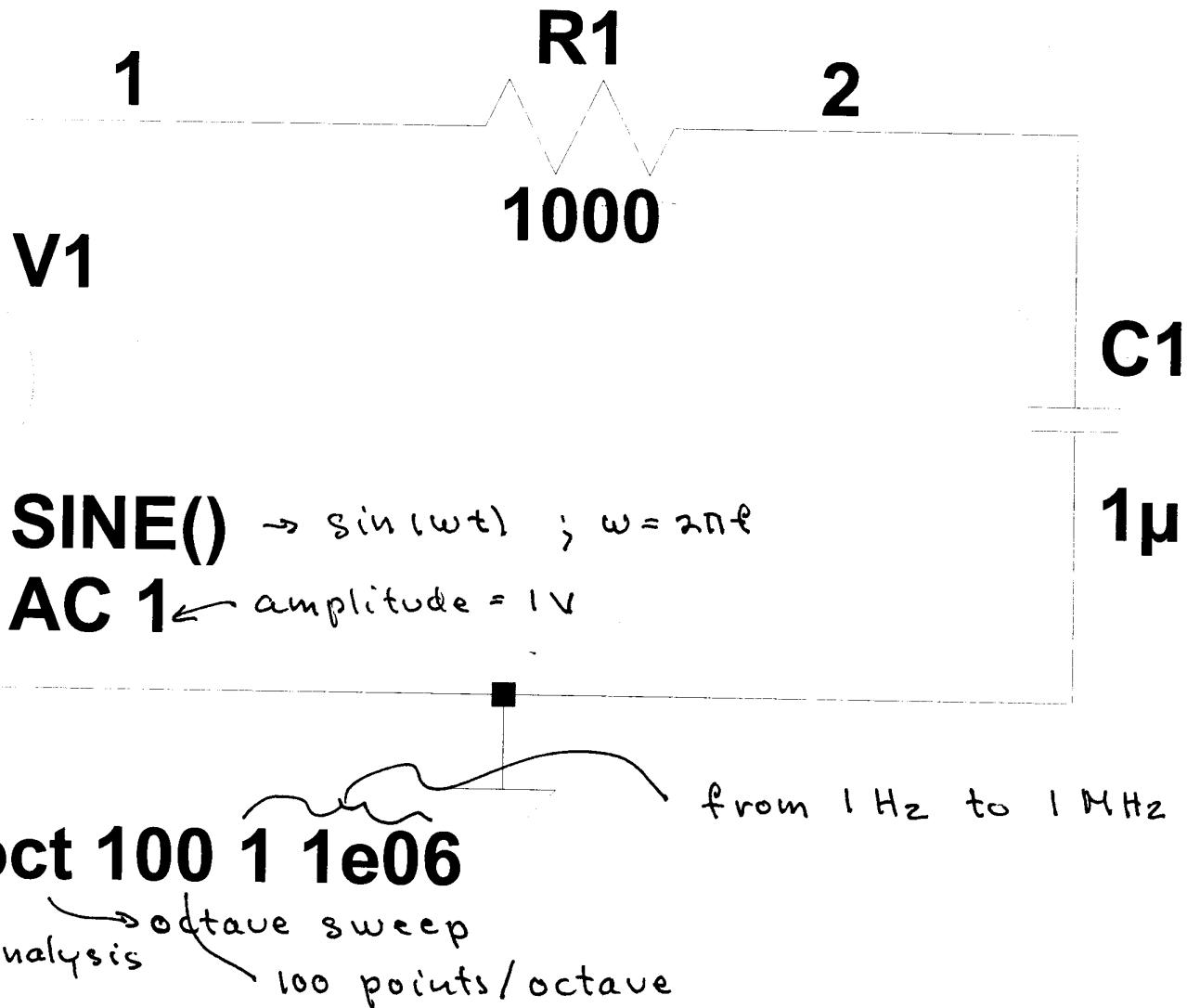Problem No 2 AC Analysis
AC Amplitude 1 volt
Octave Sweep from 1 to 10^6 Hz
No of points/octave 100
Stop frequency 10^6 Hz

Note Only asked to Plot Results., and compare
with $\tan^{-1} \omega RC$ and $1/\sqrt{1+(\omega RC)^2}$



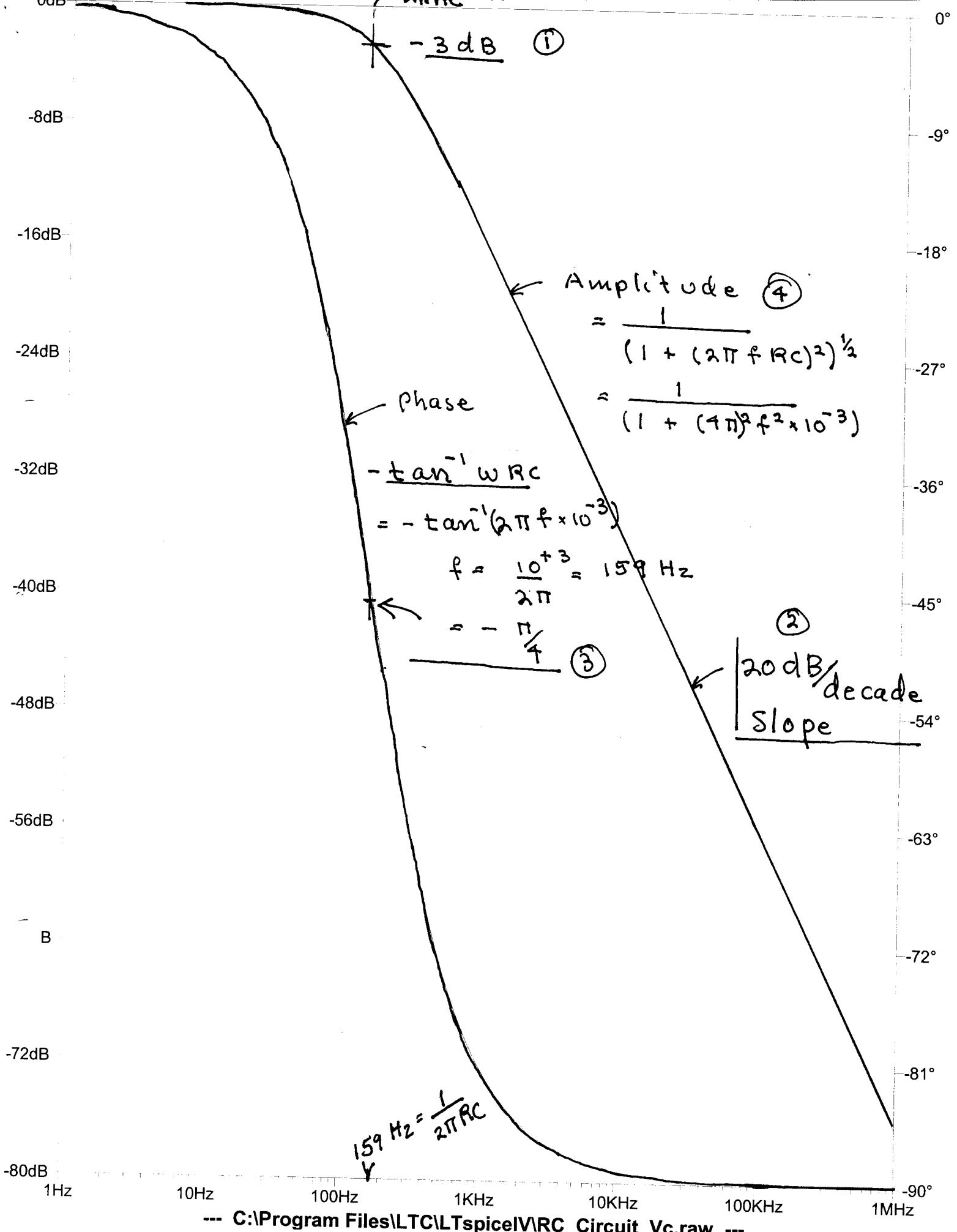

--- C:\Program Files\LTspice\RC_Circuit_Vc.raw ---

Note: On problem 14.32 Hambley states "since $\frac{v_o}{v_{in}}$ is independent of R_L the output R is ∞ . This is seen for Norton Equiv. If $i_{R_L} = I_{sc}$ for all R_L , then R_0 must be ∞

Problem 4 Problem 14.34 of Hambley

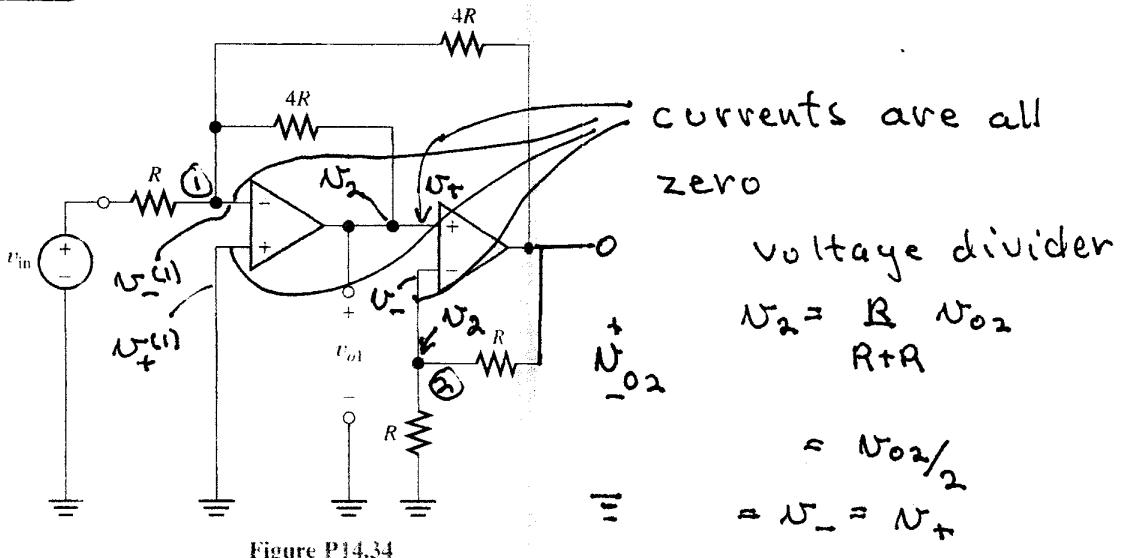


Figure P14.34

Consider Node Equation at ①

$$v_f^{(1)} + N_-^{(1)} = 0$$


$$\text{Thus } \frac{v_{in}}{R} + \frac{N_2}{4R} + \frac{N_{02}}{4R} = 0$$

$$\frac{v_{in}}{R} + \frac{N_{02} + 1}{2} \frac{N_{02}}{4R} + \frac{N_{02}}{4R} = 0$$

$$\therefore N_{02} = \frac{4}{3} v_{in}$$

$$N_{01} = N_2 = \frac{N_{02}}{2} = \frac{2}{3} v_{in}$$

Problem No 5)

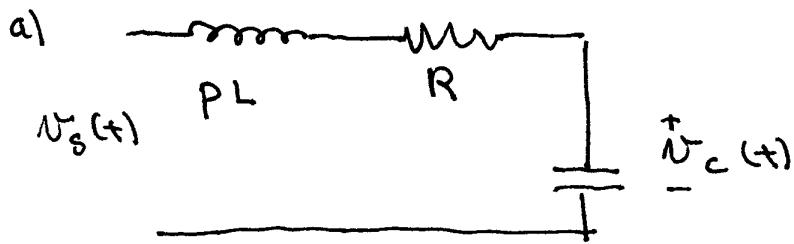

$$N_c(t) = \frac{\frac{1}{\rho C}}{\frac{1}{\rho C} + PL + R} N_s(t)$$


$$= \frac{1}{1 + \rho^2 LC + \rho CR} N_s(t)$$

DE $(1+LC \frac{d^2}{dt^2} + RC \frac{d}{dt}) N_c(t) = N_s(t)$


b) $N_c(t) = N_s(t)$ since $\rho \rightarrow 0$

c) $N_c(t) = 0$ since $\rho \rightarrow \infty$

An excitation with a sharp jump

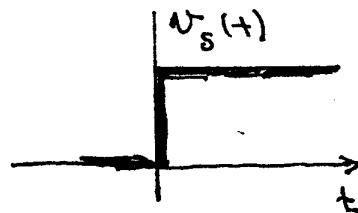

Problem No. 6

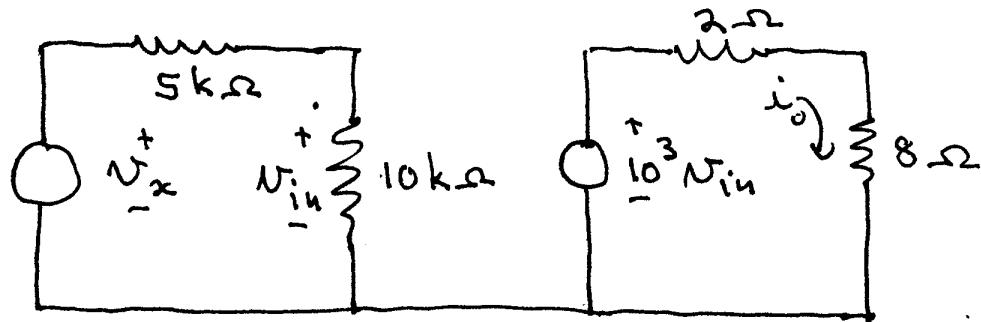

$$\text{Power delivered} = I_o^2 R_L = I_o^2 8 = 8$$

$$\therefore I_o = 1 \text{ Amp.}$$

$$\text{KVL} \quad I_o = \frac{10^3 N_{in}}{2+8} = \frac{10^3}{10} N_{in} = 1$$

$$\therefore N_{in} = 10^{-2} \text{ Volts.}$$

Voltage divider

$$N_{in} = \frac{10}{10+5} \times 15_{dc} = 10^{-2} \text{ Volts}$$

$$\therefore 15_{dc} = \frac{15}{10} \times 10^{-2} \text{ Volts}$$


$$= 15 \text{ mV.}$$

Problem No. 7

$$V_{oc} = 12.6 \text{ V}$$

supplies 100 Amp for a 0.1Ω resistance

Equivalent Circuit

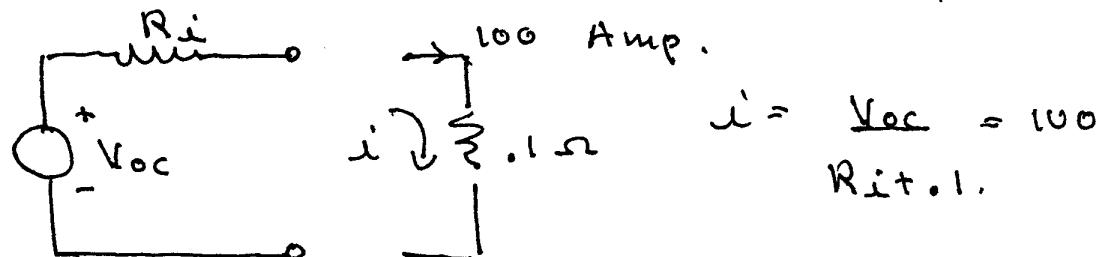


Thevenin
Equivalent

$$\therefore V_{oc} = 100 R_i + 10$$

$$R_i = \frac{2.6}{100} = .026 \Omega \quad (\text{Very Small!})$$

$$I_{sc} = \frac{V_{oc}}{R_i} = \frac{12.6}{.026} =$$

Norton Equivalent

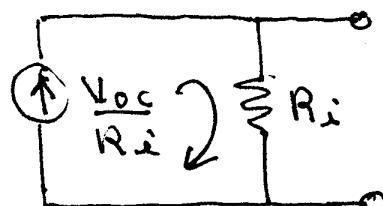

From the terminal point of view they are equivalent. However the book suggests that the Thevenin is more realistic because the Norton would imply dissipation in R_i by a circulating current!