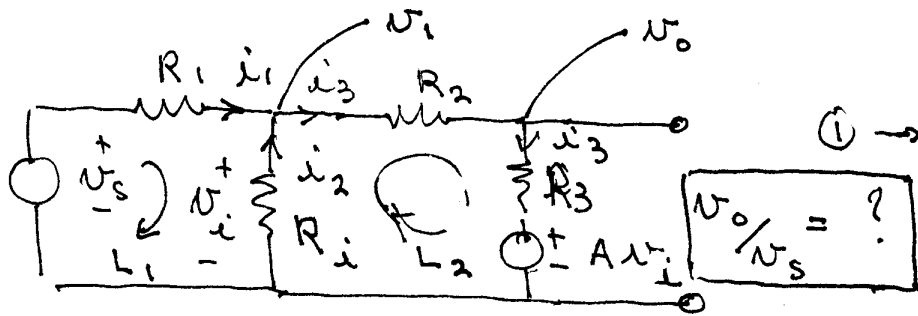


Example: 2-5 (Ulab4) → Can solve by KVL of course ①



KCL

$$\frac{V_1 - V_s}{R_1} + \frac{V_1}{R_i} + \frac{V_1 - V_o}{R_2} = 0$$

KVL solutions

② → $\frac{V_o - V_1}{R_2} + \frac{V_o - A i_1}{R_3} = 0$

③ → $V_i = V_1$

④ $V_s = R_1 i_1 - R_i i_2$ Loop 1 (L_1)

⑤ $R_i i_2 + R_2 i_3 + R_3 i_3 + A V_i = 0$ Loop 2 (L_2)


⑥ $V_o = A V_1 + R_3 i_3$ → constraint gives V_o only

Solve for i_1 , i_2 and i_3


But $i_3 = i_1 + i_2$; $V_i = R_i i_1$ → use these in ④ and ⑤ to obtain i_1 and i_2 . Then use ⑥ to obtain V_o

Input resistance with dependent sources.

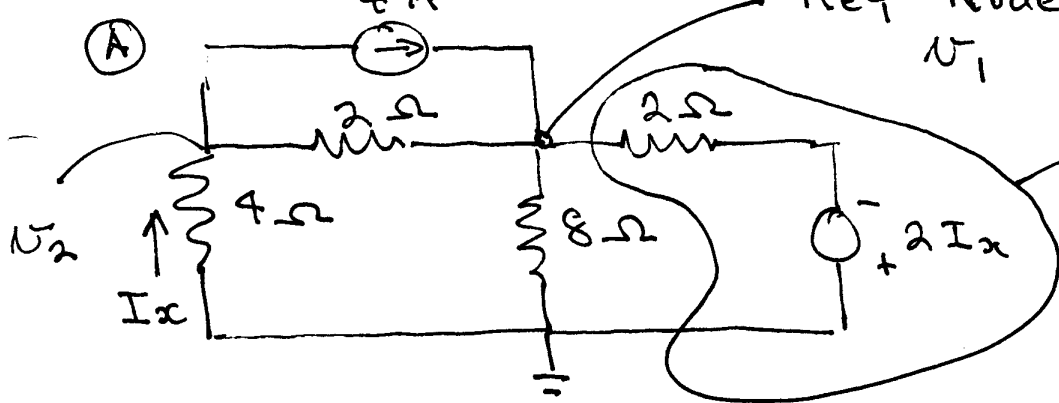Cannot just set dependent sources equal to zero because a change in voltage causes a change in these sources which changes the slope of $i-v$



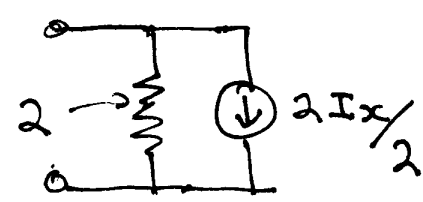Voltage Not Natural for KCL change to Norton



Note $I_x = -U_2/4$

KCL at ① $= U_2/4$

$$\frac{U_1}{8} + I_x + \frac{U_1}{2} - 4 + \frac{(U_1 - U_2)}{2} = 0$$

at ②

$$\frac{U_2}{4} + 4 + \frac{(U_2 - U_1)}{2} = 0 \Rightarrow \frac{3}{4} U_2 = \frac{U_1}{2} - 4$$

$$U_2 = \frac{2}{3} U_1 - \frac{16}{3}$$

$$U_1 \left(\frac{1}{8} + \frac{1}{2} + \frac{1}{2} \right) + \left(\frac{2}{3} U_1 - \frac{16}{3} \right) \left(-\frac{1}{4} - \frac{1}{2} \right) - 4 = 0$$


$$U_1 \left(\frac{9}{8} + \frac{2}{3} \left(-\frac{3}{4} \right) \right) + \frac{16}{3} \left(\frac{3}{4} \right) - 4 = 0$$

$$U_1 \left(\frac{9 - 4}{8} \right) + 4 - 4 = 0$$

$$U_1 \left(\frac{5}{8} \right) = 0 \quad U_1 = 0$$

$$\therefore U_2 = -\frac{16}{3} \quad \therefore I_x = -\frac{U_2}{4} = +\frac{4}{3}$$

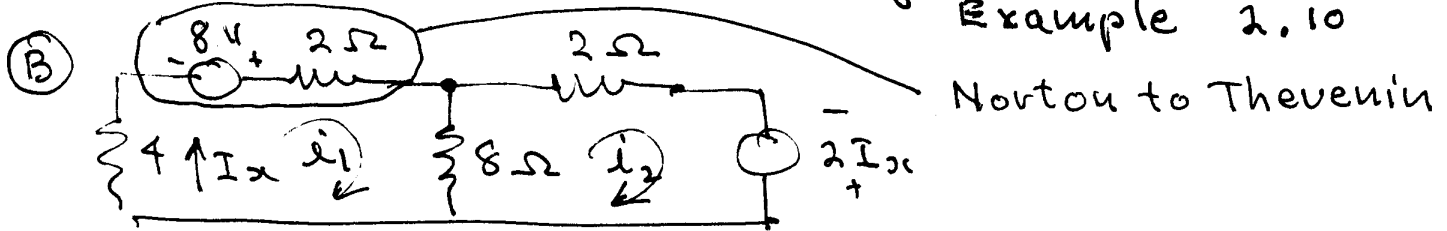Alternative Ways of Analyzing Ulabij + Maharbitz (3)
 Example 2.10



$8 = 2i_1 + 8(i_1 - i_2) + 4i_1$ (1) KVL


$2Ix = +8(i_2 - i_1) + 2i_2$ (2) KVL
 \uparrow
 i_1

From (2) $10i_1 = 10i_2 \rightarrow i_1 = i_2 \therefore V_1 = 0$


$8 = 2i_1 + 4i_1 \quad i_1 = 8/6 = 4/3 = -Ix$

$\therefore V_2 = -16/3 \quad \therefore Ix = +4/3 \text{ Amps}$

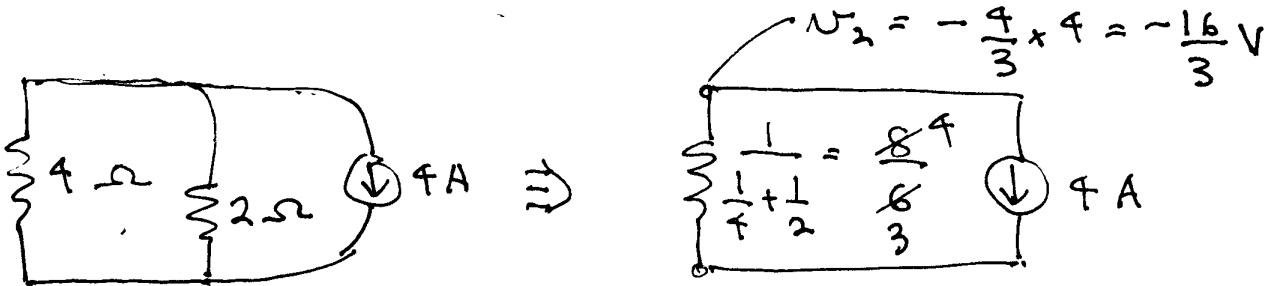(C) $V_1 = 0 \rightarrow$ This is a virtual short! (accidental)



Why does it work?

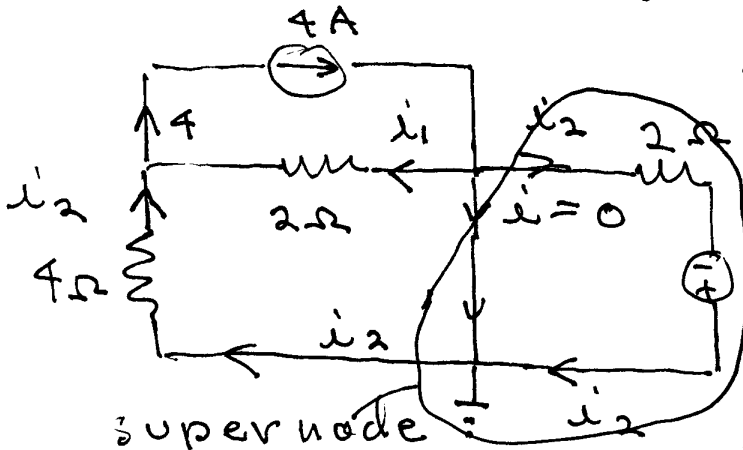

We must have
 $4 = i_1 + i_2$
 Since $i = 0$
 $2i_1 = 4i_2$
 $\therefore 4 = 3i_2 \quad i_2 = 4/3$
 $\therefore V_2 = -16/3 \text{ Volts.}$

Note on Coil \rightarrow Flux = (Magnetic Field (Wb/m^2)) Area $\text{\textcircled{4}}$


Faraday $N = \frac{d\text{Flux}}{dt}$ no of
Turns
 \downarrow
 $L \propto A \frac{N}{l}$

$$\text{Flux} = L i$$

$$N = L \frac{di}{dt} = (\rho L) i$$

Magnetic Permeability μ
Area A N turns


Note on Capacitor \Rightarrow

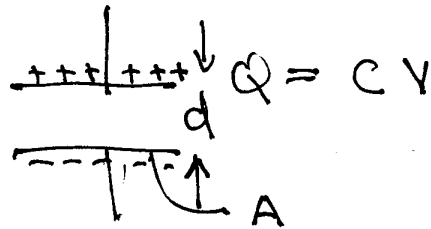

$$C \propto \frac{A}{d}$$

$$= \epsilon \frac{A}{d}$$

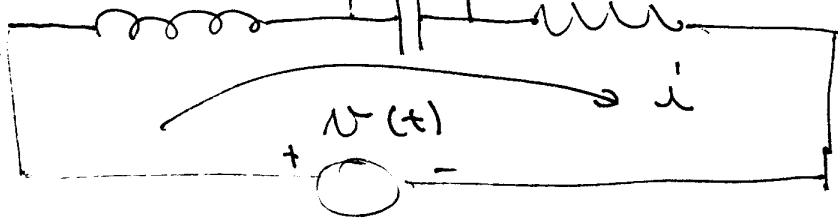Example Use N_c of $\frac{d}{dx} = p$ operator



$$i = \frac{1}{\rho L + \frac{1}{\rho C} + R} U(t)$$

$$N_c = \frac{L}{\rho C} i = \frac{\frac{1}{\rho C}}{\rho L + \frac{1}{\rho C} + R} U(t)$$

$$= \frac{1}{\rho^2 LC + 1 + \rho CR} U(t)$$

DE (Differential Equation)


$$(\rho^2 LC + 1 + \rho CR) N_c(t) = U(t)$$

$$\left(\frac{d^2}{dt^2} + \frac{R}{L} \frac{d}{dt} + \frac{1}{LC} \right) N_c(t) = \frac{U(t)}{LC}$$

Current Divider } Review
Voltage Divider }

(5)

Current Divider as an exercise

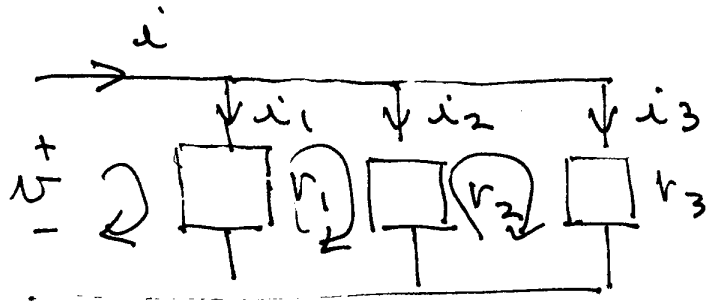

want to replace r_1, r_2, r_3 by equivalent resistor

$$\text{KCL } i = i_1 + i_2 + i_3$$

Branch Relations

$$i = \frac{U}{r_1} + \frac{U}{r_2} + \frac{U}{r_3}$$


KVL around 3 loops gives

$$U = U_1; \quad U_1 = U_2, \quad U_2 = U_3$$

$$\therefore i = U \left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right) = \frac{U}{r_{\text{equiv.}}}$$

$$\therefore \frac{1}{r_{\text{equiv}}} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}$$

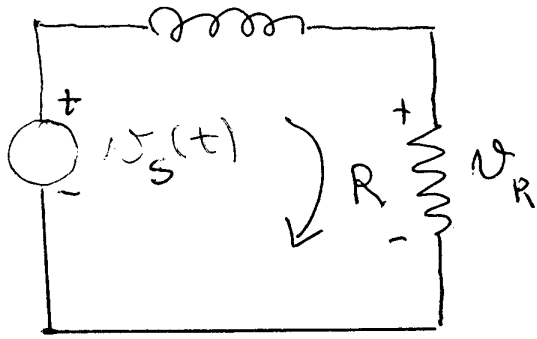L-R Circuit : Find the differential equation for $V_R(t)$ in terms of $V_S(t)$ (6)



$$\text{KVL } V_S(t) = (Lp) i + R i$$

$$\begin{aligned} V_R &= R i \\ &= \frac{R}{(R + pL)} V_S(t) \end{aligned}$$

$$(R + pL) V_R = R V_S(t)$$

$$\left(\frac{R}{L} + \frac{d}{dt} \right) V_R = V_S(t)$$

is the differential Equation
to solve