

UNIVERSITY OF CALIFORNIA  
College of Engineering  
Department of Electrical Engineering  
and Computer Sciences  
EECS 100/42  
Midterm Examination Fall 2009

T.K. Gustafson  
Oct 2 2009

PRINT YOUR NAME:

Answers

S.I.D. :

SIGNATURE:

Do your work on the exam.  
If you do need to use extra sheets  
attach these to the exam  
so that these are considered as well.


Make your methods clear so that partial credits is possible.

There are three problems  
THE PROBLEMS ARE EACH WORTH 12
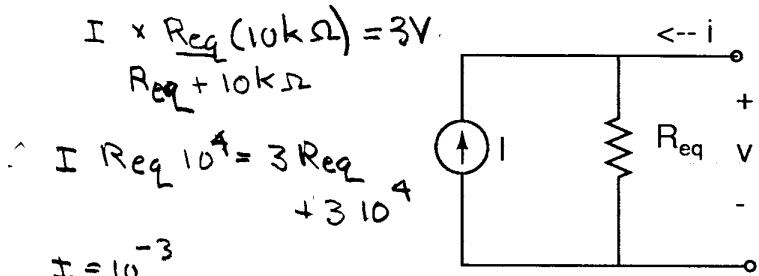
## Problem Number One ) (Total 12)

A power supply is observed to produce a current of 1 mA when the output is shorted. When connected to a 10 kΩ resistor the observed voltage across the resistor is 3 V.


2/12 a) What is the Norton equivalent of the supply? That is, give the values of  $I$  and  $R_{eq}$  in the following Figure.



$$I = \frac{1 \text{ mA}}{1}$$

$$R_{eq} = \frac{3}{7} \times 10^4 \Omega$$

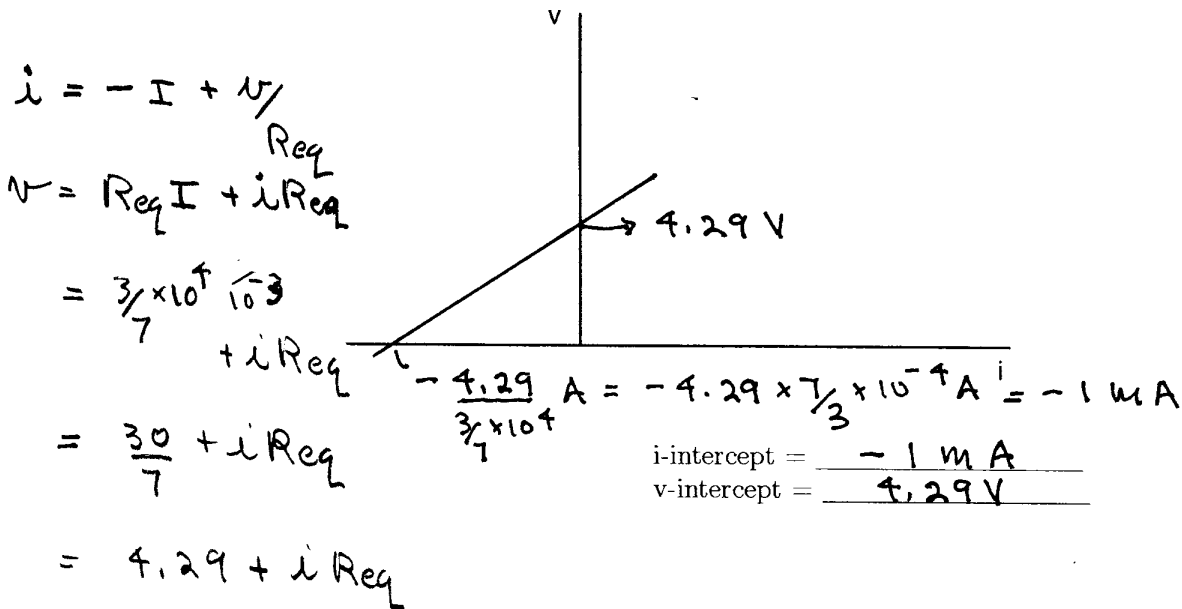2/12 b) Plot the straight line  $i$ - $v$  characteristic corresponding to the answer of part a). Give the numerical values of the  $i$  and  $v$  intercepts.




2/12 c) What open circuit voltage,  $V_{oc}$  would be measured?

$$V_{oc} = \frac{4.29 = \frac{30}{7} \text{ V}}{7}$$


Check

$$I \times R_{eq} \\ = 10^{-3} \times \frac{3}{7} \times 10^4 = \frac{30}{7} \text{ V}$$

2/12 d) Draw the Thevenin equivalent.

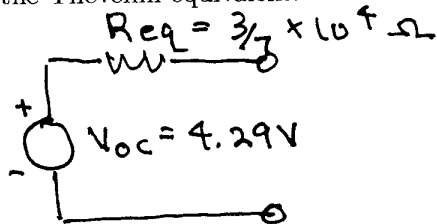

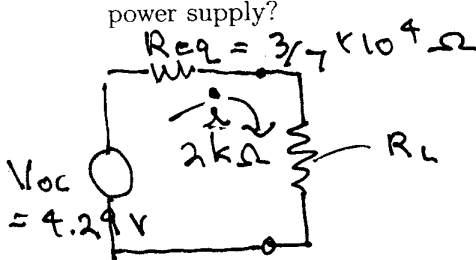2/12 e) How much power,  $P$ , would be dissipated in a  $R_L = 2k\Omega$  resistor connected to the power supply?



$$i = \frac{30/7}{\frac{3}{7} \times 10^4 + 2 \times 10^3} = \frac{30/7 \times 10^{-3}}{(30 + 14)/7} \\ = \frac{30 \times 10^{-3}}{44} = \frac{15}{22} \text{ mA} \\ i^2 R_L = \left(\frac{15}{22}\right)^2 \times 2 \times 10^3 \times (10^{-3})^2 = \frac{225}{484} \times 2 \text{ mW} \\ = 225/242 \\ P = .93 \text{ MWatts}$$

2/12 f) Is it possible to state how much power the supply dissipates when no load is connected to it? If yes, state its value.


Possible? Yes or No No in general

If answer is yes  $P_{Diss} =$  \_\_\_\_\_

If answer is no state why Dissipation Depends

Upon internal configuration of the power supply elements  
If Thev or Norton represents the actual configuration then this would give diss but in general. No.

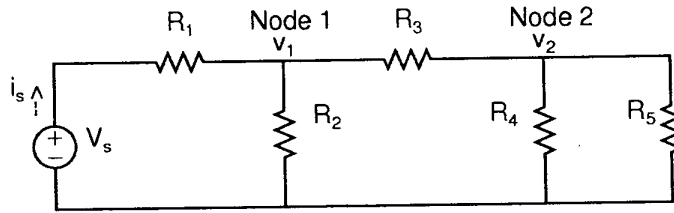Problem Number Two ) (Total 12)  
For the circuit shown below:



2/12 a) What is the node equation at node 1 in terms of  $v_1$  and  $v_2$  (and  $v_s$ ) and the resistors?

$$\text{Node Eq 1 } \frac{v_1 - v_s}{R_1} + \frac{v_1}{R_2} + \frac{v_1 - v_2}{R_3} = 0$$

2/12 b) Similarly what is the node equation at node 2 in terms of  $v_1$  and  $v_2$  (and  $v_s$ ) and the resistors?

$$\text{Node Eq 2 } \frac{v_2 - v_1}{R_3} + v_2 \left( \frac{1}{R_4} + \frac{1}{R_5} \right) = 0$$

3/12 c) The combined resistance of  $R_2$  to  $R_5$  between node 1 and ground,  $R_c$  can be expressed as follows:

$$\frac{1}{R_c} = \frac{1}{\frac{1}{A+B} + C} + \frac{1}{D} \quad (1)$$

Specify A to D in terms of  $R_1$  to  $R_5$ .

For  $R_4$  and  $R_5$

$$\frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{R_{eq}}$$

$R_3$  in series so including that

$$R_3 + \frac{1}{\frac{1}{R_4} + \frac{1}{R_5}} ; R_2 \text{ is in parallel with this}$$

$$\frac{1}{R_c} = \frac{1}{R_2} + \frac{1}{R_3 + \frac{1}{\frac{1}{R_4} + \frac{1}{R_5}}}$$

$$\begin{aligned} A &= R_4 \text{ or } R_5 \\ B &= R_5 \text{ or } R_4 \\ C &= R_3 \\ D &= R_2 \end{aligned}$$

3/12 d) For  $V_s = 3V$ ,  $R_1 = R_2 = 2\Omega$ ,  $R_3 = 1\Omega$ ,  $R_4 = R_5 = 2\Omega$ , what is the voltage  $v_2$  and the source current  $i_s$ .

$$\frac{1}{R_c} = \frac{1}{2} + \frac{1}{1 + \frac{1}{\frac{1}{2} + \frac{1}{2}}} = \frac{1}{2} + \frac{1}{1 + 1} = 1$$

$$\therefore V_1 = \frac{1}{1 + 2} \times 3V = 1V \text{ - Voltage Divider}$$

$$\frac{1}{R_4} + \frac{1}{R_5} = 1 \Omega^{-1} \quad R_3 = 1\Omega$$

$$\therefore V_2 = \frac{1}{2} V$$

$$R_c = 1\Omega \quad \therefore i_s = \frac{3}{R_1 + R_c} = 1 \text{ Amp}$$

$$\begin{aligned} v_2 &= \frac{1/2 V}{1 \text{ Amp}} \\ i_s &= \frac{3}{1 + 1} \end{aligned}$$


2/12 e) Give an expression for the fraction of the source power delivered to  $R_5$  in terms of  $v_2$ ,  $R_5$ ,  $v_1$ ,  $V_s$ , and  $R_1$

$$\text{Fraction of Power Delivered} = \frac{(v_2/R_5)^2 R_5}{\left(\frac{V_s - v_1}{R_1}\right) V_s}$$

$$\text{fraction} = \frac{v_2^2 / R_5}{\left(\frac{V_s - v_1}{R_1}\right) V_s}$$

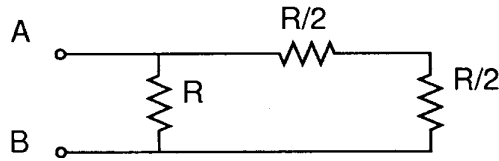
Problem Number Three) (Total 12)

What is the equivalent resistance between the terminals A and B (or resistance operator in terms of  $p = \frac{d}{dx}$ ) between the terminals for the following circuit elements and combinations?  
3/12 a)




$$R \parallel (R/2 + R/2) = R \parallel R = R/2$$

$$r(p) = \underline{R/2}$$

 



3/12 b)

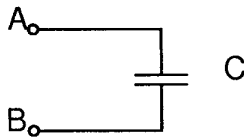

$$r(p) = \underline{\frac{1}{pc}}$$

$$p = \frac{d}{dt}$$

3/12

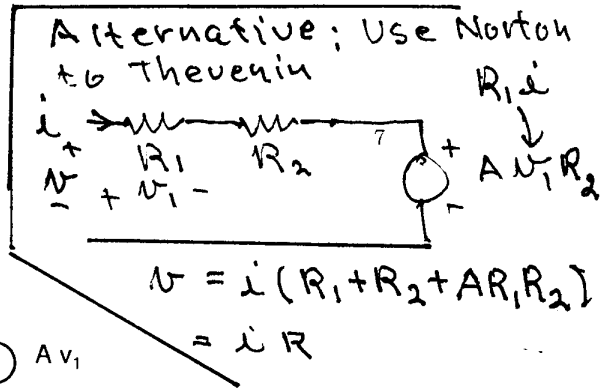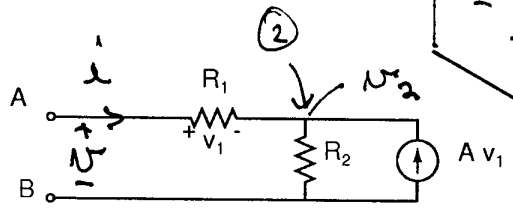

excite with  $U \rightarrow$  calculate  $i$

$$i = \frac{U - U_2}{R_1} = \frac{U_1}{R_1} \quad \text{since } U - U_2 = U_1 \quad \text{or } U_2 = U - U_1$$


Node ②  $\frac{U_2}{R_2} - A U_1 - i = 0$

$$\frac{U - U_1}{R_2} - A U_1 - i = 0$$

$$\frac{U - R_1 i}{R_2} - A R_1 i - i = 0 \quad r^{(p)} = R_1 + R_2 + A R_1 R_2$$

$$\therefore U = (R_1(1 + A R_2) + R_2) i$$

3/12

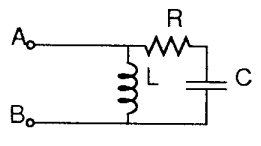

$$PL \parallel (R + \frac{1}{pc})$$

$$= \frac{PL(R + \frac{1}{pc})}{PL + R + \frac{1}{pc}}$$

$$r^{(p)} = \frac{1}{\frac{1}{PL} + \frac{1}{\frac{1}{pc} + R}}$$