

5.1 - 3.6

Chapter 4 - All

Chapter 5 - RMS Value

page 203

$$v(t) = V_m \cos(\omega t + \theta)$$

$$(RMS)^2 = \frac{1}{T} \int_0^T v^2(t) dt = \frac{2}{T} \int_0^{T/2} v^2(t) dt$$


can do as in book or!

$$v(t) = \frac{V_m}{2} e^{i(\omega t + \theta)} + c.c.$$

$$v^2(t) = 2 \times \frac{V_m^2}{4} + \frac{V_m^2}{4} \underbrace{(e^{2i(\omega t + \theta)} + c.c.)}_{2 \cos(2\omega t + 2\theta)}$$

Thus $RMS = \left(\int_0^{T/2} v^2(t) dt \frac{2}{T} \right)^{1/2} = \frac{V_m}{\sqrt{2}}$
 only contribution (periodic in $\frac{T}{2} = \frac{\pi}{\omega}$ and area of positive value = area of negative value so $\int_0^{T/2} (\cdot) dt = 0$)

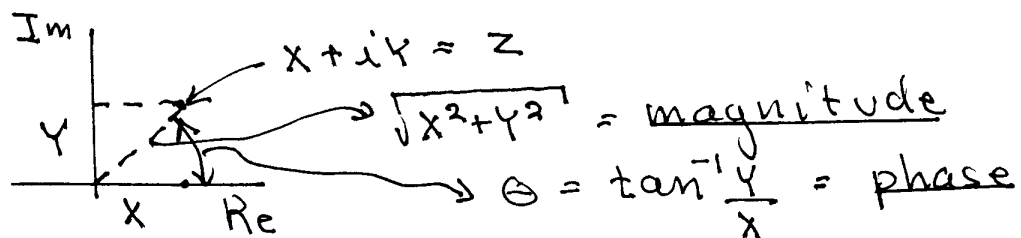5.2 Phasor - Simply complex amplitude multiplying $e^{i\omega t}$. Review rectangular and polar plot of a complex number




To find function represented by phasor Z

$$\begin{aligned} z(t) &= \text{Re}(Z e^{i\omega t}) \quad \text{don't forget this!} \\ &= \text{Re}(Z) \cos \omega t - \text{Im}(Z) \sin \omega t \\ &= \sqrt{x^2 + y^2} \cos(\omega t + \theta) \end{aligned}$$

$$Z(\omega) \triangleq r(p) \Big|_{p=j\omega}$$

Example

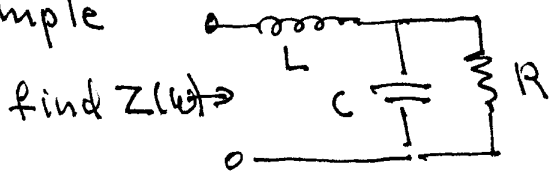

Solution

$$\begin{aligned} r(p) &= pL + \frac{1}{pC} \parallel R \\ &= pL + \frac{\frac{1}{pC} R}{R + \frac{1}{pC}} \end{aligned}$$

$$\text{So } Z(\omega) = j\omega L + \frac{R}{1 + j\omega RC}$$

Section 5.4 : Once again just find $r(p)$ and substitute $p=j\omega$. The rest is complex arithmetic

5.5 Power. - just as for any $v(t) i(t)$ this gives instantaneous power. For sinusoids (periodic) we like to use time averaged power. (Your house meter measures this). The other terms average to zero. Example $v(t) = V \cos \omega t$ and $i(t) = I \cos \omega t$ $v(t) i(t) = VI \cos^2 \omega t = \frac{VI}{2} (1 + \underbrace{\cos 2\omega t})$ Average
 thus time Average power = $(\frac{VI}{2})$.
 The instantaneous power oscillates between this $(\frac{VI}{2})$ and twice this (VI) [Also $\frac{VI}{2} = V_{RMS} i_{RMS}$]

Power Factor : If $v(t) = \text{Re}(V e^{j\theta} e^{j\omega t})$
 $i(t) = \text{Re}(I e^{j\phi} e^{j\omega t})$

$$v(t) i(t) \Big|_{\text{time Avg}} = \frac{VI}{4} \underbrace{e^{j(\theta-\phi)} + \text{cc.}}_{\text{these are the only terms not involving } e^{2j\omega t}} = \frac{VI}{2} \underbrace{\cos(\theta-\phi)}_{\text{power factor}}$$

Note real time Avg Power = $V I e^{j(\theta-\delta)} + c.c.$ (3)

$$= \underbrace{\frac{VI \cos(\theta-\delta)}{4}}_{P/2} + \underbrace{j \frac{VI \sin(\theta-\delta)}{4}}_{\text{cancel}} + \underbrace{\frac{VI \cos(\theta-\delta)}{4}}_{\text{cancel}} - \underbrace{j \frac{VI \sin(\theta-\delta)}{4}}_{\text{cancel}}$$

$\frac{VI \sin(\theta-\delta)}{2} = \text{Reactive Power} = Q$ by definition

The reactive power cancels from $v(t) i(t)$ because $v(t) i(t)$ is real. Real Power = $\frac{VI}{2} \cos(\theta-\delta)$

page 229-230 Apparent Power = $\frac{VI}{2}$
 Note for L & C Since $\theta-\delta = \pm \pi/2$ the power is reactive. Do it this way for sines and cosines Define

$v(t) = \frac{V e^{j\omega t}}{2} + c.c.$ $\frac{I(\omega)}{2}$ Complex Power
 $P_c = 2 \left(\frac{V e^{j\omega t}}{2} \right) \left(\frac{I e^{j\omega t}}{2} \right)^* = P + jQ$

for C; $(I e^{j\omega t}) = C \frac{d}{dt} (V e^{j\omega t}) = (C j\omega V) e^{j\omega t}$

Thus $P_c = V e^{j\omega t} (-j\omega) C V \frac{1}{2} e^{-j\omega t}$

$= -j \frac{V V^* \omega C}{2} = jQ$
 Real

Note By defining Complex power we can discuss L and C. Reactive power just relates to the energy stored.

Also we see that $P_c = \underbrace{P}_{\text{Real power}} + jQ$

Forget examples 5.8 and 5.9 but 5.9 is interesting!

Do. 5.6 just use $\text{rcp} |_{p=j\omega}$ once again (4)

Forget 5.7, - interesting though (and practical)

Chapter 6 Look at 6.4 - You did this with
RC and LTSpice $f_B = \frac{1}{RC}$

Forget 6.5

6.6 to 6.8 → Read

6.9 DSP is interesting - ignore for exam

Chaps 7-9 - Will cover portions after midterm

Chapt 10 10.1-10.6 (Ideal Diode)

Chapt 11 : This is basically Analysis with
Dependent Sources. Neglect 11.6 to end
of Chapter. Concentrate on the assigned
home work problem from this chapter

Chapt 12 FETS. (Not on Midterm)

12.1 - 12.3

Read 12.7

Chapt 13 (Not on midterm)

13.1 - 13.5

Chapt 14 (Op Amps)

14.1 - 14.4

14.8, 14.9

Problem Sets 3 and 4