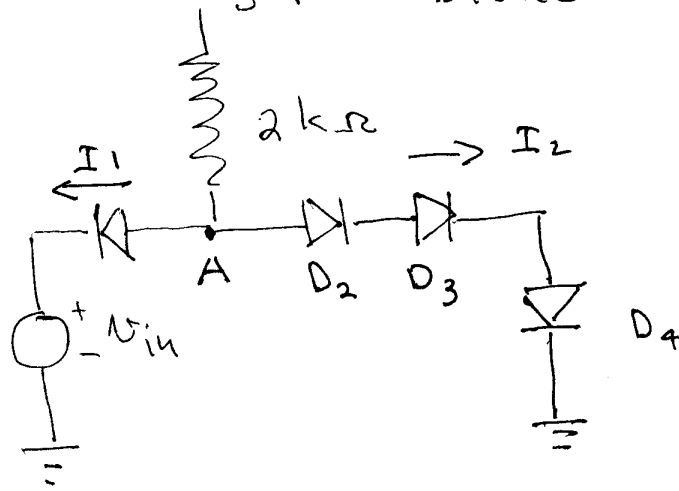


Example 1


5 V Diode Problem

(1)




$$V_{in} = 0 - 5V$$

$$V_D = .7V$$

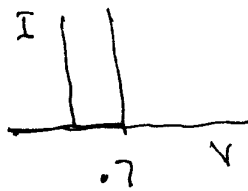


Break points

- $V_{in} = 4.3V$ then $V_A = 5V$ if D_1 is on
- But then D_2, D_3, D_4 are then on $V_A = 2.1V$.
contradiction. Thus D_1 is off
- $V_{in} = 2.1 - .7 = 1.4V$ is a break point
- $V_{in} = 1.4V$ All diodes are on
- $I_1 = I_2 = \frac{1}{2} \frac{5 - 1.4}{2k\Omega}$ at $V_{in} = 1.4$
- $V_{in} < 1.4V$ $V_A < 2.1V$ D_2, D_3, D_4
off only D_1 on $I_2 = 0$ $I_1 = \frac{5 - (V_{in} + .7)}{2k}$
- $V_{in} > 1.4$ D_1 is off D_1, D_2, D_3
on

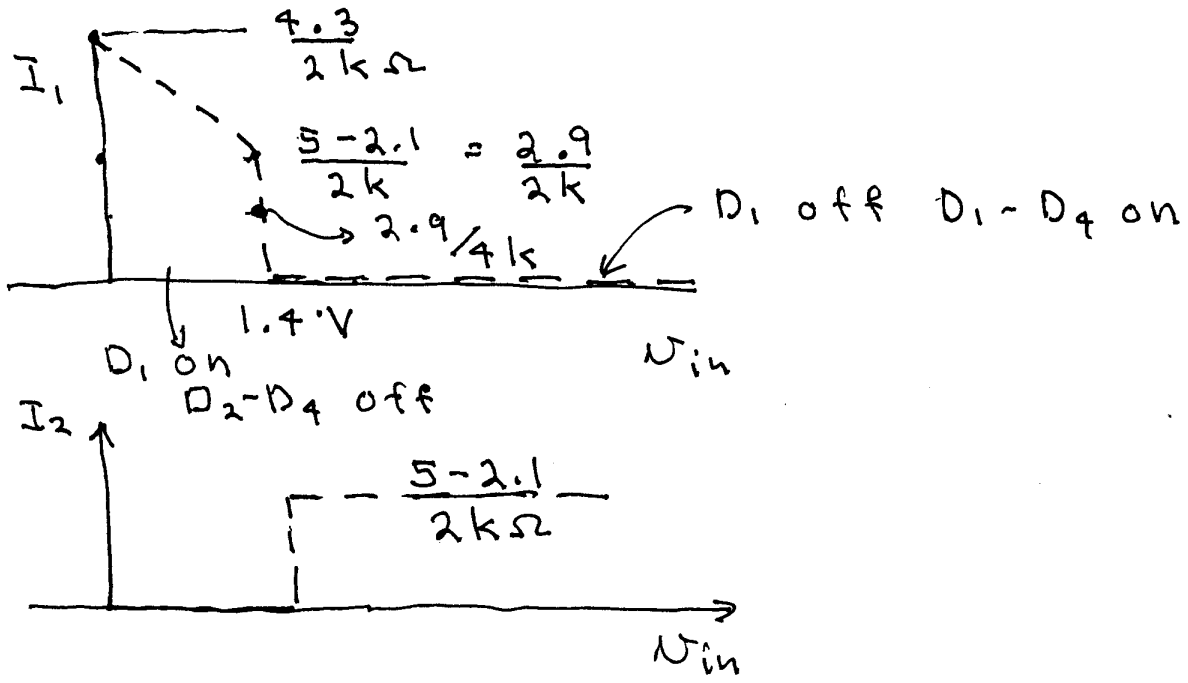

Example 2 , Diode Problem

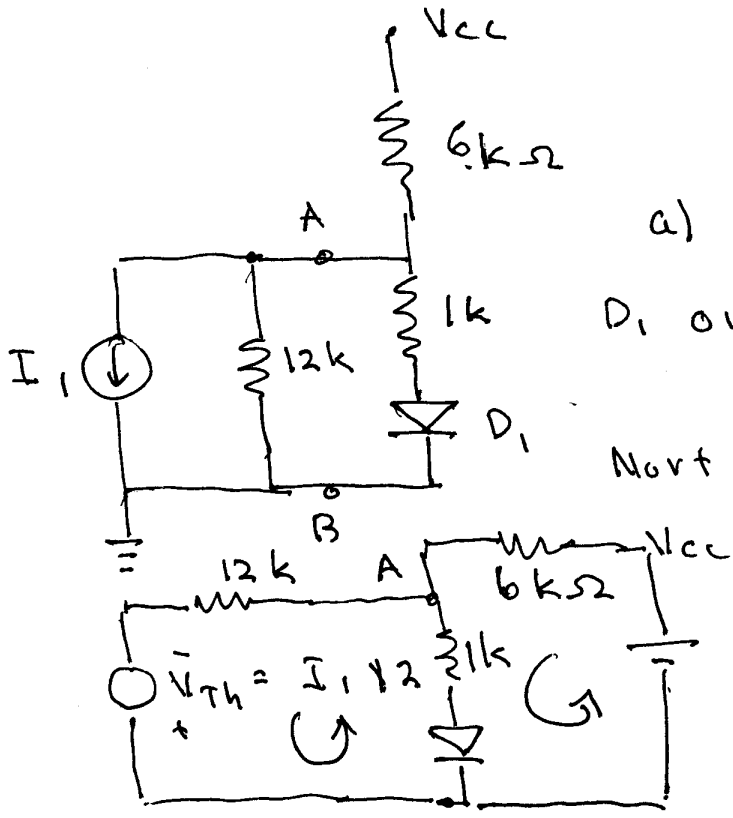

a) $V_{cc} = 12V$ $I_1 = 1.25 mA$

D_1 on.

Nort. to Thev.

or Thev. to Norton

KCL


$$V_A \left(\frac{1}{6} + \frac{1}{12} \right)$$

$$+ \frac{V_A - 0.7}{1k} + I_1 - \frac{V_{cc}}{6k} = 0$$

$$V_A \left(\frac{1}{6} + \frac{1}{12} + 1 \right)$$

$$= \frac{0.7}{1} - I_1 + \frac{V_{cc}}{6}$$

Is this positive

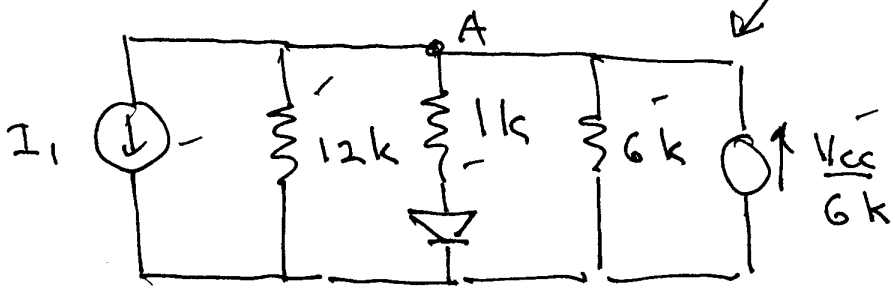

a) $\frac{V_{CC}}{6} = 2 \text{ mA} > I_1 (1.25 \text{ mA})$ so diode is on (3)

$$V_A = \frac{.7 - 1.25 + 2}{\left(\frac{4}{5}\right)} = (2.7 - 1.25) \times \frac{4}{5}$$

$$= \frac{1.45}{5} \times 4 = .29 \times 4 = \underline{1.16 \text{ V}}$$

$\therefore I_D = (1.16 - .7) / 1 \text{ mA} = .46 \text{ mA}$

b) $V_{CC} = -6 \quad I_1 = -1.25$ diode on

$$V_A = (.7 + 1.25 - 1) \times \frac{4}{5} = .95 \times \frac{4}{5} = .76$$


Note Condition for Diode to be on: $I_D = .04 \text{ mA}$

$$V_A = (.7 - I_1 + \frac{V_{CC}}{6}) / \left(\frac{5}{4}\right)$$

$$I_D = (V_A - .7) / 1 = \left(4 \left(\frac{.7 - I_1 + \frac{V_{CC}}{6}}{5}\right) - .7\right) / 5 > 0$$

$$= \frac{4}{5} \left(-I_1 + \frac{V_{CC}}{6}\right) > 0$$

3) Diode Gate

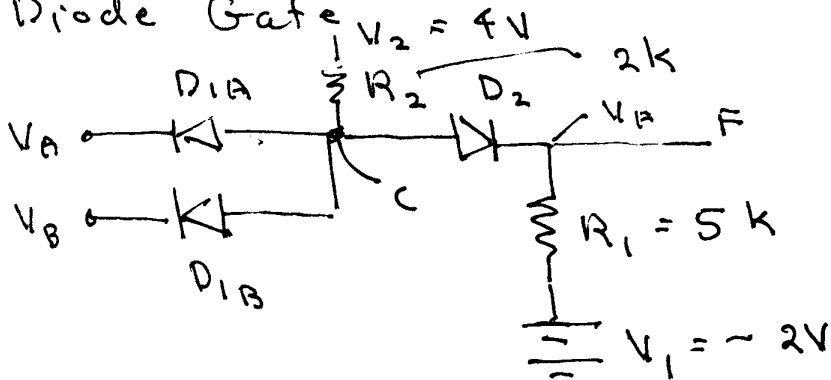

$$V_2 + V_1 > 0$$

$$F = 2.9$$

And Gate

Determine V_F for

a) $V_A = .2 \text{ V} \quad V_B = .2 \text{ V}$

$D_{1A}, D_{1B} = \text{on} \quad V_C = .9 \text{ V} \quad D_2 \text{ off}$


$$V_F = -2 \text{ V}$$

b) $V_A = 4 = V_B = 4 \text{ V} \quad D_{1A}, D_{2A} = \text{off}$

$$I_{D_2} = (6 - .7) / 7; \quad V_F = -2 + 5 \times 5.3 / 7 = 1.8 \text{ V}$$

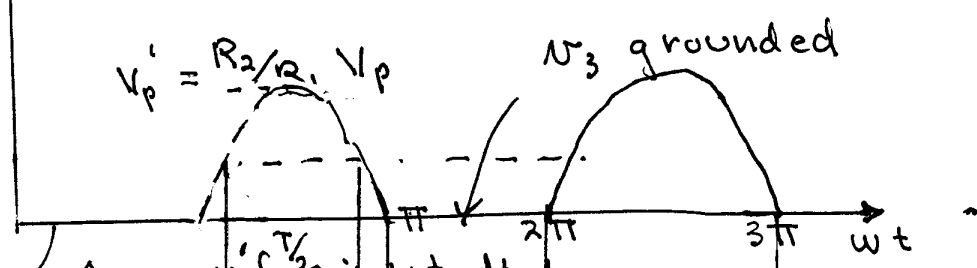Problem Set 5/

$V_1(t)$ (output after second diode) (before filter)




Diodes on
so V_3 is
grounded

$$\text{Avg} = \frac{1}{T} \int_0^T V_p' \sin \omega t \, dt$$

$$= \frac{V_p'}{\omega T} \int_0^{\pi} \sin \alpha \, d\alpha = V_p' \frac{2}{\omega T} = \frac{V_p'}{\pi}$$

$V_2(t)$ (output after RC filtering)

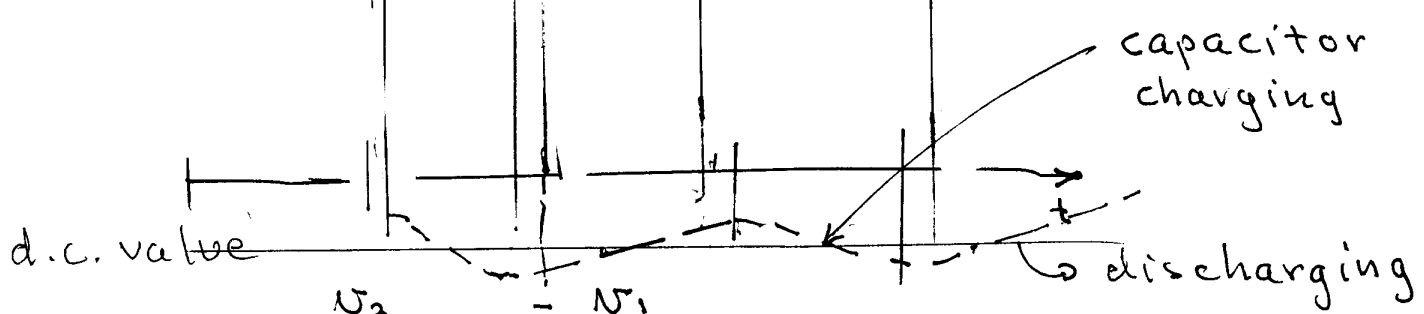

$$\frac{V_2}{\frac{1}{\omega C} \parallel R_4} = - \frac{V_1}{R_3}$$

$$\therefore V_2 = - \frac{R_4}{1 + R_4 \omega C} \frac{V_1}{R_3} \quad R_4 C \text{ is large}$$

Governing D.E.

$$(1 + R_4 \omega C) V_2 = - \frac{R_4}{R_3} V_1$$

$$\left(\frac{1}{R_4 C} + \frac{d}{dt} \right) V_2 = - \frac{1}{R_3 C} V_1$$

$$\frac{d}{dt} (V_2 e^{t/R_4 C}) = - \frac{1}{R_3 C} e^{t/R_4 C}$$


Consider signal $V_1(t)$ above

The average of the signal $V_1(t)$

$$= V_p \int_0^{T/2} \sin \omega t \, dt \times \frac{1}{T} \times \frac{R_2}{R_1} = V_p \frac{R_2}{R_1} \times \frac{1}{T} \times \frac{T}{2} = V_p \frac{R_2}{R_1} \times \frac{1}{2}$$

This is the d.c. component.
which gets filtered out

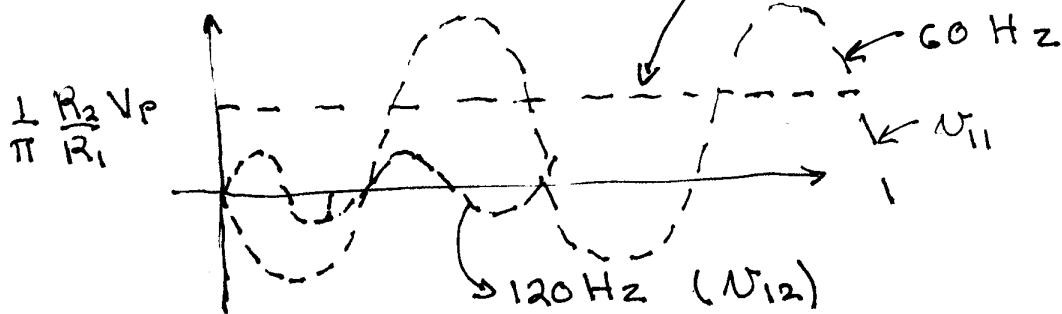model $V_1(t)$ as $V_{10} + V_{11} + V_{12} + \dots$



Now look at V_2 for each of these
 $p=0$ for d.c.

$$V_{20} = -\frac{R_4}{R_3} V_{10} = -\frac{R_4}{R_3} \frac{R_2}{R_1} \times \frac{1}{2}$$

$$V_{21} = -\frac{R_4}{1 + R_4 j\omega C} \frac{V_{11}}{R_3} \quad \text{for } 60 \text{ Hz} \quad \omega = 2\pi \times 60$$

$$\approx -\frac{1}{j\omega C} \frac{V_{11}}{R_3} = -\frac{R_4}{R_3 R_1} \frac{1}{j(\omega C R_4)}$$

$$\omega C R_4 \gg \pi$$

Thus V_{21} is small. (example $1 \text{ k}\Omega \times 50 \mu\text{F}$
 $\times 60 \text{ Hz}$) = $50 \times 10^{-3} \times 2\pi \times 60 = 6\pi$

And output is close to a constant V_{20}

$$= -\frac{R_4}{R_3} \frac{R_2}{R_1} \times \frac{1}{2}$$