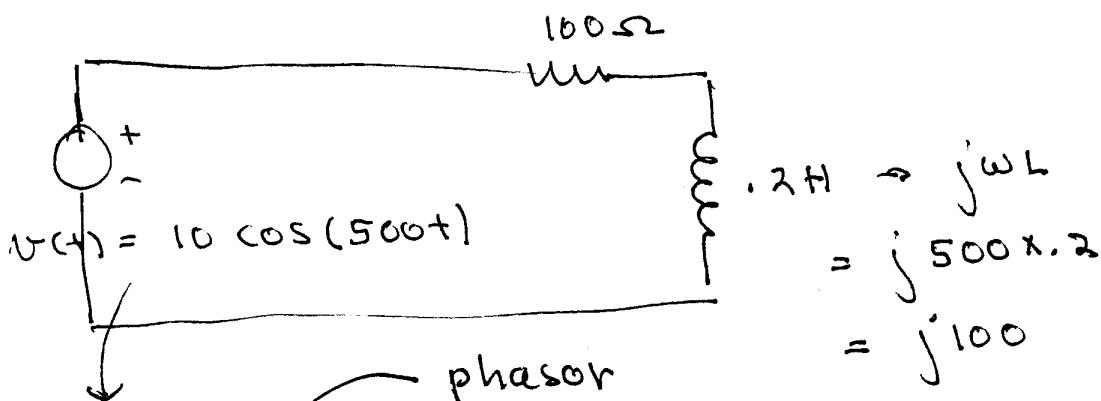


(1)


Problem 5.41 -



write

$$V(t) = 10 e^{\frac{j500t}{2}} + \text{c.c.}$$

↑
find response

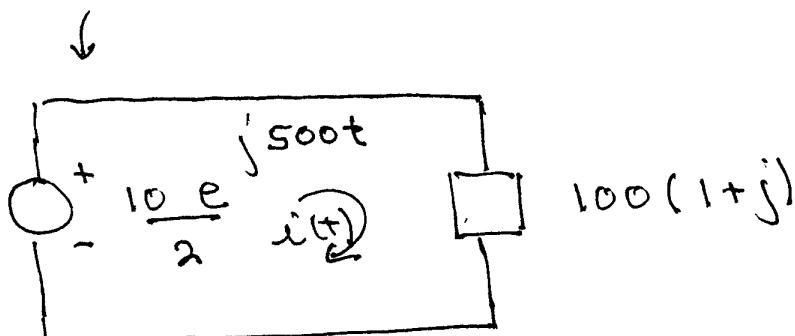

$$i(t) = 2 \operatorname{Re} \frac{10 e^{j500t}}{2} / (100(1+j))$$

$$= 2 \operatorname{Re} \frac{10}{2} e^{j500t} / (100\sqrt{2} e^{j\tan^{-1} 1})$$

$$= 2 \operatorname{Re} \left[\frac{10}{2} \times \frac{1}{100} \times \frac{1}{\sqrt{2}} e^{j500t} e^{-j\frac{\pi}{4}} \right]$$

phasor voltage
(everything but the 2's (since they cancel and the $e^{j\omega t} = e^{j500t}$)

$$i(t) = \frac{1}{10\sqrt{2}} \cos(500t - \frac{\pi}{4})$$

This is the Steady-State Response

phasor current

$$\frac{10}{100} \times \frac{1}{\sqrt{2}} e^{-j\frac{\pi}{4}}$$

$$V_L(t) = L \frac{di}{dt}$$

$$= L \left(\frac{d}{dt} \text{Re} \frac{1}{10\sqrt{2}} e^{j500t} e^{-j\frac{\pi}{4}} \right)$$


$$= \text{Re} \left(500 e^{j500t} e^{-j\frac{\pi}{4}} \frac{L}{10\sqrt{2}} \right)$$

$\frac{d}{dt}$ gives

this

$$= \text{Re} \left(\frac{500L}{10\sqrt{2}} e^{-j\frac{\pi}{4}} e^{+j\frac{\pi}{2}} \right) e^{j500t}$$
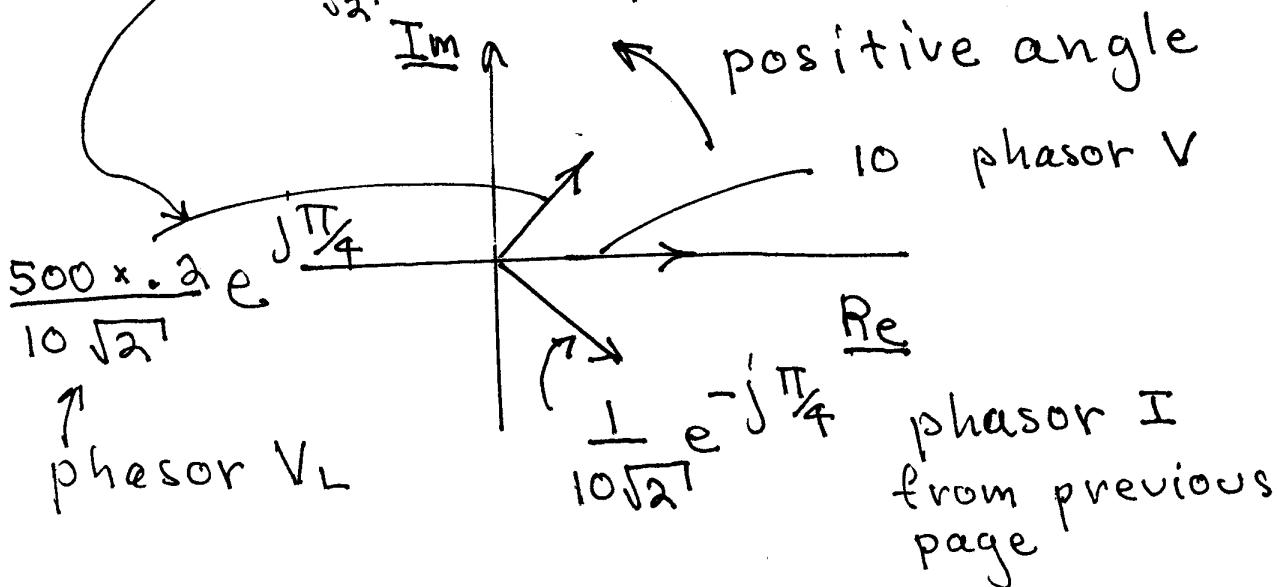
$$V_L(t) = \frac{10}{\sqrt{2}} \cos(+\frac{\pi}{4} + 500t)$$



Note that $i(0) \neq 0$. $i(0) = \frac{1}{10\sqrt{2}} \cos \frac{\pi}{4}$

We need the homogeneous solution (or natural solution to have $i(0) = 0$
(Next page))

Natural solution

$$① \quad i(t) = \frac{v(t)}{R+PL} \quad v(t) = 10 \cos 500t$$

If $v(t) = 0$ $i(t) \neq 0$ when $p = -\frac{R}{L}$, that is denominator = 0

$$\text{Thus } i(t) = B e^{-\frac{R}{L}t} = B e^{-500t}$$

$$i(0) = B = -\frac{1}{10\sqrt{2}} \cos(\frac{\pi}{4}) = -\frac{1}{20} \text{ from}$$

the previous page. Thus complete solution is

$$i(t) = \frac{1}{10\sqrt{2}} \cos(500t - \frac{\pi}{4}) - \frac{1}{20} e^{-500t}$$

Integration Factor Approach

obtain DE. From ① above

$$(R + L \frac{d}{dt}) i(t) = v(t)$$

$$\text{or } L \left(\frac{d}{dt} (i(t) e^{\int R/L dt}) \right) = v(t) e^{\int R/L dt} \quad \text{Integration factor}$$

integrate (definite integral) both sides

$$\int [i(t) e^{\int R/L dt} - i(0)] = \int_0^t v(t') e^{\int_0^{t'} R/L dt'} dt'$$

$$\int_0^t 10 \cos 500t' e^{\int_0^{t'} R/L dt'} dt' = 2 \operatorname{Re} \left[\int_0^t \frac{10}{\sqrt{2}} e^{j500t' + R/L t'} dt' \right]$$

$$= \operatorname{Re} \left[10 \frac{e^{j500t + R/L t} - 1}{j500 + R/L} \right] ; \quad R/L = 500$$

$$i(t) e^{500t} = \operatorname{Re} \left[\frac{10}{500\sqrt{2}} e^{-j\frac{\pi}{4}} (e^{j500t + 500t} - 1) \right]$$

$$\text{or } i(t) = \frac{1}{10\sqrt{2}} (\cos(500t - \frac{\pi}{4}) - \cos \frac{\pi}{4} e^{-500t})$$

which is the same as above