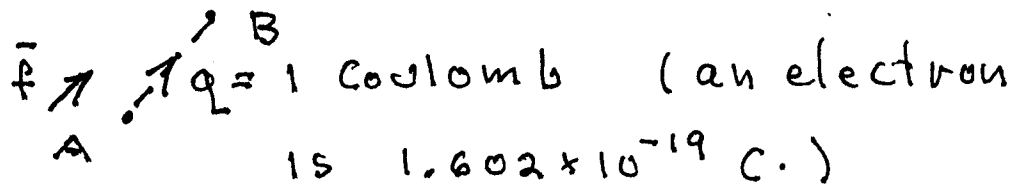


(1)

Variables we will deal with.

a) voltage - The work we do in moving a unit charge from point A to point B




$$\text{Work} = \underset{\substack{\uparrow \\ \text{newtons}}}{(\text{force we exert})} \times \underbrace{(B - A)}_{\text{meters}}$$

$= V_{BA} =$ Volts at B with respect to A. The voltage is always relative to some chosen reference point.

The work done by "the field" is thus $-V_{BA}$

b) Current - rate of flow of charge

$$i = \frac{dq(t)}{dt}$$

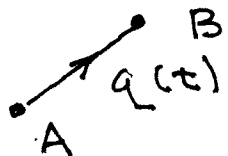

$$i_{BA} = \frac{dq(t)}{dt}$$

(what if $q(t)$ depends on where I am on A B \rightarrow then I had better specify the position as well!

$$i_{BA}(\vec{r}) = \frac{dq(t, \vec{r})}{dt}$$

(This generally does not happen for our purposes)


(2)

Example 1.2 $q(t) = 0.01 \sin(200t)$

$$i_{BA} = -0.01 \times 200 \cos(200t)$$

$$= -i_{AB}$$

Direction Choose Fig 1.14

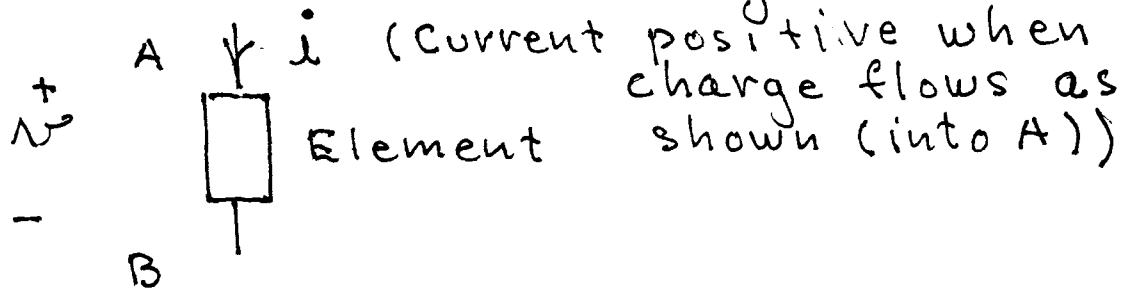

\mathcal{N} is positive when $V_{AB} > 0$

power?

Power = rate at which work is done

$$\Delta q \left(\frac{\text{force} \times \text{distance}}{\text{Coulomb}} \right) \frac{1}{\Delta t}$$

$$= \frac{\Delta q}{\Delta t} (V_{BA})$$

This is the work we do in overcoming the field to move charges from A to B. It's the work we put into the field


(3)

The work done by the field is the negative of this. This is the power of interest in electronics. Thus:

Power = rate at which work is done by the field is

$$= - \frac{\Delta q}{\Delta t} V_{BA} = \frac{(-\Delta q)}{\Delta t} V_{BA}$$

$$= i V_{BA}$$

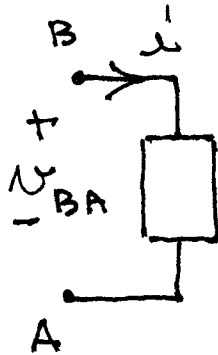

when the current reference is as shown. This implies field puts energy into the element. This can be dissipated or stored

Thus page 15

$$p = v i$$

↑ ↗ amps
Volts

$$= \frac{\text{joules}}{\text{coulomb}} \times \frac{\text{coulomb}}{\text{sec}} = \frac{\text{joules}}{\text{sec}}$$

$$\triangleq \text{Watts}$$

Basic Circuit Elements

Element	Symbol	Linear Relation	In. General
Resistor		$v = R i$	$v = R(p) i$ with $p = \frac{d}{dt} ; \frac{1}{p} = \dots$
Inductor		$v = L p i$	Can we write? $p(\frac{1}{p}) = 1$
Capacitor		$v = \frac{1}{c} \frac{1}{p} i$	Yes, since $\frac{d}{dt} \int_0^t v dt = v$


which $\underbrace{\hspace{2cm}}$
is $p \times \frac{1}{p} v = \dots$

Resistors

Basic σ conductivity (More/advanced)

Units $\frac{\text{Amps} \times \text{m}}{\text{m}^2 \times \text{Volt}} = \frac{\text{Amps}}{\text{Volt m}} = \frac{1}{\text{Ohm-m}}$

Ω is called Sieman
Ohm

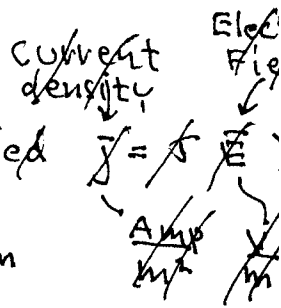


$\rho \triangleq \frac{1}{\sigma}$ called resistivity (units are Ohm-cm)

Table 2-1 of Maharibiz gives a table of resistivities

(Eg Al $2.62 \times 10^{-8} \Omega\text{-m}$ Si $2.3 \times 10^3 \Omega\text{-m}$)

Going from ρ to R (resistance)

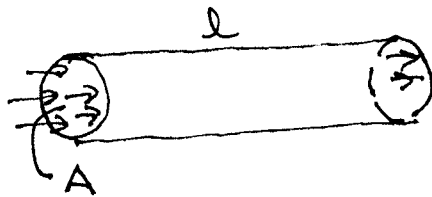

Total current is (Amps)
current density $\left(\frac{\text{Amps}}{\text{m}^2}\right) \times$
Area (m^2)

Thus σ gets multiplied by A to obtain current. Consequently its (ρ/A) to obtain "total resistivity"

Also Volts is "Electric Field multiplied by distance, l" so

$I = \text{Total current} = \sigma \times A \times \text{Electric Field}$
 $I = \sigma \times A \times \frac{\text{Volts}}{l} = \left(\frac{\sigma A}{l}\right) \text{Volts}$

Consequently, from this

$\text{Volts (V)} = \left(\frac{l}{\sigma A}\right) I \triangleq R' I$

Thus

$R = \frac{l}{\sigma A}$

Example Si Rod $d = 1\text{mm}$, 5cm long


$R = \rho \frac{l}{A} = 2.3 \times 10^3 \times \frac{.05}{\pi (0.5 \times 10^{-3})^2} \approx 3 \times 10^2 (\text{M}\Omega)$

2.2
1.4
88
22
308

Various types of resistors

- Thermistor
- Piezoresistor
- Rheostat
- Potentiometer

$v = iR \rightarrow \text{plot}$

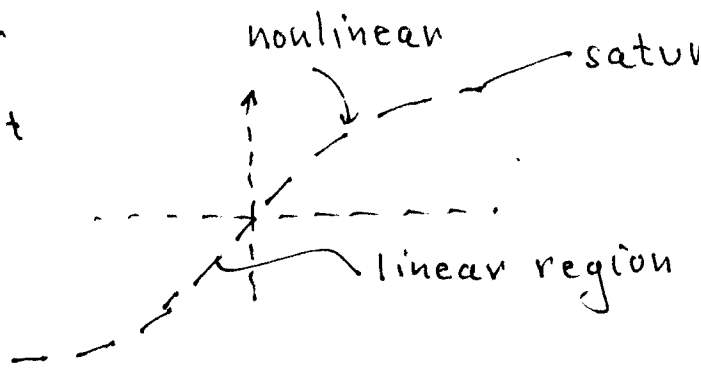

power Watts = Volts x Amps
 (How do we establish this? Force = charge x Field
 coulomb (charge unit) $\frac{V}{m}$

Energy = Force x distance
 = Force x (meters)

Thus [Force x (m)] = (charge x $\frac{V}{m}$) x m

Power = Energy/time = (charge/time) x V
 = current x V
 = i v


To calculate power then

power = i v = i (i R) = i² R

Can work out Example 2-1 dc. Motor

⑥

A circuit element is abstracted as

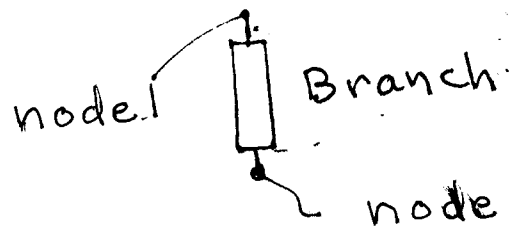

- A node in a circuit is a conducting connection of two or more elements
- A branch is a trace between two nodes
- A path - trace of continuous sequence of branches for which a node is encountered only once
- A loop - path ending and starting on the same node
 - * Independent - one that contains at least one branch not contained in another loop
 - * Mesh - loop that encloses no other loop

Basic Theorem $b = \text{No of Branches}$ $l = \text{No of independent loops}$ $n = \text{No of nodes}$

$$b = n + l - 1 \quad - \text{ prove by induction}$$

7

Proof
(Induction)



$$b = 1$$
$$n = 1$$
$$l = 1$$

$$b = n + l - 1$$

True

Assume True ($b_n = n_n + l_n - 1$)



add 2 loops
and node

$$b = b_n + 2$$

$$n = n_n + 1$$

$$\therefore (b_n + 2) = (n_n + 1) + (l_n + 1) - 1$$


Thus $b = n + l - 1$ — true

Thus true in general

Series And Parallel



Series!

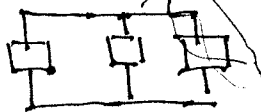

parallel!

Planar — If we can possibly draw the circuit in 2d.

(8)
Loop and Node Systems of Equations


↓
Kirchoff's
Voltage "Law"

↓
Kirchoff's
Current "Law" (KCL)

KCL → conservation of charge
Nodes do not store charge

Thus sum of currents into or out of a node has to be zero.

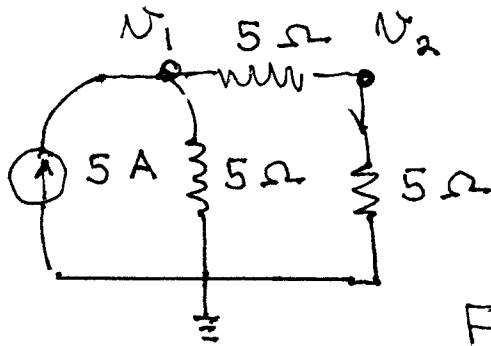Ideal for circuits with Nodes and current sources. Let unknowns be node voltages - pick one as ground (our zero). So $n-1$ independent equations. for $n-1$ node voltages.



$$5 = \frac{V_1}{5} + \frac{(V_1 - V_2)}{5}$$

$$\frac{V_2}{5} + \frac{V_2 - V_1}{5} = 0$$

Find V_2

Simultaneous Equations

Graphical Solution Technique


$$G = \frac{1}{\Delta} \sum_{\text{All Forward paths}} G_k \Delta_k$$

Variant of Cramer's Rule


$$V_1 \left(\frac{1}{5} + \frac{1}{5} \right) = \frac{V_2}{5} + 5$$

$$V_2 \left(\frac{1}{5} + \frac{1}{5} \right) = \frac{V_1}{5}$$
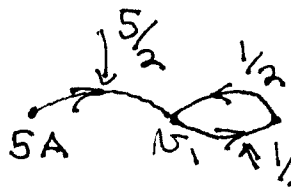
$$V_2 = 5G = 5 \times \frac{5}{4} \times \frac{1}{1 - \frac{1}{4}} = 20$$




Other way combining resistors.

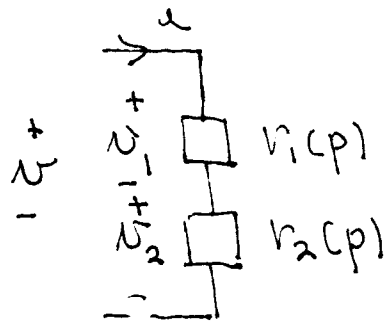


$$\begin{aligned}
 v &= v_1 + v_2 \\
 &= i_1 r_1(p) + i_2 r_2(p) \\
 &= i (r_1(p) + r_2(p)) \\
 &= i (r(p))
 \end{aligned}$$

Thus $r(p) = r_1(p) + r_2(p)$

So circuit is equivalent to

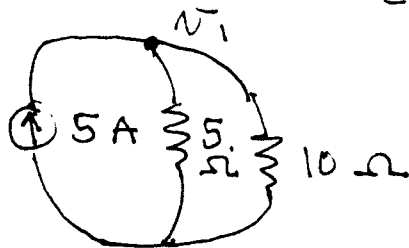


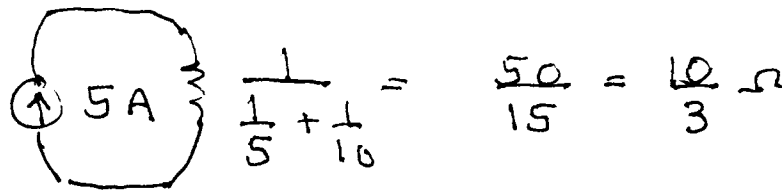prove resistors in parallel add inversely! So equivalent to



$$\therefore v_1 = 5 \text{ A} \times \frac{10}{3} \Omega = \frac{50}{3} \text{ V}$$

Now we unfold it.

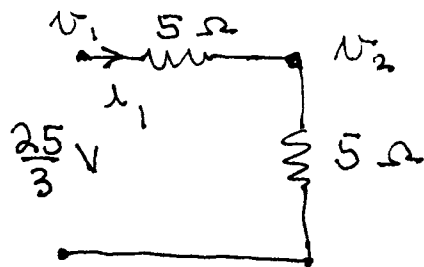

$$i_1 = \frac{v_1}{10} = \frac{50}{30} \text{ Amp}$$

$$\therefore v_2 = 5 \times i_1 = \frac{25}{3} \text{ Volt}$$

We have actually use KVL

KVL - The potential at any point is uniquely defined. Thus the sum of the voltage drops across elements around a loop must be zero