
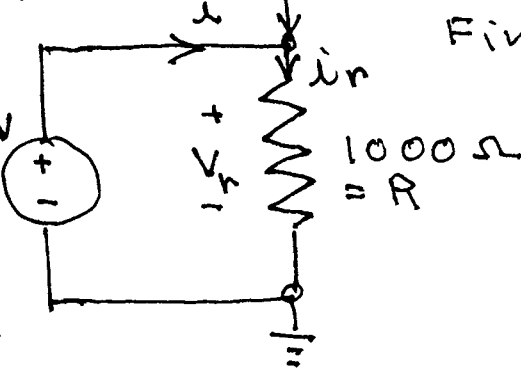


Example Calculation With Resistor

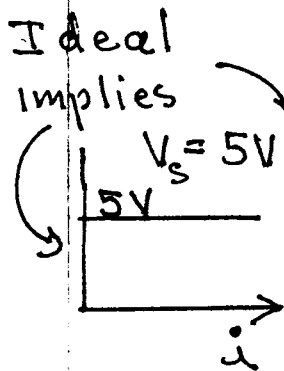

Find the current

KVL

$$V_r = V_s = 5 \text{ Volts}$$

Branch relation

$$V_r = i R$$

$$= i \times 1000$$

$$\therefore i = \frac{V_r}{1000} = 5 \times 10^{-3} \text{ A} = 5 \text{ mA}$$

What is the power dissipated

$$\begin{aligned} \text{Power delivered} &= 5 \text{ V} \times 5 \text{ mA} \\ &= 25 \times 10^{-3} \text{ Watts} \\ &= i^2 R \end{aligned}$$

↑ J/sec



Energy dissipated in 1 hr

$$\begin{aligned} &= 25 \times 10^{-3} \times 3600 \text{ Watt hr} \\ &= .25 \times 360 \text{ Watt hr} \\ &= 90 \text{ Watt hr} = .09 \text{ kWatt hr} \end{aligned}$$


If the voltage source is limited to 100 mA, how small can R be and still experience 5 V ; ans. $\frac{5V}{100 \text{ mA}} = 50 \Omega$

Below this the source


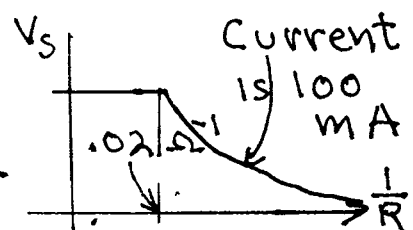
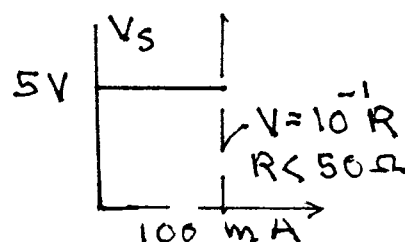
acts as a current source and the voltage falls



Non Ideal Voltage Source

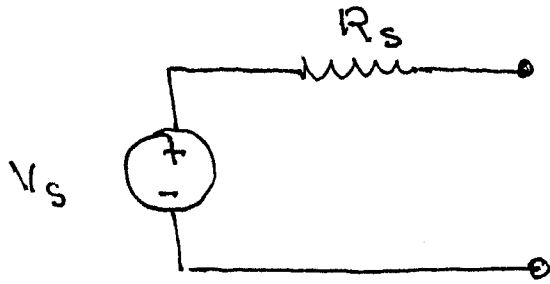

Solar Generator (p-n junction)

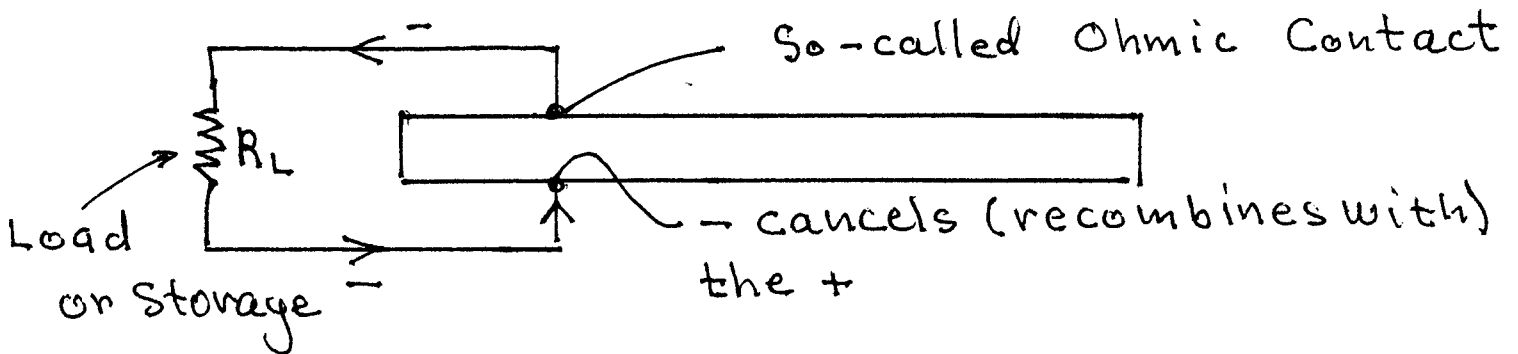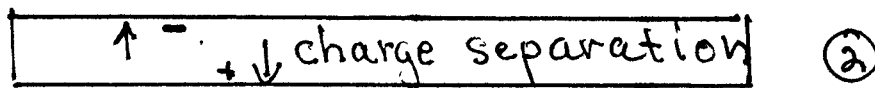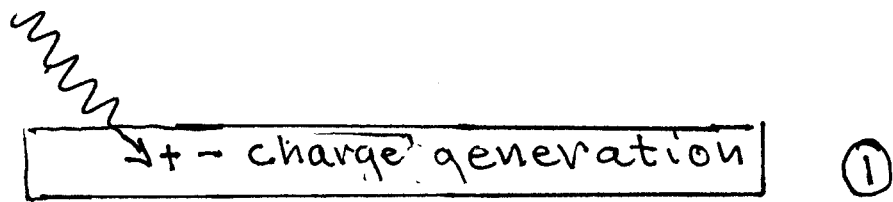

Solar radiation $\approx 1 \text{ kW/m}^2$

Efficiency $\approx 20\%$

- Problems :
- a) loss of carrier energy during separation
 - b) recombining of electron and + in the material
 - c) Absorption of sunlight depends upon color
 - d) Ohmic Contacts
 - e) R_s

(3) Loop and Node Systems of Equations


↓
Kirchoff's
Voltage "Law"

↓
Kirchoff's
Current "Law" (KCL)

KCL → conservation of charge
Nodes do not store charge

Thus sum of currents into or out of a node
has to be zero.

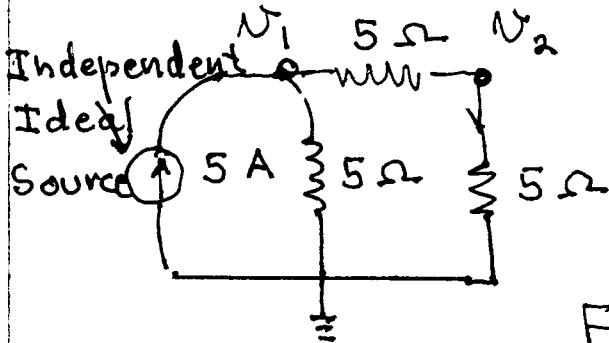Ideal for circuits with Nodes and current sources. Let unknowns be node voltages - pick one as ground (our zero) So $n-1$ independent equations. for $n-1$ node voltages,



$$5 = \frac{V_1}{5} + \frac{(V_1 - V_2)}{5}$$

$$\frac{V_2}{5} + \frac{V_2 - V_1}{5} = 0$$

Find V_2

Simultaneous Equations


Graphical Solution Technique

$$G = \frac{1}{\Delta} \sum_{\text{All Forward paths}} G_k \Delta_k$$

Variant of
Cramer's Rule

$$V_1 \left(\frac{1}{5} + \frac{1}{5} \right) = \frac{V_2}{5} + 5$$

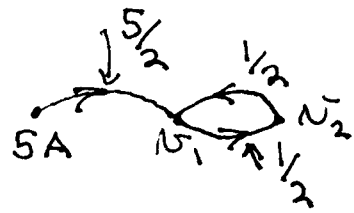
$$V_2 \left(\frac{1}{5} + \frac{1}{5} \right) = \frac{V_1}{5}$$



$$V_2 = 5G = 5 \times \frac{5}{4} \frac{1}{1 - \frac{1}{4}} = 2\frac{5}{3} \text{ Volts}$$

(4)


Other way combining resistors.

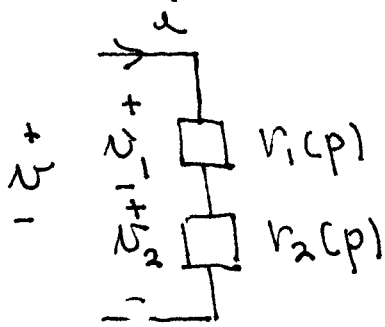


$$\begin{aligned}
 v &= v_1 + v_2 \\
 &= i_1 r_1(p) + i_2 r_2(p) \\
 &= i (r_1(p) + r_2(p)) \\
 &= i (r(p))
 \end{aligned}$$

Thus $r(p) = r_1(p) + r_2(p)$

So circuit is equivalent to

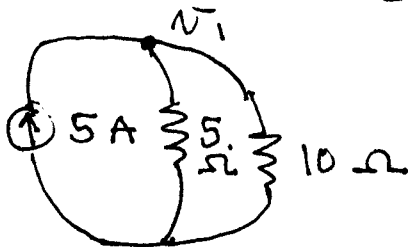


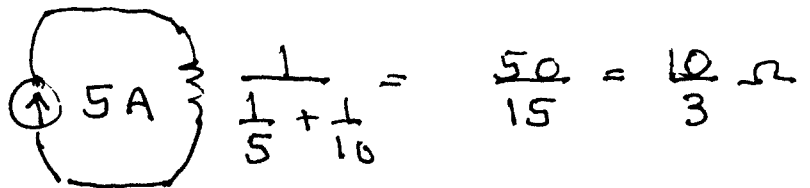prove resistors in parallel add inversely! So equivalent to



$$\therefore v_1 = 5 \text{ A} \times \frac{10}{3} \Omega = \frac{50}{3} \text{ V}$$

Now we unfold it.

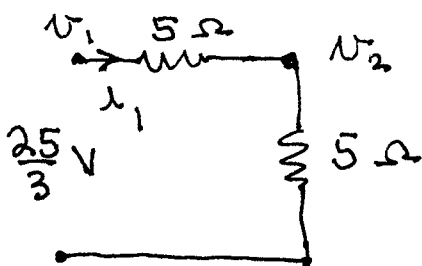


$$i_1 = \frac{v_1}{10} = \frac{50}{30} \text{ Amps}$$

$$\therefore v_2 = 5 \times i_1 = \frac{25}{3} \text{ Volts}$$

We have actually use KVL

KVL - The potential at any point is uniquely defined. Thus the sum of the voltage drops across elements around a loop must be zero

Current Division

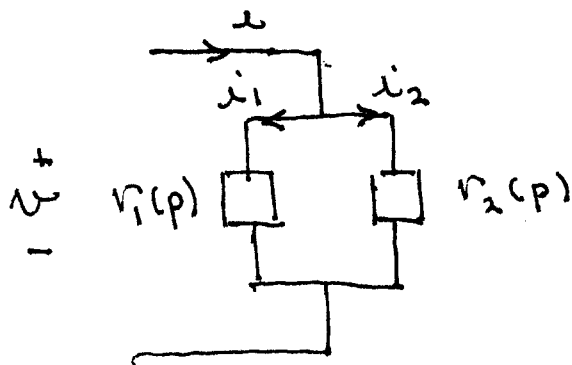


$$\begin{aligned}
 i &= i_1 + i_2 \\
 &= \frac{v}{r_1(p)} + \frac{v}{r_2(p)} \\
 &= \frac{v}{r(p)}
 \end{aligned}$$

$$\therefore v = i / \left(\frac{1}{r_1(p)} + \frac{1}{r_2(p)} \right)$$

$$i_2 = \frac{v}{r_2(p)} = i \left(\frac{\frac{1}{r_2(p)}}{\frac{1}{r_1(p)} + \frac{1}{r_2(p)}} \right)$$

Example page 65

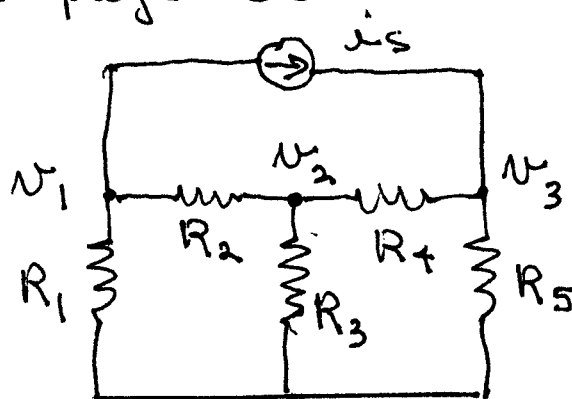

Once we have node voltages we have all variables since we can use branch

relations to obtain currents

$$\frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} + i_s = 0$$

$$\frac{v_2 - v_1}{R_2} + \frac{v_2}{R_3} + \frac{v_2 - v_3}{R_4} = 0$$

$$\frac{v_3}{R_5} - i_s + \frac{v_3 - v_2}{R_4} = 0$$

Solving. Write equations as


(6)

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = V_2 / R_2 - i_s \rightarrow \text{write as } V_1 = T_1 V_2 + T_2 i_s$$

$$V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) = V_1 / R_2 + V_3 / R_4 \rightarrow \text{write as } V_2 = T_3 V_1 + T_4 V_3$$

$$V_3 \left(\frac{1}{R_5} + \frac{1}{R_4} \right) = V_2 / R_4 + i_s \rightarrow \text{write as } V_3 = T_5 V_2 + T_6 i_s$$

Draw a graph

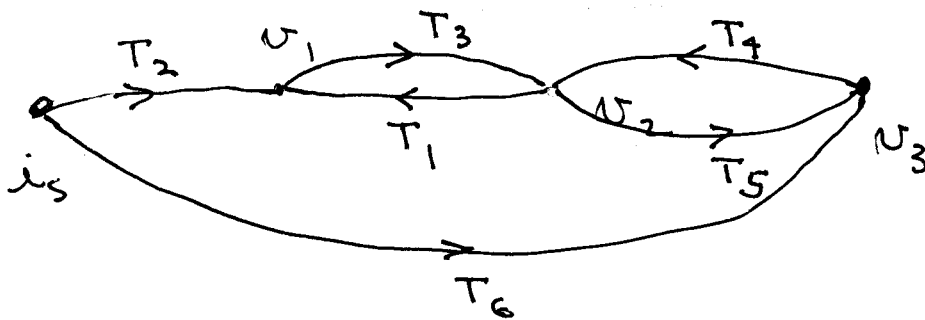

Definitions

$$T_2 = - \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$T_1 = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$T_3 = \frac{\frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_3}}$$

$$T_4 = \frac{\frac{1}{R_4}}{\frac{1}{R_2} + \frac{1}{R_3}}$$

$$T_5 = \frac{\frac{1}{R_4}}{\frac{1}{R_5} + \frac{1}{R_4}}$$

$$T_6 = \frac{1}{\frac{1}{R_5} + \frac{1}{R_4}}$$

solve for V_3

$$V_3 = \frac{(T_2 T_3 T_5 + T_6 (1 - T_1 T_3)) i_s}{1 - T_3 T_1 - T_4 T_5} i_s$$

Alternate and more common

$$\begin{vmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & 0 \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ 0 & -\frac{1}{R_4} & \frac{1}{R_4} + \frac{1}{R_5} \end{vmatrix} \begin{matrix} V_1 \\ V_2 \\ V_3 \end{matrix} = \begin{matrix} i_s \\ 0 \\ i_s \end{matrix}$$


solution

$$V_3 = \frac{\Delta_{13}}{\Delta} i_s + \frac{\Delta_{33}}{\Delta} i_s$$

Δ = determinant
row column
 Δ_{13} = 13 cofactor

$$\text{General } V_j = \frac{\Delta}{\Delta} \text{ cause}_j \times (\text{cause})$$

Example: The Delta-Y Transformation (7)

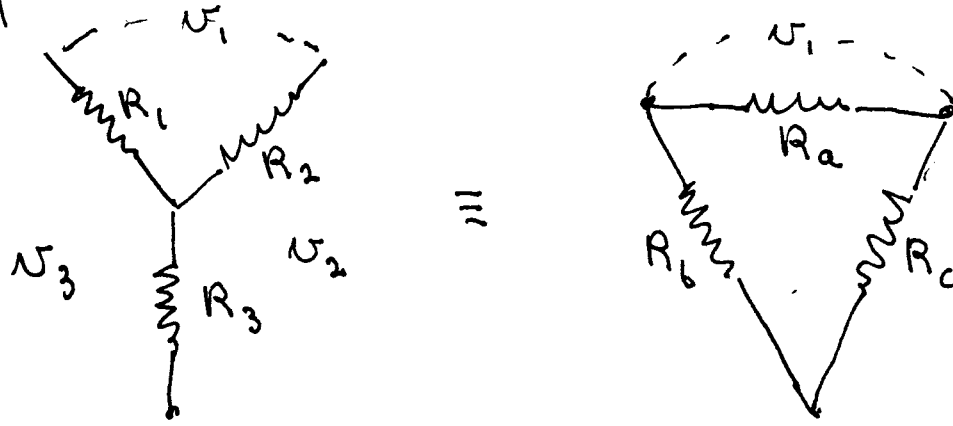

$$U_1 = (R_1 + R_2) i_1$$


$$U_1 = \left(\frac{R_b + R_c}{R_a + R_b + R_c} \right) R_a i_1$$

$$\therefore R_1 + R_2 = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c} = T_1$$

cyclically permute

$$R_2 + R_3 = \frac{R_c (R_a + R_b)}{R_a + R_b + R_c} = T_2$$
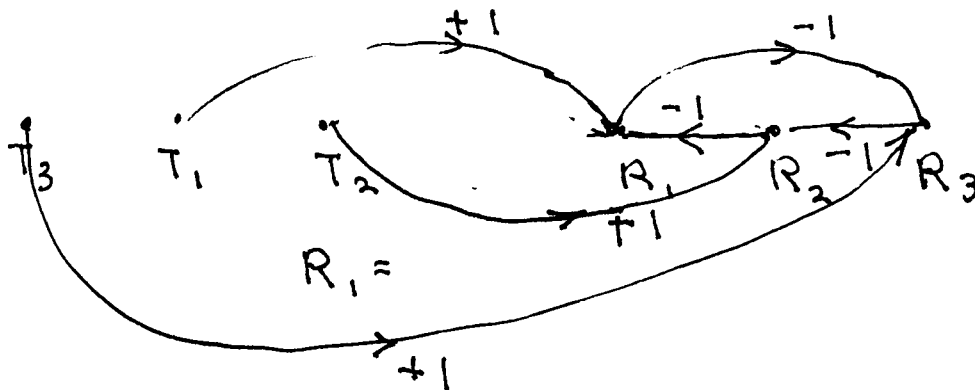
$$R_3 + R_1 = \frac{R_b (R_c + R_a)}{R_a + R_b + R_c} = T_3$$



Cramers Rule

$$R_1 = (-T_2 + T_1 + T_3) / 2$$

$$= (R_a R_b) / (R_a + R_b + R_c)$$

$$R_2 = (-T_3 + T_1 + T_2) / 2$$

$$= R_c R_a / (R_a + R_b + R_c)$$

$$R_3 = R_b R_c / (R_a + R_b + R_c)$$

Note $R_1 R_2 + R_2 R_3 + R_3 R_1$

$$= (R_a^2 R_b R_c + R_c^2 R_a R_b + R_b^2 R_c R_a) / (R_a + R_b + R_c)^2$$

$$= R_a (R_a R_b R_c + R_c^2 R_b + R_b^2 R_c) / (R_a + R_b + R_c)^2$$

$$= R_a R_b R_c (\cancel{R_a + R_c + R_b}) / (R_a + R_c + R_b)^2$$

$$= R_a R_b R_c / (R_a + R_b + R_c)$$

$$= R_a R_3 = R_b R_2 = R_c R_1$$

Thus $R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

Table 1-4: Passive circuit elements and their symbols.













Element	Symbol	$i-v$ Relationship
Resistor		$v_R = R i_R$
Capacitor		<p>Define $\frac{d}{dt} \triangleq p$ treat it as any number</p> $i_C = C \frac{dv_C}{dt} = C p v_C$ so $v_C = \left(\frac{1}{C p}\right) i_C$ $= v_C(p) i_C$
Inductor		$v_L = L \frac{di_L}{dt} = L p i_L = v_L(p) i_L$ so $i_L = \frac{1}{L p} v_L$

Table 1-3: Voltage and current sources.

Independent Sources	
<p>Ideal Voltage Source</p>  <p>Battery dc source Any source*</p>	<p>Realistic Voltage Source</p>  <p>Any source</p>
<p>Ideal Current Source</p>  <p>dc source Any source</p>	<p>Realistic Current Source</p>  <p>Any source</p>
Dependent Sources	
<p>Voltage-Controlled Voltage Source (VCVS)</p>  <p>$v_s = \alpha v_x$</p>	<p>Voltage-Controlled Current Source (VCCS)</p>  <p>$i_s = g v_x$</p>
<p>Current-Controlled Voltage Source (CCVS)</p>  <p>$v_s = r i_x$</p>	<p>Current-Controlled Current Source (CCCS)</p>  <p>$i_s = \beta i_x$</p>
<p><i>Note: α, g, r, and β are constants; v_x and i_x are a specific voltage and a specific current elsewhere in the circuit. *Lowercase v and i represent voltage and current sources that may or may not be time varying, whereas uppercase V and I denote dc sources.</i></p>	

Fun With LT Spice .

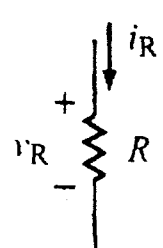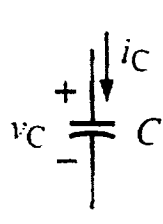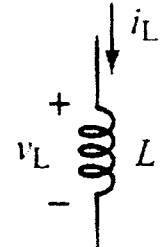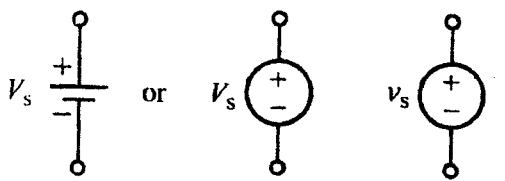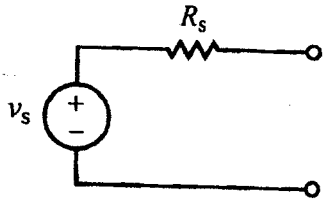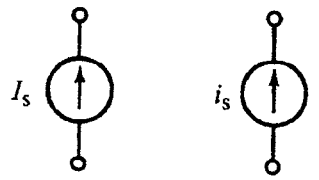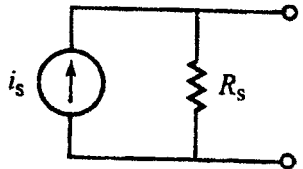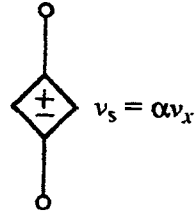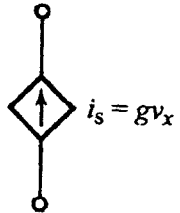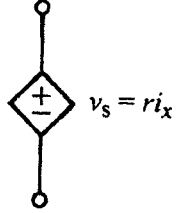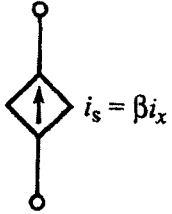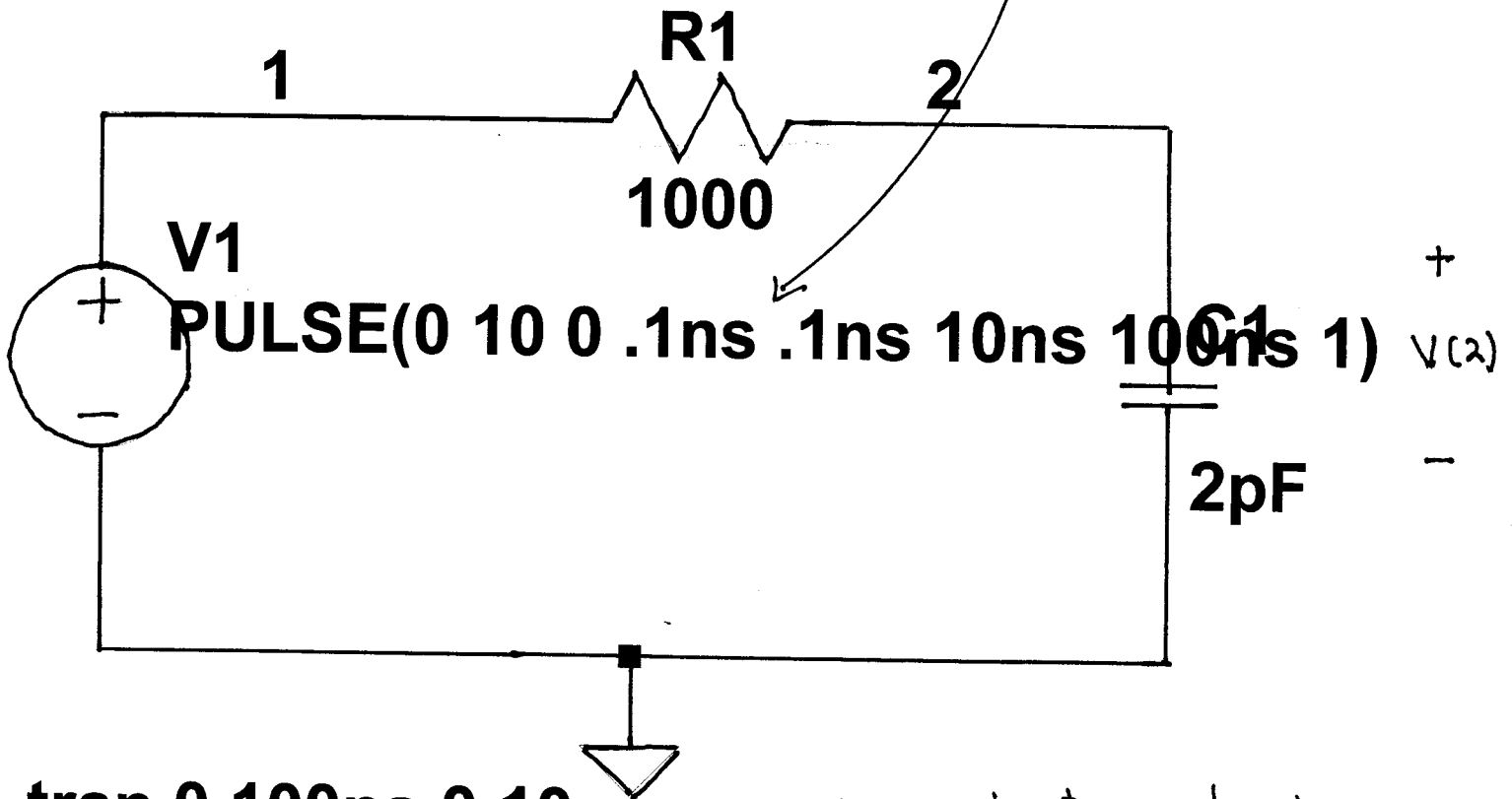
Pulse starting at 0 Volts ramping up to 10 Volts with a rise-time .1nsec, fall time of .1nsec, 10nsec. in duration a period of 100nsec. 1 cycle plotted. This is the spice netlist statement



`.tran 0 100ns 0 10ns` ← transient analysis

from 0 to 100nsec for a pulse from 0 to 10nsec


Result for V(2) next page

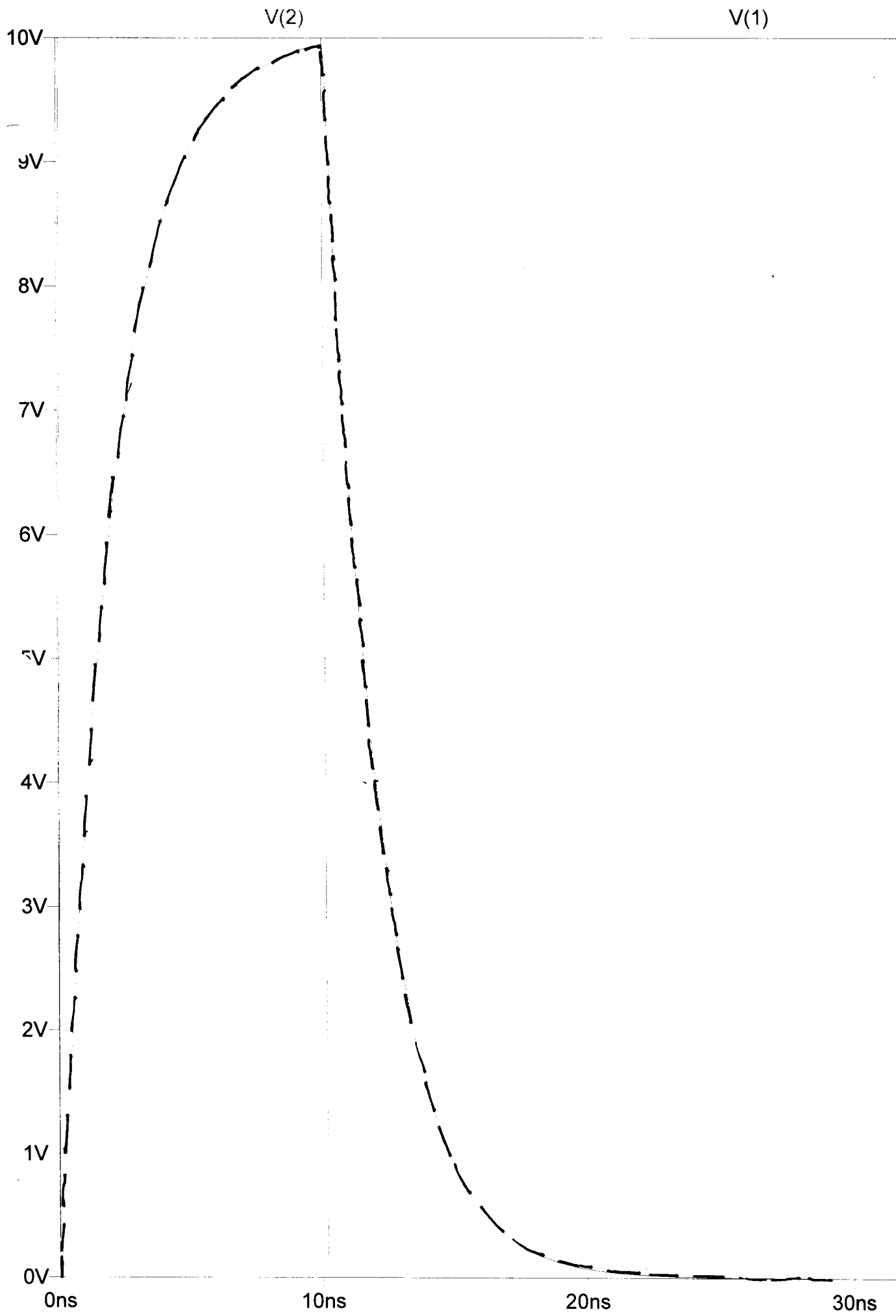

--- H:\WebDesign\Templates\Documents\Simulations\RC_Circuit_Vc_Pulse.raw

Try This For Fun With LT Spice

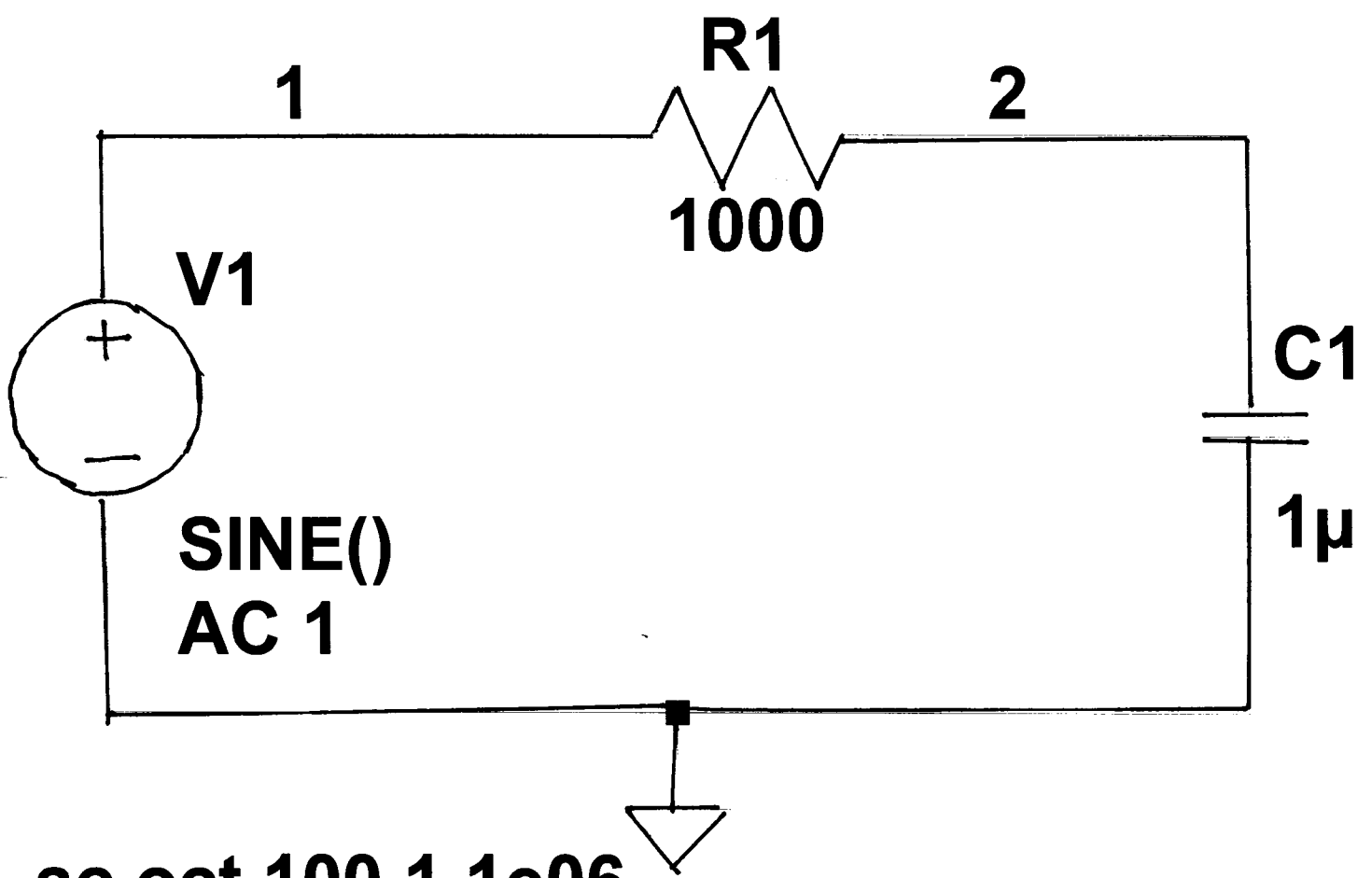R-C Circuit LTSpice
sinwave excitation
frequency scanned from
100 Hz to 10⁶ Hz



V(2)

