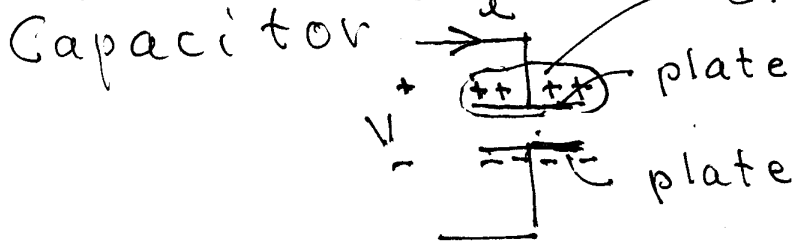


Capacitor & Inductor: They do not dissipate energy - They store it!



$$i = \frac{dQ}{dt}$$

Q proportional to V


$Q \propto V$ $C = \text{capacitance}$

$Q = CV$ [Farads]

$$\text{Thus } i = \frac{dQ}{dt} = C \frac{dV}{dt} = Cp V(t)$$

$$V(t) = \frac{1}{pC} i(t) = r_C(p) i(t)$$

Inductor coil of wire

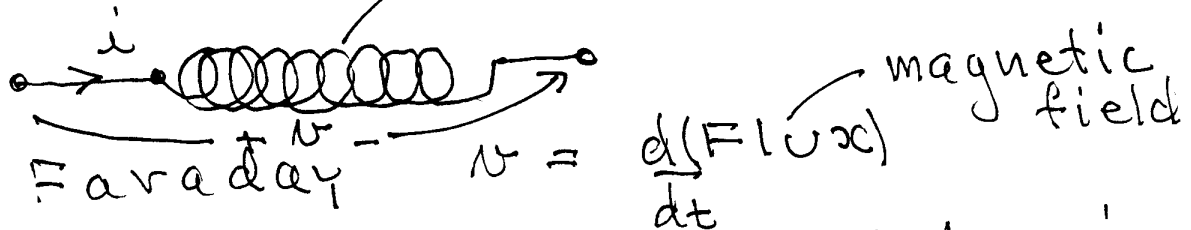


But Flux proportional to i

$$\text{Flux} = Li \quad L = \text{inductance [Henries]}$$


$$\text{Thus } v = L \frac{di}{dt} = pL i(t) = r_L(p) i(t)$$

Treat $r_C(p) = \frac{1}{pC}$ and $r_L(p) = pL$ as any resistor (Do the same algebra)

Examples of Thevenin and Norton

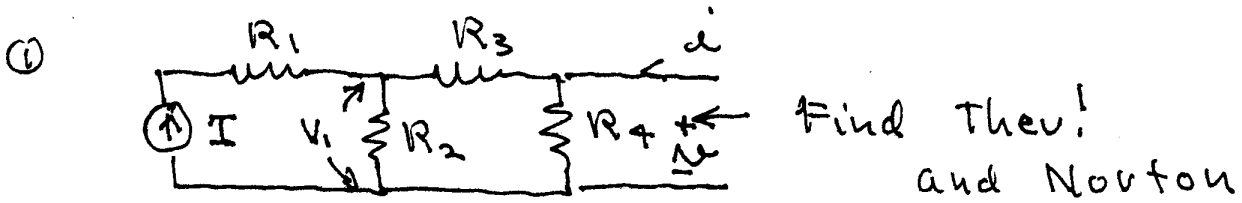

a) Find R_{eq}
Open I

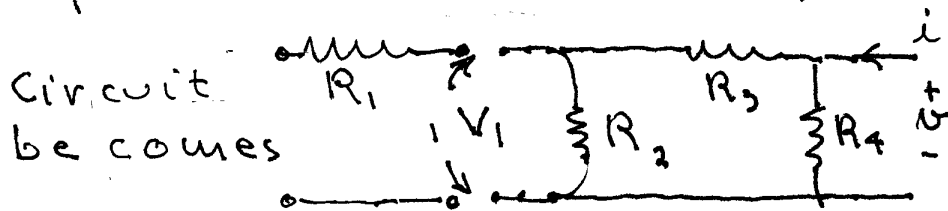


Combine R_2 , R_3 & R_4 to obtain R_{eq}
(looking in from v)

$$R_{eq} = R_4 \parallel (R_3 + R_2) = \frac{R_4 (R_3 + R_2)}{R_2 + R_3 + R_4}$$

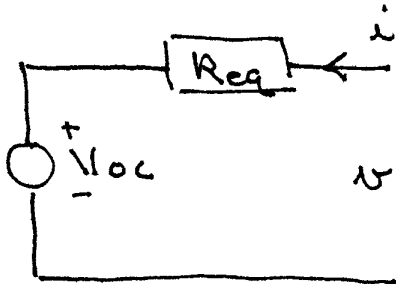
b) Use voltage divider to find V_{oc}

$$V_{oc} = V_1 \left(\frac{R_4}{R_4 + R_3} \right)$$

$$\text{But } V_1 = I R_2 \parallel (R_3 + R_4) = I \frac{R_2 (R_3 + R_4)}{R_2 + R_3 + R_4} \frac{R_4}{R_4 + R_3}$$



Norton

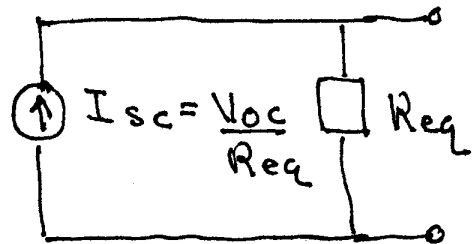

②

Can also find $I_{sc} = I \left(\frac{R_2}{R_2 + R_3} \right)$ (current divider)
Then $R_{eq} = \frac{V_{oc}}{I_{sc}}$

$$= \frac{(R_2 + R_3) \times \cancel{I} \cancel{R_2}}{R_2 \cancel{I}} \times \frac{R_4}{R_2 + R_3 + R_4} (R_4 + R_3)$$


which is the same as above.

② Replace R_4 by an inductor, find R_{eq} , V_{oc} and I_{sc} .

ans. simply substitute $R_4 = pL$
in the above

Note In general then I is time varying (otherwise $V_L = L \frac{di_L}{dt} = 0$, the inductor is a short (d.c.))

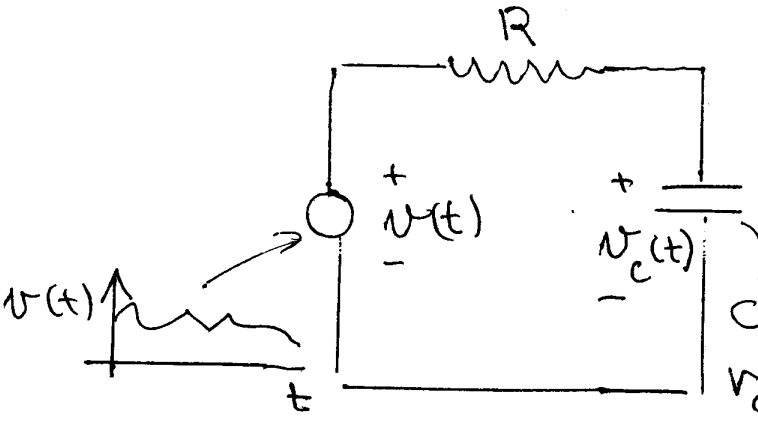Simple Derivation using $p = \frac{d}{dt}$ "operator" when we have storage elements (L and C)
Consider



Find the DE for $v_c(t)$

Capacitor $v_c(p) = \frac{1}{pC}$: Treat p as any number

Use the voltage divider relation

$$v_c(t) = \frac{v_c(p)}{v_c(p) + R} v(t)$$

$$= \frac{\frac{1}{pC}}{\frac{1}{pC} + R} v(t)$$

Now clear the p 's

a) multiply through by pC on the R.H.S.

$$v_c(t) = \frac{1}{1 + pCR} v(t)$$

b) multiply both sides by $(1 + pCR)$

$$(1 + pCR) v_c(t) = v(t)$$


c) let $p = \frac{d}{dt}$ so the final DE

$$is \quad v_c(t) + CR \frac{dv_c}{dt} = v(t)$$

One of the LT spice pictures shows the solution when $v(t)$ is a rectangular pulse

page 71

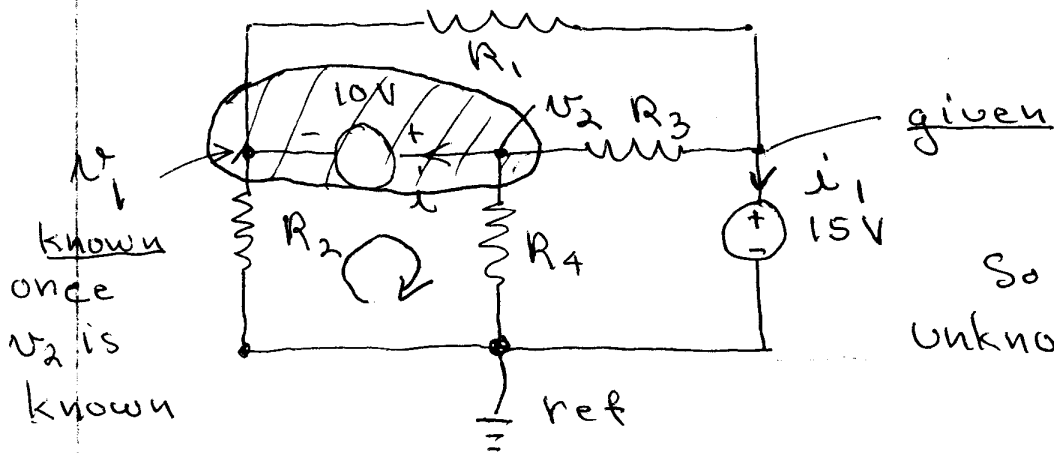Node Analysis with a Voltage Source
Super nodes.



known
once
 v_2 is
known

given

So only one
unknown - v

①
$$\frac{v_2 - 15}{R_3} + \frac{v_2}{R_4} + i = 0$$

gives i once v_2 is known

②
$$\frac{v_1}{R_2} - i + \frac{v_1 - 15}{R_1} = 0$$


③ KVL $\rightarrow v_1 + 10 = v_2$

④ plus ② to eliminate i in supernode equation

$$v_2 \left(\frac{1}{R_3} + \frac{1}{R_4} \right) + v_1 \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{15}{R_3} - \frac{15}{R_1} = 0$$

Use ④ & ③ to obtain v_2 and v_1

Graph

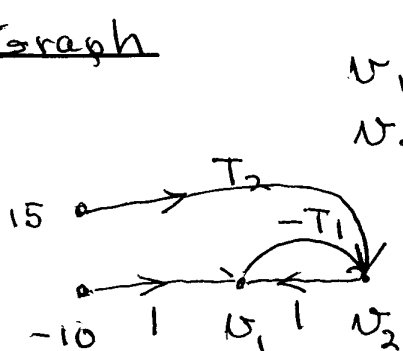

$v_1 = -10 + v_2$

$$v_2 = -v_1 \frac{(\frac{1}{R_2} + \frac{1}{R_1})}{(\frac{1}{R_3} + \frac{1}{R_4})} + 15 \frac{(\frac{1}{R_3} + \frac{1}{R_1})}{(\frac{1}{R_3} + \frac{1}{R_4})}$$

$$v_1 = \frac{-10 + 15 \times T_2}{1 + T_1}$$

$$v_2 = \frac{[-T_2 \times 15 + T_1(10)]}{(1 + T_1)}$$