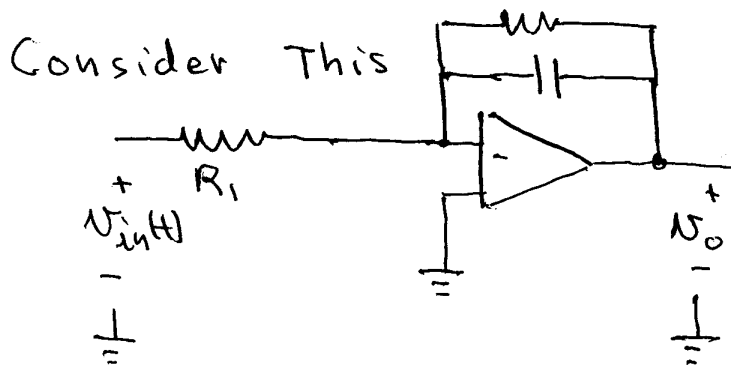


Exponential Excitation




$V_{in} = e^{st}$
a growing
exponential
excitation

$$\frac{V_o}{\frac{1}{pC} \parallel R} = \frac{V_{in}}{R}$$

$$V_o = \frac{1}{R} \frac{R}{1 + pCR} V_{in}(t)$$
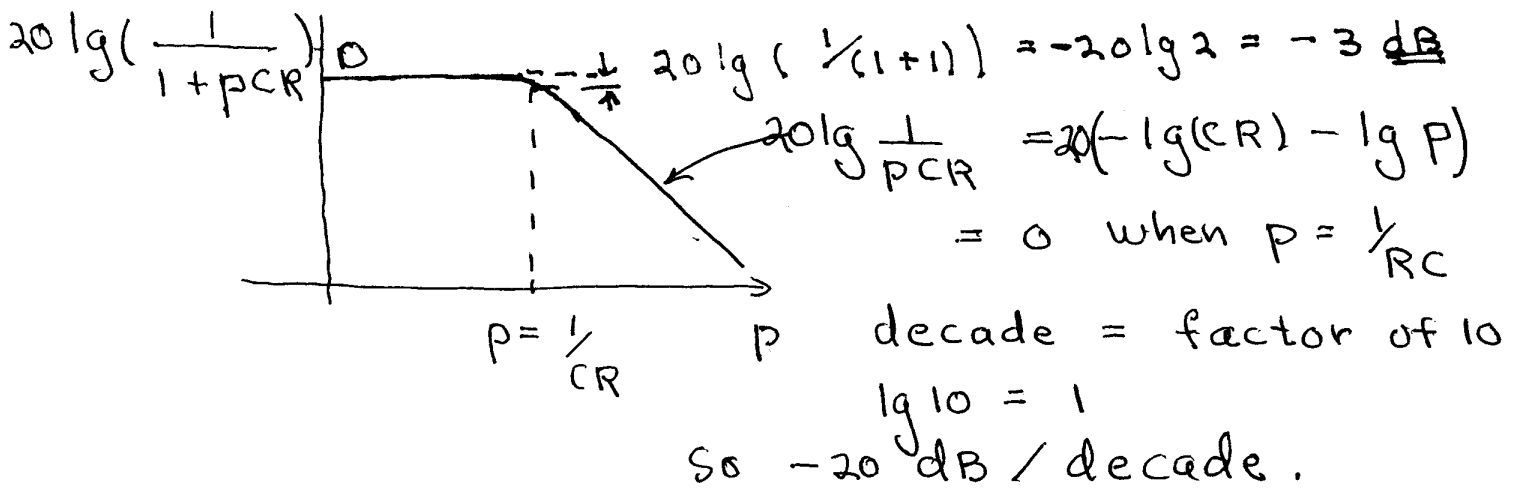
$$= \frac{1}{1 + pCR} V_{in}(t) \quad \text{--- (1)}$$



What is p - consider the differential equation from (1) $(1 + pCR) V_o(t) = V_{in}(t)$ with $V_{in}(t) = A e^{st}$ \rightarrow a growing exponential

Assuming $V_o(t) = \text{Constant} + \text{Constant} e^{st}$,
 for $V_o(t)$, the D.E. implies

$$(1 + RC \frac{d}{dt}) V_o(t) = A e^{st} \quad (2)$$

$$B + D e^{st} + RC p D e^{st} = A e^{st}$$

Thus $B = 0$ $D = \frac{A}{1 + sRC}$

Consequently, the above plot is telling one that as $p = s$ increase beyond $1/RC$, the voltage across the capacitor decreases below the excitation amplitude. The voltage to an increasing extent is dropped across the resistor.

Example 2 let $V_{in}(t) = D e^{j\omega t} \rightarrow \text{complex}$

Now we just substitute $p = j\omega$
 (If you don't believe this just put it into Eq(2) with the $A e^{pt}$ replaced by $A e^{j\omega t}$)

$$\text{Thus } D = \frac{A}{1 + j\omega RC} = \frac{A}{\sqrt{1 + (\omega RC)^2}} e^{-j \tan^{-1}(\omega RC)}$$

when we change to polar notation for the complex number $1 + j\omega RC$

These are precisely the parameters plotted in problem set 3 problem 2