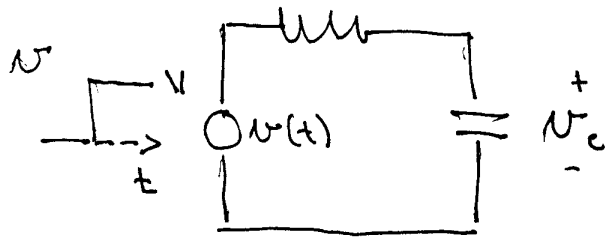


# Exponential Response of a Capacitor Resistor Circuit.



$$V_c(t) = \frac{1/p_c}{1/p_c + R} V(t)$$

$$= \frac{1}{p_c R} \frac{1}{1 + 1/p_c R} \cdot V(t) \quad (1)$$

expand  $\frac{1}{1 + 1/p_c R}$  using  $\frac{1}{1+x} = 1 - x + x^2 - x^3 + \dots$   
with  $x = \frac{1}{p_c R}$

$$\frac{1}{p} = \int dt$$

$$\therefore V_c(t) = \left( \frac{1}{p_c R} - \frac{1}{(p_c R)^2} + \frac{1}{(p_c R)^3} - \dots \right) V(t)$$


integral      double integral      (integral of double integral) ...

$V(t) = V$  a constant so

$$V_c(t) = \frac{V}{CR} \left( t - \frac{1}{CR} \frac{t^2}{2} + \frac{t^3}{3 \cdot 2 (CR)^2} - \dots \right)$$

$$= V \left( \frac{1}{CR} - \left( 1 - \frac{t}{RC} - \frac{1}{2} \left( \frac{t}{RC} \right)^2 + \frac{1}{3!} \left( \frac{t}{RC} \right)^3 + \dots \right) \right)$$

(2)  $V_c(t) = V(1 - e^{-t/RC})$

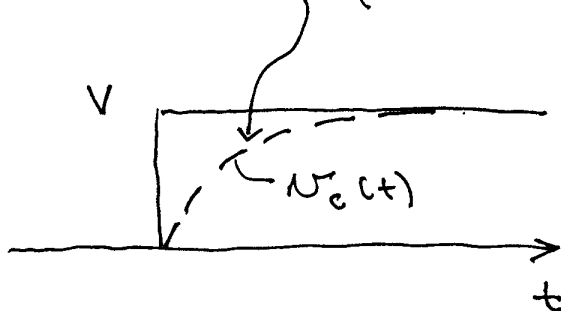

Differential Equation  
From (1)

$$(3) - (p_c R + 1) V_c(t) = V(t)$$

$$CR \frac{dV_c}{dt} + V_c(t) = V$$

Substitute Eq (2)

$$CR \frac{dV_c}{dt} = +V e^{-t/RC}$$

Thus we immediately see this satisfies (3) with  $V_c(0) = 0$  (initially uncharged)