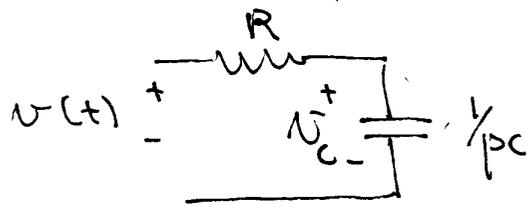


St. State Response of An RC Circuit

(1)



$$V_c = \frac{\frac{1}{pC}}{\frac{1}{pC} + R} v(t)$$

$$= \frac{1}{1 + pCR} v(t)$$

Expand $\frac{1}{1 + pCR} = 1 - pCR + (pCR)^2 - \dots$

∴ If $v(t) = V \sin \omega t$


$$V_c(t) = V (\sin \omega t - (\omega CR) \cos \omega t + (\omega CR)^2 \sin \omega t - (\omega CR)^3 \cos \omega t + (\omega CR)^4 \sin \omega t + \dots)$$

$$= V [\sin \omega t (1 + (\omega CR)^2 + (\omega CR)^4 + \dots) - \cos \omega t (\omega CR) (1 + (\omega CR)^2 + (\omega CR)^4 + \dots)]$$

$$= V (\sin \omega t \frac{1}{(1 + (\omega CR)^2)} - \cos \omega t \frac{\omega CR}{1 + (\omega CR)^2})$$

$$= V (\sin \omega t \frac{1}{(1 + (\omega CR)^2)} - \cos \omega t \frac{\omega CR}{1 + (\omega CR)^2})$$

Define ϕ - phase angle

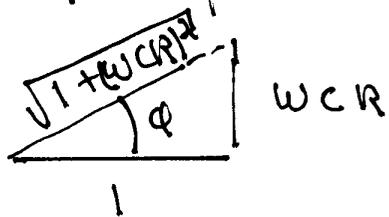

$$\tan^{-1} \omega CR = \phi$$

Thus $V_c(t) = \frac{V}{\sqrt{1 + (\omega CR)^2}} [\sin \omega t \cos \phi - \cos \omega t \sin \phi]$

$$= \frac{V}{\sqrt{1 + (\omega CR)^2}} \sin(\omega t - \phi)$$

Second Way! Use exponential Notation ②
 for $\sin \omega t = \frac{e^{j\omega t}}{2j} - \frac{e^{-j\omega t}}{2j}$

$$\frac{1}{1+pCR} \sin \omega t = \left(\frac{1}{1+pCR} \left(\frac{e^{j\omega t}}{2j} - \frac{e^{-j\omega t}}{2j} \right) \right)$$

$$= (1 - pCR + (pCR)^2 + \dots) \left(\frac{e^{j\omega t}}{2j} - \frac{e^{-j\omega t}}{2j} \right)$$

$$= (1 - (j\omega CR) + (j\omega CR)^2 + \dots) \frac{e^{j\omega t}}{2j} - (1 - (-j\omega CR) + (j\omega CR)^2 + \dots) \frac{e^{-j\omega t}}{2j}$$

Complex Conjugates

$$= \underbrace{\left(\frac{1}{1 + j\omega CR} \right)}_{\textcircled{1}} \frac{e^{j\omega t}}{2j} - \underbrace{\frac{1}{1 + j\omega CR}}_{\textcircled{2}} \frac{e^{j\omega t}}{2j}$$

Note several observations

(A) For term ① $\frac{1}{1+pCR} \rightsquigarrow \frac{1}{1+j\omega CR}$

while term ② $\frac{1}{1+pCR} \rightsquigarrow \frac{1}{1-j\omega CR}$

That is substitute $p = \pm j\omega$
 for $e^{\pm j\omega t} \rightarrow$ very simple

(B) Term ② is just the complex conjugate of ①. Thus we need only solve for ①, we can always add term ② (superposition).

(c) When ① and ② are added the result is real. We can write the solution as

$$2 \operatorname{Re} \left(\frac{V}{1 + j\omega CR} \frac{e^{j\omega t}}{2j} \right)$$

The imaginary parts cancel.

(d) Since $\frac{1}{1 + j\omega CR}$ in polar notation is $\frac{1}{\sqrt{1 + (\omega CR)^2}} e^{-j \tan^{-1} \omega CR} = \varphi$

we can write the solution as

$$2 \operatorname{Re} \left(\frac{V}{\sqrt{1 + (\omega CR)^2}} \frac{e^{-j\varphi + j\omega t}}{2j} \right)$$

$$= \frac{V}{\sqrt{1 + (\omega CR)^2}} \sin(\omega t - \varphi) \quad \text{As before}$$

Conclusion: For sinusoidal (or cosinusoidal)

St. State response

- 1) Only use the $\frac{e^{j\omega t}}{2j}$ term (or $\frac{e^{j\omega t}}{2}$) for sin (or cosine) excitations
- 2) Use the p-operator technique with $p = j\omega$ to find responses
- 3) Take $2 \operatorname{Re}$ part of the complex term which results to obtain the real response