

# Text book Review

## Chapt 1 - reference directions

- power and energy  $P = v(t) i(t)$

phasor  $v(t) = \frac{V}{2} e^{j\omega t} + c.c.$

$V$  complex

$i(t) = \frac{I}{2} e^{j\omega t} + c.c.$

$I$  complex

$P = \frac{VI^*}{2} \rightarrow$  complex power - to handle energy stored (C and L)

Real  $P = \frac{VI^* + V^*I}{4} = \frac{|V||I|}{2} \cos(\angle V - \angle I)$

$j \text{Im } P = \left( \frac{VI^* - V^*I}{4} \right) = j(\text{reactive power flow})$

(e.g. capacitor  $= -j\omega C \frac{|V|^2}{2}$ )

energy  $\int_0^t v(t) i(t) dt$

$\frac{|V||I|}{2}$  Apparent power

- KCL + KVL

↑ conservation of charge      ↗ uniqueness of voltage



- Dependent voltage and current sources

- Resistors Resistance  $\propto$  length / (Area)

## Chapt 2 - Resistive Circuits. - Voltage Divider and Current Divider.

- Node & Mesh Analysis.

- Thevenin & Norton Equivalent (2.6)

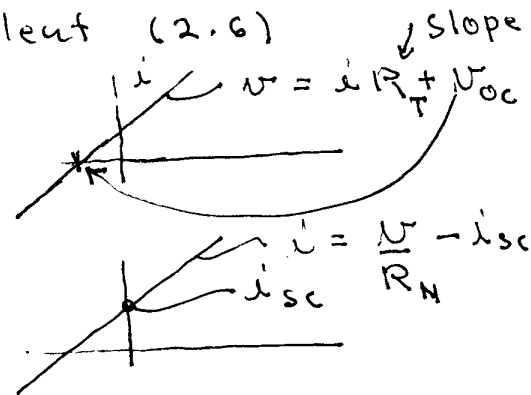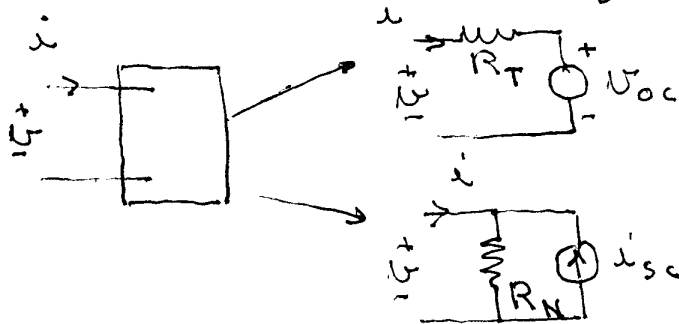

Equivalent: Thus  $R = R_N = R_{Th}$        $i_{sc} = \frac{v_{oc}}{R}$

- Can use the same logic for phasors and circuits having C's and L's

superposition

- Calculate response due to one source at a time
- Take care with dependent sources (must be considered for each independent source)
- Review wheatstone bridge

Solving several Simultaneous Equations

- Cramers Rule
- Flow Graph Procedure
- substitution

Chapt. 3 L + C

$i = C \frac{dV}{dt} = C p V$  ;  $V = L p i$  [  $q = e V$   
[flux =  $L i$ ] ]

for steady state sinusoid  $p = j\omega$  use only  $e^{+j\omega t}$  part of  $V$  and  $i$  and use superposition

stored energy  $\int_0^t V i dt$

e.g. inductor =  $\int_0^t L \frac{di}{dt} i dt = \frac{1}{2} L i(t)^2$


capacitor =  $\frac{1}{2} C V^2 = \frac{q^2}{2C}$



Area A

$C = \epsilon \frac{A}{t}$

$L = \mu N^2 \frac{A}{L}$  ← Area

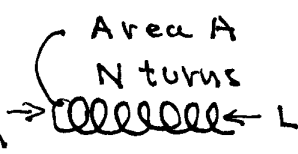


Mutual Inductance (3.7) for problem 4 PSet 6

Chapt 4 RC & RL Circuits - transients.

4.1 time constant RC - dimensional

$R/L \frac{[ \Omega ]}{[ H ]} = \frac{[ \Omega ]}{[ \text{volt} ] / [ \frac{\text{Amp}}{\text{sec}} ]} = [ \text{sec} ]$  argument

differential operator

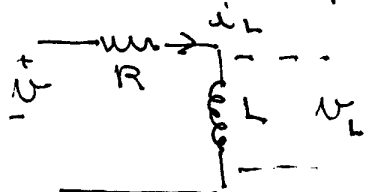

$V_L = \frac{pL}{pL + R} V$

$L \frac{dV_L}{dt} + R V_L = L \frac{dV}{dt}$

$\frac{dV_L}{dt} + \frac{R}{L} V_L = \frac{dV}{dt}$

e.g.  $i(0^-) = 1 \text{ Amp}$   
 $i(0^+) = 1 \text{ Amp}$

$V_L(0^+) = V(t=0^+) - i(0^+)R$

$V_L = \int_{0^+}^t \frac{dV}{dt} e^{-(t-t')R/L} dt'$  ← complementary

homogeneous →  $V_L(0^+) e^{-R/L t}$

1) D.C. Steady state -  $p = 0$  L - short C - open (3)

2) Initially  $\square$   $v = L p i$   $p \rightarrow \infty$  L open  
 $i = C p v$   $p \rightarrow \infty$  C short

Complementary solution - solution due to source (forced)

Homogeneous solution - natural solution (needed to satisfy initial conditions)

page 171 Transient solution of an RC circuit with sinusoidal source - includes transient and steady-state

4.5 (175) Second order circuits. - needs 2 initial conditions

critical-, under- and over-damped

Use  $p$ -operator to obtain D.E. - solve

Homogeneous + forced (complementary) solutions

can shorten calculations by using

$$\cos(j\omega t) = \cosh(\omega t)$$

$$\sin(j\omega t) = -j \sinh(\omega t)$$

Excitation with a constant source - page 180 go through 1 case!

Chapt 5 Phasors and Steady-State

Neglect 3 phase circuits

Phasors - Component of Fourier Series


$$v(t) = \frac{V}{2} e^{j\omega t} + c.c. \quad ; \quad V \text{ complex} \\ = |V| e^{j\angle V}$$

To analyze use  $r(p)$  - set  $p = j\omega$

$$\text{Argument: for } e^{j\omega t} \quad p(e^{j\omega t}) = j\omega e^{j\omega t} \\ \frac{1}{p}(e^{j\omega t}) = \frac{1}{j\omega} e^{j\omega t}$$

Thus  $p = j\omega$

Example

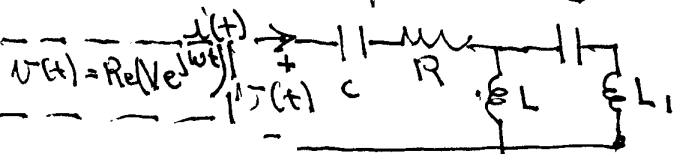

Find I

$$r(p) = \left( \frac{1}{pC} + R \right) \parallel \left( pL \parallel \left( \frac{1}{pC} + pL1 \right) \right)$$

Evaluate & set  $p = j\omega$

$$I(\omega) = V / r(j\omega) \triangleq V / Z(j\omega)$$

Chapt. 6 - Look at 6.1 and recall problem Set (4) 5 (Op Amp with Diodes) (only pages 270 and 271)

6.2. Low Pass Filter - Just RC Steady - State Analysis

skip 289 - 288

6.4 - 6.7 - Good Review of Steady - State Sinusoidal analysis

6.8 - Also from the point of view of steady - State analysis.

Chapter 7 - All

Note Synthesis - SOP's POS's

POS's take complement of Karnaugh map

$\overline{K}$	$\overline{A}$	$\overline{B}$	$\overline{C}$	$A$	$B$	$C$
	00	01	11	10		
$\overline{K}$	0	1	0	1		
complement	1	1	0	1	0	

$$\overline{K} = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}C + A\overline{B}\overline{C}$$

$$\therefore K = \overline{\overline{A}\overline{B}C} \overline{\overline{A}B\overline{C}} \overline{A\overline{B}C} \overline{A\overline{B}\overline{C}}$$

$$= (A+B+\overline{C})(A+\overline{B}+C)(\overline{A}+\overline{B}+\overline{C})(\overline{A}+B+C)$$

parallel in serial out shift register

ripple counter  
counter design  
state diagrams

Flip Flops  $\begin{cases} R, S \\ D \\ J, K \end{cases}$

clocked.


RS and the de-bounced switch as example

gates.


Chapt 8 - Forget

Chapt 9 - Forget

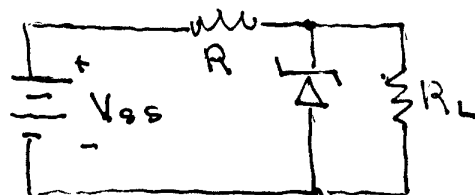
Chapt 10 - Diodes 10.3 Load Line Analysis of Zener Diode Circuit as example



Look for Thevenin Equivalent


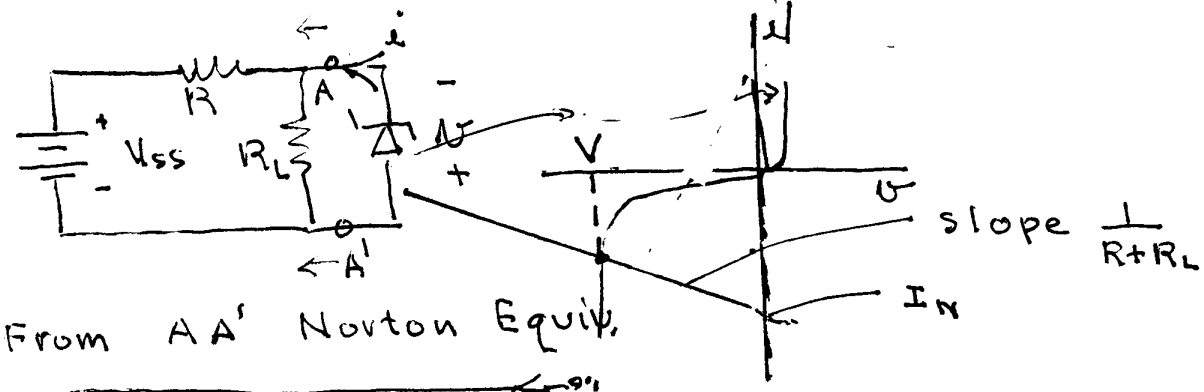


From AA' Norton Equiv.

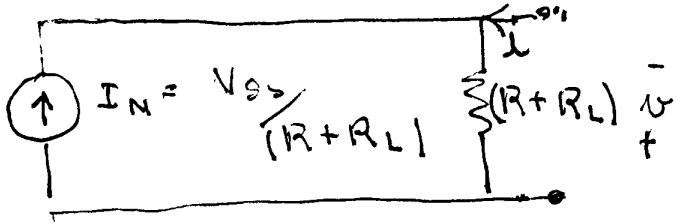

$$i = + \frac{V}{R + R_L} - I_N$$

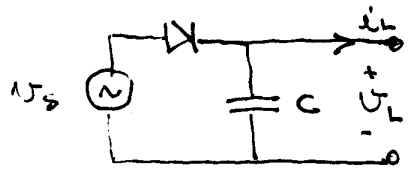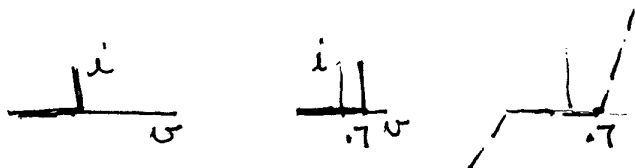- 10.4 - Ideal Diode
- 10.5 - Piece-wise Models
- 10.6 - Rectifier Models



During cap charging

$$V_L = \text{Re} \left( \frac{pC \parallel R_L}{pC \parallel R_L + R_s} V e^{j\omega t} \right)$$


$$= \text{Re} \frac{R_L}{R_L + R_s (1 + pCR_L)}$$

$$V_s = V \cos \omega t$$

$$\text{Thus } V_L = \text{Re} \left[ \frac{1/R_s}{1 + \frac{R_L + R_s}{R_s R_L} + pC} V e^{j\omega t} \right]$$

For  $R_L \gg R_s \approx \text{Re} \left( \frac{V}{R_s} e^{j\omega t} \right) \rightarrow$  so follows  $V_s(t)$

During cap discharging

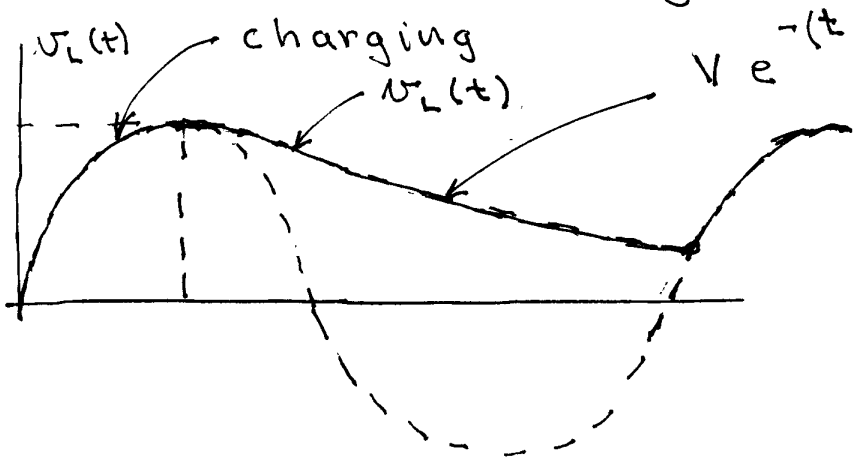

10.8 - small signal equivalent - Based on Taylor Expansion (6)  
 page 499 - recommended notation

$V_D$  = total instantaneous voltage

$V_{DQ}$  = Expansion point (d.c. quiescent voltage)

$v_d = (V_D - V_{DQ})$  - Taylor expansion variable  
 $= \Delta V_D$

Uses diode as example

$$\begin{aligned}
 i_D &= I_s (e^{V_D/V_T} - 1) \\
 &= I_s (e^{(V_{DQ} + v_d)/V_T} - 1) \\
 &\approx \underbrace{I_s (e^{V_{DQ}/V_T} - 1)}_{I_{DQ}} + \underbrace{I_s e^{V_{DQ}/V_T} \frac{v_d}{V_T}}_{i_d} \rightarrow \text{so } i_d = v_d / r_d \\
 &= I_{DQ} + i_d
 \end{aligned}$$

Ignore voltage controlled attenuator (page 500)  $r_d = \frac{V_T}{I_{DQ}}$

## Chapt 11 - Amplifiers

11.1 - 11.3 Basic - Dependent Sources

Ignore 11.8 - end just realize two voltage sum  
 can be written as  $v_1 + v_2 = v(t)$

$$\begin{aligned}
 v_1 &= \underbrace{\frac{v_1 + v_2}{2}}_{\text{Common mode}} + \underbrace{\frac{v_1 - v_2}{2}}_{\text{differential mode (Operational Amplifier)}} \\
 v_2 &= \underbrace{\frac{v_1 + v_2}{2}} - \underbrace{\frac{v_1 - v_2}{2}}
 \end{aligned}$$

## Chapt 12 - FET's

12.1 - 12.5

12.7 CMOS Inverter NAND Gate NOR Gate

## Chapt 13 - BJT's

Active Region, Cut-off, Saturation

Emitter Followers and Common Emitter


Amplifiers as examples of dependent sources

Small signal - base-emitter a pn junction

$$i_b = (r_b)^{-1} v_{be} \quad r_b = \frac{V_T}{I_{BQ}}$$

Since  $i_c = \beta i_b$   $\Delta i_c = i_c = \beta \Delta i_b = \beta i_b$

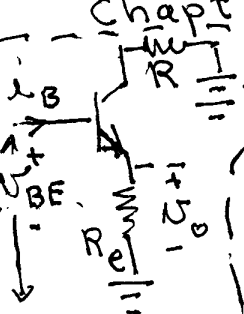so  $i_c = (\frac{\beta}{r_b}) v_{be}$  - Voltage controlled current source



$v_o \approx v_{BE}$   
 Emitter Follower

## Chapt 14

Neglect 14.5 - 14.7, 14.10 (Active Filters)  
except for problem set 5 - RC filter

Appendix A - complex numbers

For Final General Comments

- a) Review Problem Sets
- b) Review Midterms
- c) Final Covers the full course
- d) One or two problems will be modified  
Midterm 1 or 2 problems
- e) There will be six problems

General Areas Thus:

Chapt 1 KVL KCL, power

Chapt 2 Resistive circuits Thevenin & Norton

Chapt 3, 4 L, C, RC & RL transients

Chapt 5 "Phasors" + steady state - (complex numbers)

Chapt 6 From point of view of  $I_q - I_q$  plot and

phasors (sinusoidal analysis) [If  
Bode plot asked for it would be couched in  
terms of logs - Review LTspice RC frequency  
behavior problem - problem set 3]

Chapt 7 Logic design

Chapt 10 Diode - Ideal Piecewise linear. Zener  
diode discussion - good review of load line.  
Page 5 of these notes for Rectifier problem  
with capacitor

Chapt 11 Amplifiers

Chapt 12 FET CMOS Inverter

Chapt 13 BJT's