

Realistic Amplifiers Common Mode Rejection

① U_1 has a different Amplification factor from U_2



Thus $U_o = (A_1 U_1 - A_2 U_2)$ rather than $A(U_1 - U_2)$

$$= A_1 \left(\frac{U_1 - U_2}{2} + \frac{U_1 + U_2}{2} \right) + A_2 \left(+ \left(\frac{U_1 - U_2}{2} \right) - \left(\frac{U_1 + U_2}{2} \right) \right)$$

$$\underline{U_1 - U_2} = U_{dit} \quad ; \quad \underline{U_1 + U_2} = U_{cm}$$

$$U_o = \underbrace{\left(\frac{A_1 + A_2}{2} \right)}_{\text{Differential Mode Amplification}} U_{dit} + \underbrace{(A_1 - A_2)}_{\text{Common Mode Amplification}} U_{cm}$$

$= A_d U_{dit} \quad \quad A_{cm} U_{cm}$

Common mode rejection ratio

$$CMRR = 20 \log \left| \frac{A_d - 1}{A_{cm} - 1} \right| \quad (\text{page 559})$$

Example page 554 Electro cardiograph

$$A_d = 1000$$

$$U_{dit} = 1 \text{ mV} \quad U_{cm} = 100 \text{ V} \quad (60 \text{ Hz})$$

output of cm to be 1% of dit, thus

$$\bullet 0.01 \text{ mV} \times 1000 = 10 \text{ mV} = 10^{-2} \text{ V. Thus } A_{cm} = \frac{10^{-2} \text{ V}}{100 \text{ V}}$$

$$= 10^{-4}$$

$$CMRR = 20 \log \frac{1000}{10^{-4}} = 20 \times 7 = 140 \text{ dB}$$