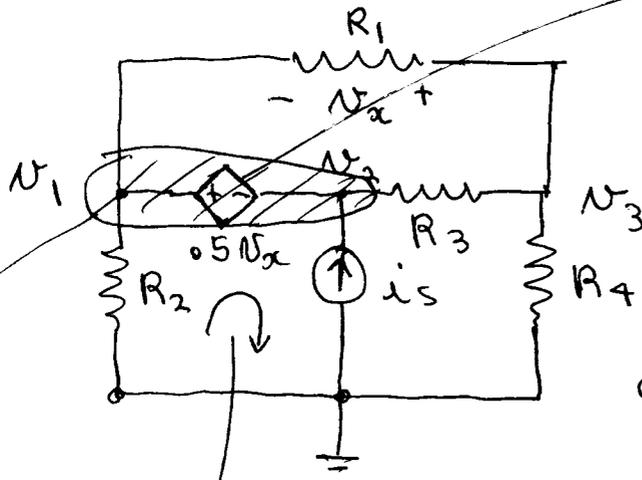


# Example 2.10 Node-Voltage with a dependent voltage source



dependent source

① Note that  
 $-U_x = (U_1 - U_3)$   
 $U_x$  is a branch voltage.

Thus once  $U_1$  &  $U_3$  are known  $U_x$  is known


Analysis basically the same as previously

KVL (a)  $U_2 = U_1 - 0.5(U_3 - U_1)$  ①  
 $= \frac{3}{2}U_1 - 0.5U_3$

KCL  $\rightarrow \frac{U_1}{R_2} + \frac{U_2 - U_3}{R_3} - i_s = 0$  ②  
 write as (b)  $U_1 \left( \frac{1}{R_2} \right) = -\frac{U_2}{R_3} + \frac{U_3}{R_3} + i_s$   
 eliminate  $U_2$

KCL at ③  $\frac{U_3}{R_4} + \frac{(U_3 - U_2)}{R_3} + \frac{(U_3 - U_1)}{R_1} = 0$

or

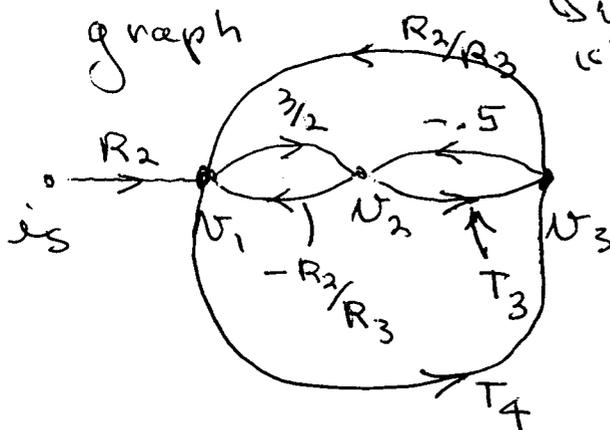

(c)  $U_3 \left( \frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_1} \right) - \frac{U_2}{R_3} - \frac{U_1}{R_1} = 0$

$$T_3 = \frac{1/R_3}{1/R_4 + 1/R_3 + 1/R_1}$$

$$T_4 = \frac{1/R_1}{1/R_4 + 1/R_3 + 1/R_1}$$

$$U_3 = \frac{(T_4 R_2 + R_2 (\frac{3}{2}) T_3)}{1 - R_2/R_3 T_4 + \frac{3}{2} R_2/R_3 + 0.5 T_3 - 0.5 R_2/R_3 T_4 - \frac{3}{2} R_2/R_3 T_3}$$

Check Using Cramers Rule

(2)

$$\textcircled{1} \quad v_3 = T_3 v_2 + T_4 v_1$$

$$\textcircled{2} \quad v_1 = -\frac{R_2}{R_3} v_2 + \frac{R_2}{R_3} v_3 + i_s R_2$$

$$\textcircled{3} \quad v_2 = \frac{3}{2} v_1 - 0.5 v_3$$

$$\begin{vmatrix} -T_4 & -T_3 & 1 \\ -1 & -\frac{R_2}{R_3} & -\frac{R_2}{R_3} \\ -\frac{3}{2} & 1 & 0.5 \end{vmatrix} \begin{vmatrix} v_1 \\ v_2 \\ v_3 \end{vmatrix} = \begin{vmatrix} 0 \\ i_s R_2 \\ 0 \end{vmatrix}$$

$$\Delta = -T_4 \left( \frac{R_2}{R_3} \times \frac{1}{2} + \frac{R_2}{R_3} \right) + T_3 \left( 0.5 - \frac{3}{2} \frac{R_2}{R_3} \right) + \left( 1 + \frac{3}{2} \frac{R_2}{R_3} \right)$$

$$\text{For } v_3 \quad \Delta_{23} = +T_4 + \frac{3}{2} T_3$$

Note

If one wants voltages KCL and Branch Relations are preferred

KCL gives currents which are expressed in terms of voltages with Branch relations

For currents KVL is favorable which with Branch relations yields currents