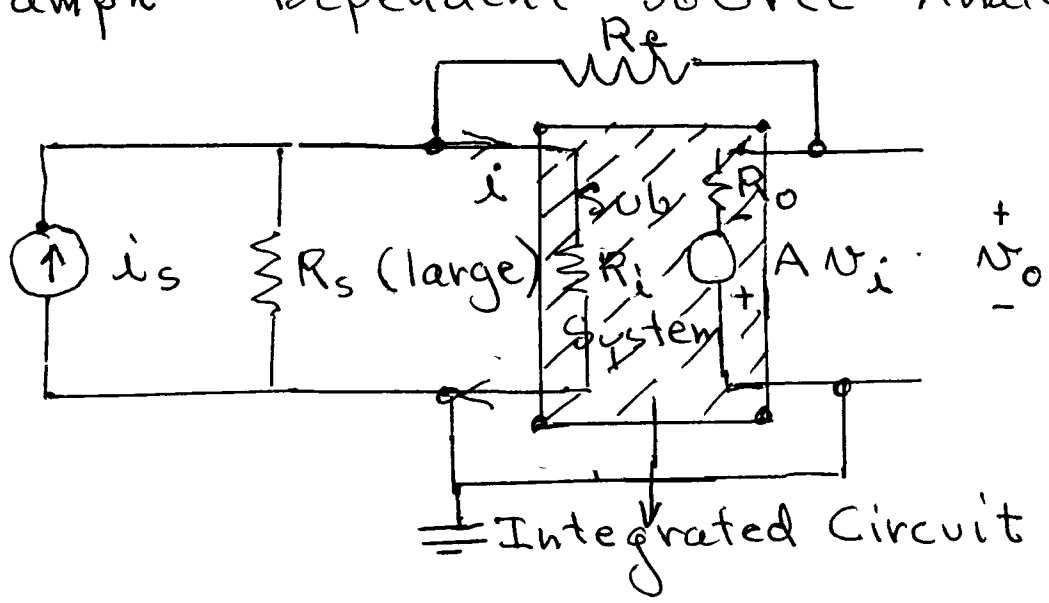



Many of the book exercises are exercises in algebra.

Many applications minimize algebra because one wishes to isolate the influence of one part of an overall circuit on another. The analysis can be broken into sub-analysis which are much simpler.

Example Dependent Source Analysis



Circuit

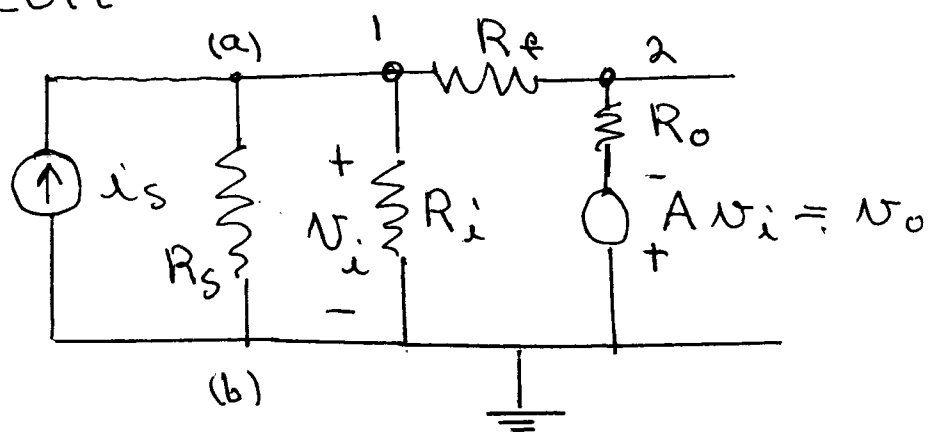

Ans ? $V_o \approx -R_f i_s$ (4)

The sub-circuit disappears

Node ①

$$\textcircled{1} \quad V_i \left(\frac{1}{R_i} + \frac{1}{R_s} \right) + \frac{V_i - V_o}{R_f} = +i_s$$

Node ②

$$\textcircled{2} \quad \frac{V_o + A V_i}{R_o} + \frac{V_o - V_i}{R_f} = 0$$

$$\textcircled{1} \quad V_i \left(\frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f} \right) = +i_s + \frac{V_o}{R_f}$$

sub in ②

$$V_o \left(\frac{1}{R_o} + \frac{1}{R_f} \right) + \left(\frac{A}{R_o} - \frac{1}{R_f} \right) \left(+i_s + \frac{V_o}{R_f} \right)$$

$$\frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f}$$

= 0

$$V_o \left(\frac{1}{R_o} + \frac{1}{R_f} + \frac{1}{R_f} \left(\frac{A-1}{R_o R_f} \right) \frac{1}{\frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f}} \right) + \left(\frac{A-1}{R_o R_f} \right) \frac{i_s}{\frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f}} = 0$$

When $A \rightarrow \infty$

$$\frac{V_o}{R_f} = -i_s$$

as above

"Feed back" Picture with Flow Graphs

Two node equations are:

$$\frac{V_o + AV_i}{R_o} + \frac{V_o - V_i}{R_f} = 0$$


$$\frac{V_i}{R_i} + \frac{V_i}{R_s} - i_s + \frac{V_i - V_o}{R_f} = 0$$

Unknowns V_i and V_o known i_s
 rewrite these as

$$V_i = \frac{\left(\frac{1}{R_o} + \frac{1}{R_f}\right) V_o}{\frac{1}{R_f} - \frac{A}{R_o}}$$

$$V_o = R_f \left(\frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f} \right) V_i - R_f i_s$$

Graph

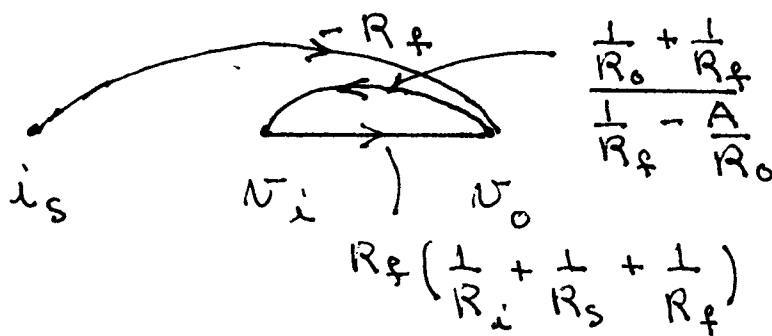

$$V_o = \frac{-R_f i_s}{1 - \frac{R_f \left(\frac{1}{R_o} + \frac{1}{R_f} \right) \left(\frac{1}{R_i} + \frac{1}{R_s} + \frac{1}{R_f} \right)}{\frac{1}{R_f} - \frac{A}{R_o}} \quad (1)$$

1 - "Feedback"

Ideal Operational Amplifier Conditions

① Input Resistance $R_i \rightarrow \infty$ (gigaohms can be realized in practice)

② $A \rightarrow \infty$ A in excess of 10^6 can be realized

③ Virtual short ($V_i \rightarrow 0$). Note, however since $R_i \rightarrow \infty$ the current is very small


The argument for $V_i \rightarrow 0$

We showed that when $A \rightarrow \infty$


$$V_o / R_f = -i_s$$

so $V_i = V_o / A = -i_s R_f / A \rightarrow 0$ (Summing Point Constraint)

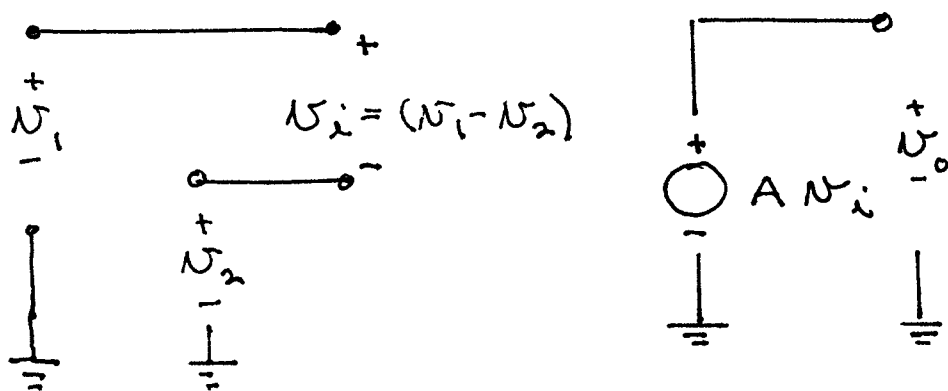Results in Ideal Op-Amp picture of Fig 14.2




Ideal

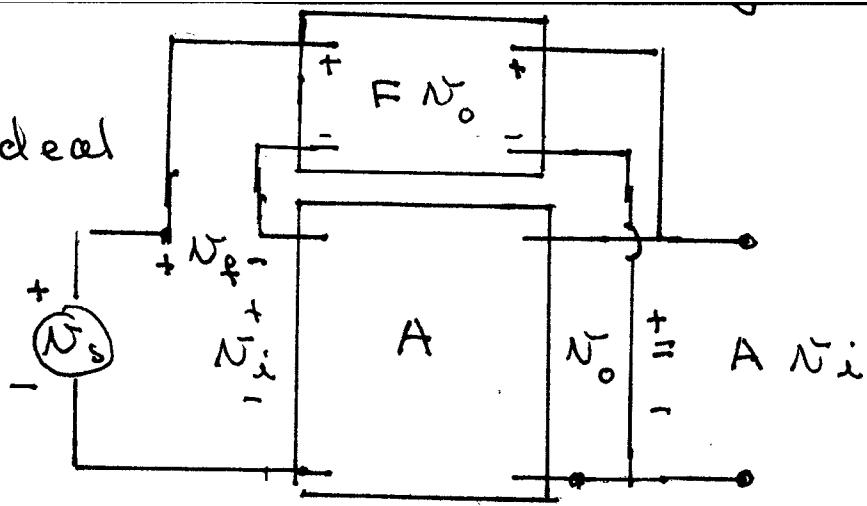

$$U_i = U_s - U_f$$

$$U_f = F U_o$$

$$U_o = A U_i = A (U_s - U_f)$$

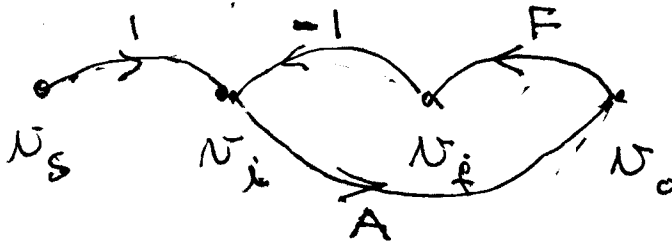

$$U_o = \frac{A U_s}{1 + AF}$$

Negative
Feedback



U_f in opposition to U_s

Current Feedback

$$i = i_s + i_f$$

$$V_o = A(R_i i) = (A R_i) i$$

$$i_f \approx V_o / R_f$$

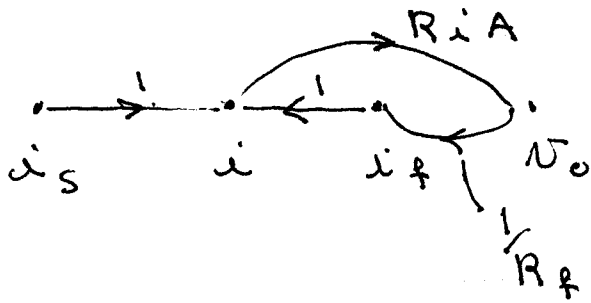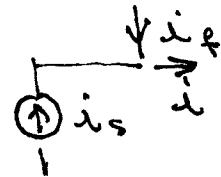

$$\therefore V_o = \frac{R_i A}{1 - \frac{R_i A}{R_f}}$$

← feed back equation
positive feedback

Ideal Picture

