

Ideal Operational Amplifier Conditions

① Input Resistance $R_i \rightarrow \infty$ (gigaohms can be realized in practice)

② $A \rightarrow \infty$ A in excess of 10^6 can be realized

③ Virtual short ($V_i \rightarrow 0$). Note, however since $R_i \rightarrow \infty$ the current is very small


The argument for $V_i \rightarrow 0$

We showed that when $A \rightarrow \infty$

$$V_o / R_f = -i_s$$

so $V_i = V_o / A = -i_s R_f / A \rightarrow 0$ (Summing Point Constraint)

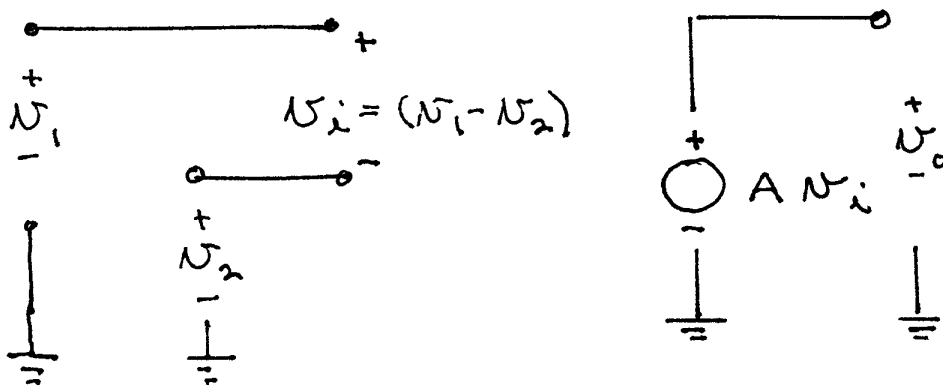
Results in Ideal Op-Amp picture of Fig 14.2



Example Op-Amp Circuits

Summing Amplifier

Equivalent Circuit

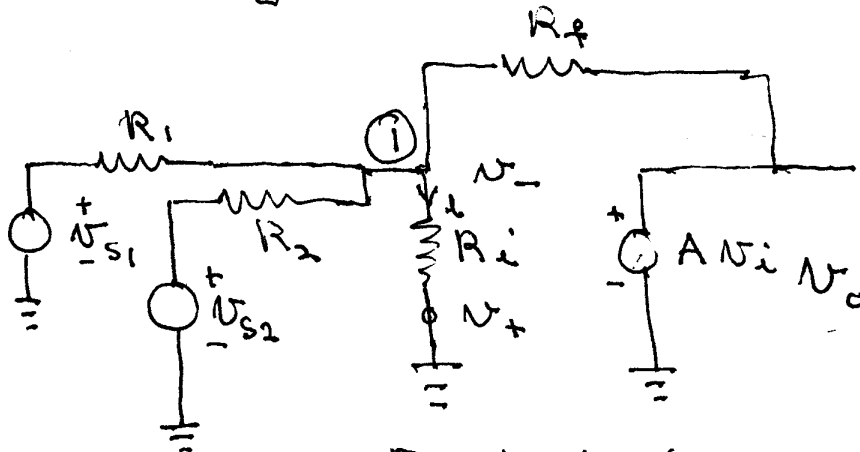

Equivalent Circuit


- Find V_o
- Take Limit as $A \rightarrow \infty$
 - $R_i \rightarrow \infty$
 - $V_+ \rightarrow V_-$
 - $i \rightarrow 0$

Then

KCL at ①


$$\frac{V_{s1}}{R_1} + \frac{V_{s2}}{R_2} = -\frac{V_o}{R_f}$$
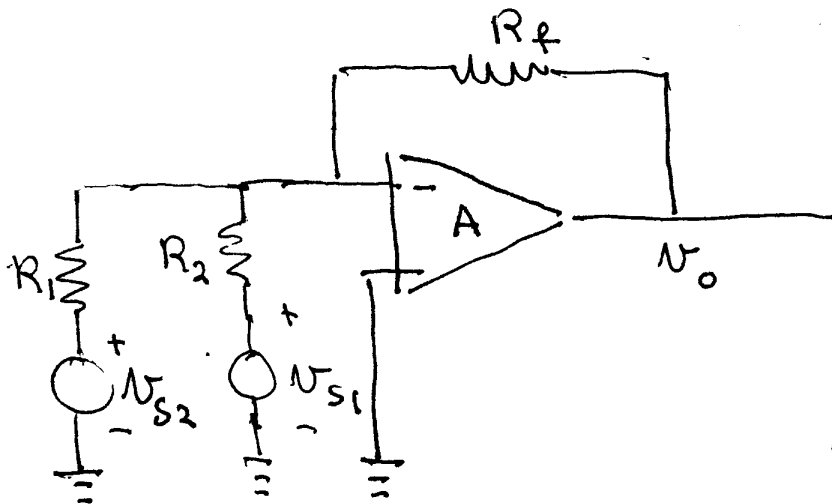
$$\text{or } V_o = -R_f \left(\frac{V_{s1}}{R_1} + \frac{V_{s2}}{R_2} \right)$$



Summing Circuit

Non inverting Amplifier

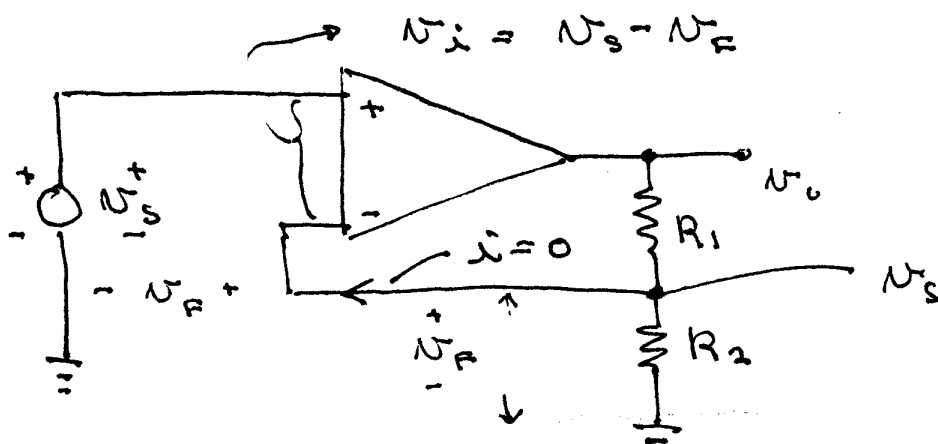

Ideal Op Amp $V_- = V_+ = V_s$

$$\text{But } V_s = \frac{R_2}{R_1 + R_2} V_o$$

$$\therefore V_o = \left(\frac{R_1 + R_2}{R_2} \right) V_s$$

Feedback Equations,

$$V_i = V_s - V_F$$


$$V_o = A V_i$$

$$V_F = V_s = \frac{R_2}{R_2 + R_1} V_o = F V_o$$


$$\therefore V_o = A V_i = A (V_s - V_F) \\ = A (V_s - F V_o)$$

$$\therefore V_o = \frac{A V_s}{1 + A F} \quad \text{negative feedback.}$$

Differential Amplifier - Examples

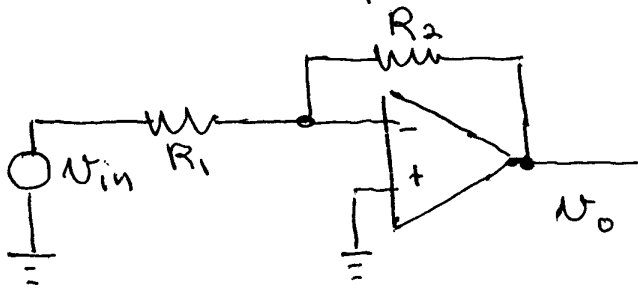
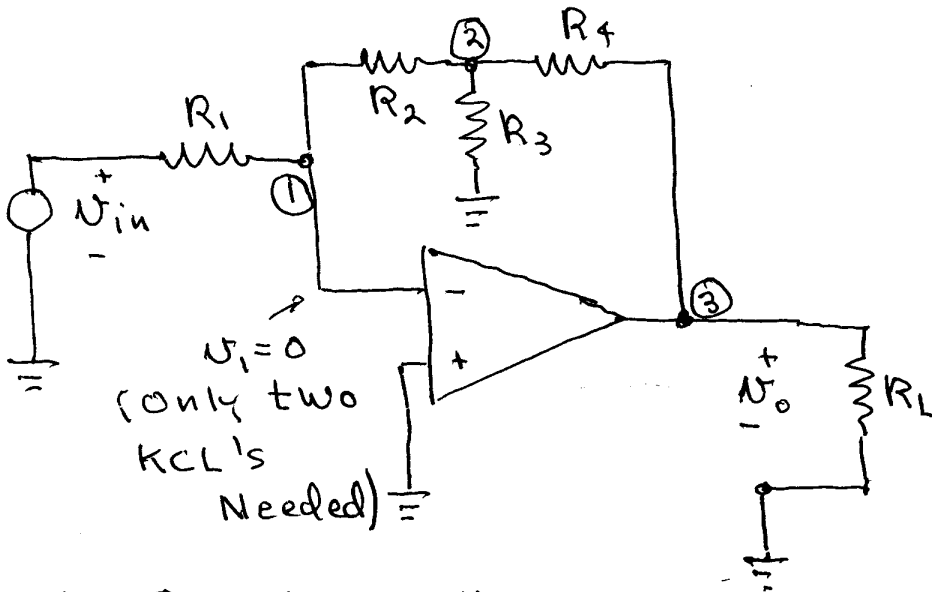
$$\frac{U_o}{R_2} = - \frac{U_{in}}{R_1}$$




Node ① $\frac{U_{in}}{R_1} + \frac{U_2}{R_2} = 0$

② $U_2 \left(\frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_4} \right) - \frac{U_o}{R_4} = 0$


Thus $-\frac{R_2}{R_1} \left(\frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_4} \right) = \frac{U_o}{R_4}$

Voltage Follower

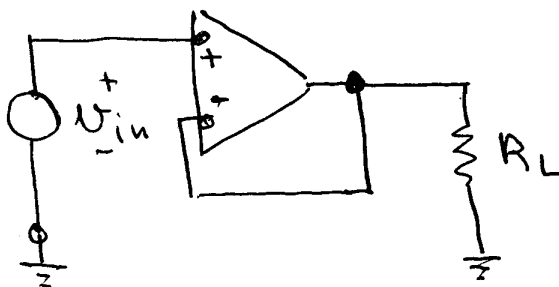


U_- forced to be U_o
 But $U_- \neq U_{in}$
 Thus $U_o = U_{in}$

Subtracting Amplifier.

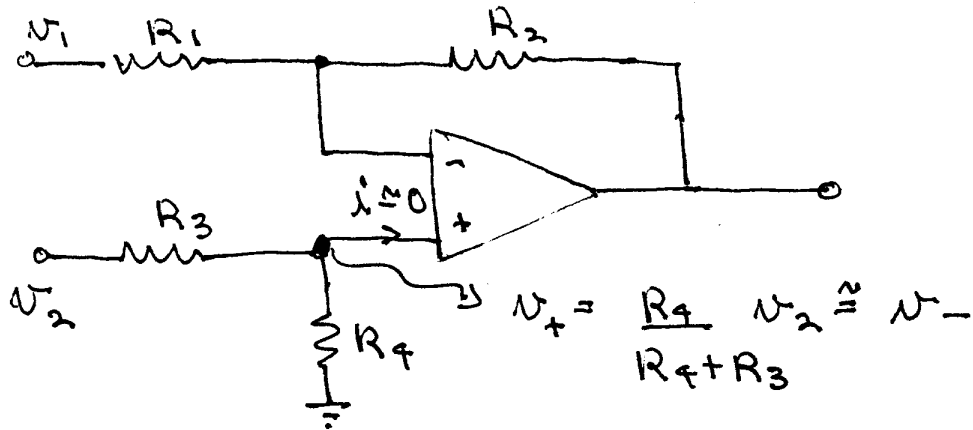

$$\therefore \frac{U_1}{R_1} - \frac{R_4}{R_1(R_4 + R_3)} U_2 = -\frac{U_o}{R_2}$$

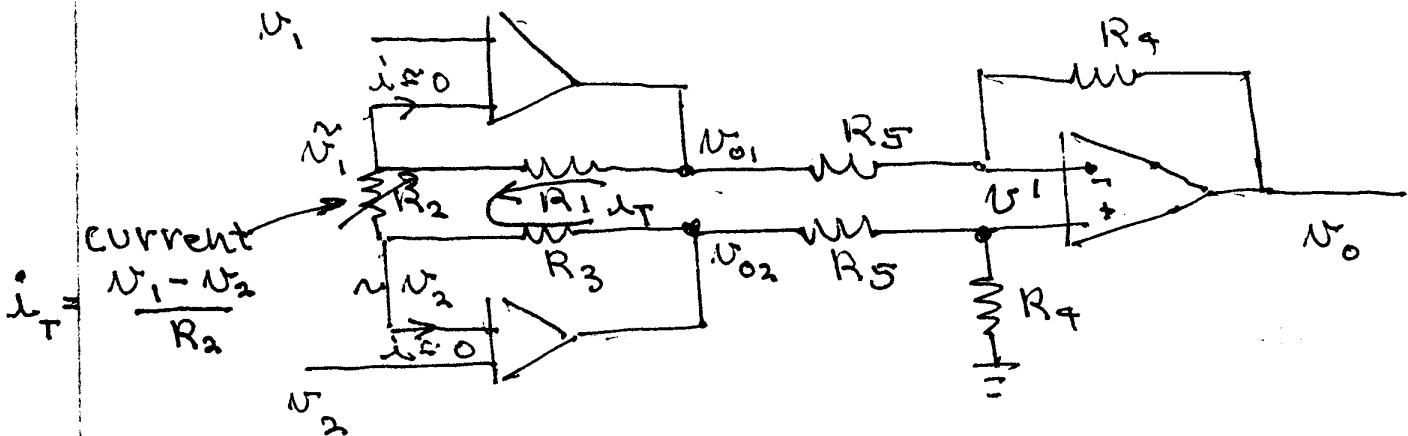Sensor Circuit (sense when $U_1 \neq U_2$)



$$\begin{aligned} \therefore U_{o1} &= U_1 + i_T R_1 \\ U_{o2} &= U_2 - i_T R_3 \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \begin{aligned} (U_{o2} - U_{o1}) &= U_2 - U_1 \\ &+ i_T (R_3 + R_1) \\ &= \frac{(U_2 - U_1) (1 + R_3 + R_1)}{R_2} \end{aligned}$$

$$\frac{U_o - U^1}{R_4} = -\frac{U_{o1} - U^1}{R_5} ;$$

$$U^1 = \frac{R_4}{R_4 + R_5} U_{o2}$$


$$\begin{aligned} \frac{V_o}{R_4} + \frac{V_{o1}}{R_5} &= \frac{R_4}{R_4 + R_5} V_{o2} \left(\frac{1}{R_4} + \frac{1}{R_5} \right) \\ &= \frac{R_4}{R_4 + R_5} V_{o2} \frac{(R_4 + R_5)}{R_4 R_5} \end{aligned}$$

$$-V_o = -\frac{R_4}{R_5} (V_{o2} - V_{o1})$$

$$V_o = -\frac{R_4}{R_5} \left(1 + \frac{R_3 + R_1}{R_2} \right) (V_2 - V_1)$$

Set $R_4 = R_5 = R_3 = R_1$ R_2 is gain control,

Simple DAC

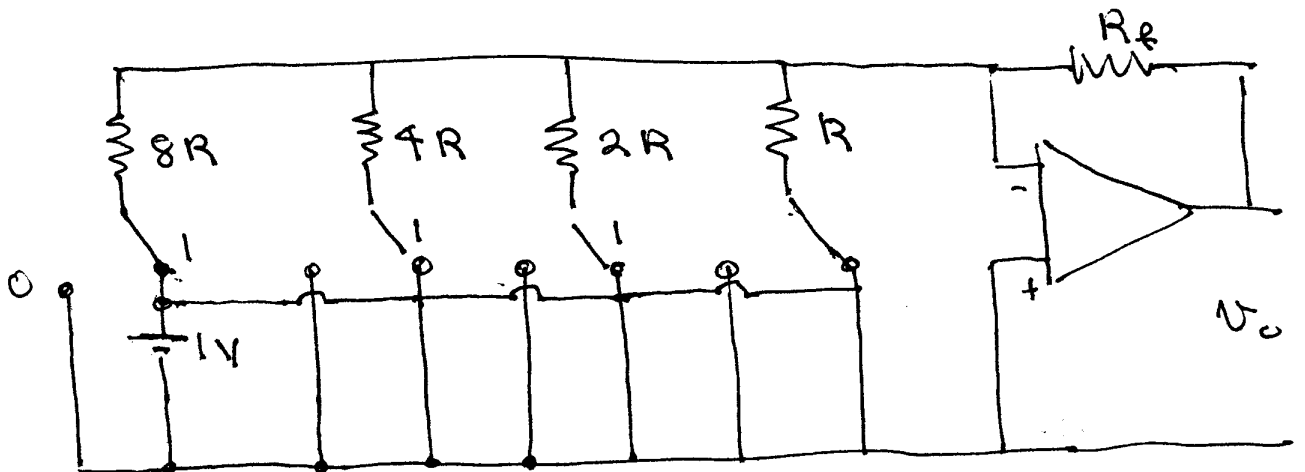

$$\begin{aligned} V_o &= -\frac{R_f}{R} \left(V_1 + \frac{1}{2}V_2 + \frac{1}{4}V_3 + \frac{1}{8}V_4 \right) \\ &= -\frac{R_f}{8R} (8V_1 + 4V_2 + 2V_3 + V_4) \end{aligned}$$