

Op - Amps Saturation Region


$$i_- = 0$$

+ Saturation


$$i_+ = 0$$

$$V_o = E_{set}$$

$$V_d = V_+ - V_- > 0$$

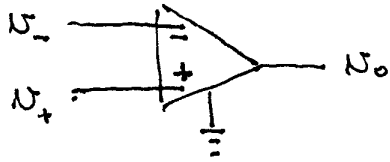

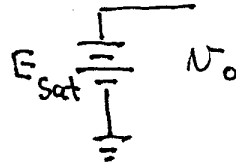
$$\begin{array}{l} \underline{V_- = 0} \\ V_d > 0 \\ \underline{V_+ = 0} \end{array}$$




$$V_d = V_+ - V_- < 0$$

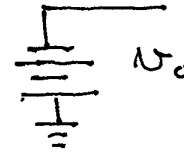
$$\begin{array}{l} \underline{V_- = 0} \\ V_d < 0 \\ \underline{V_+ = 0} \end{array}$$



$$-E_{sat} < V_o(t) < E_{sat}$$


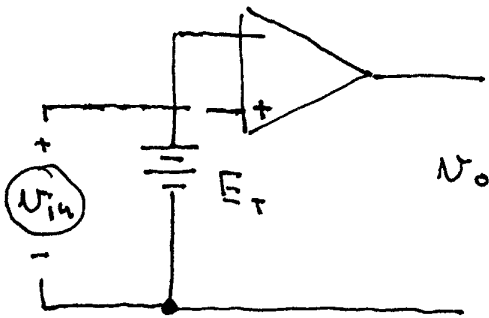


Unless $V_{in} = E_T$
saturation occurs!

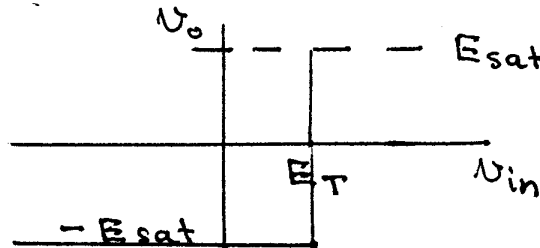

Comparator

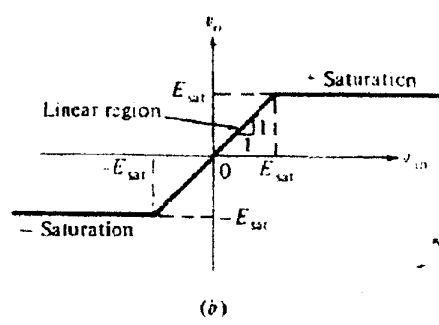
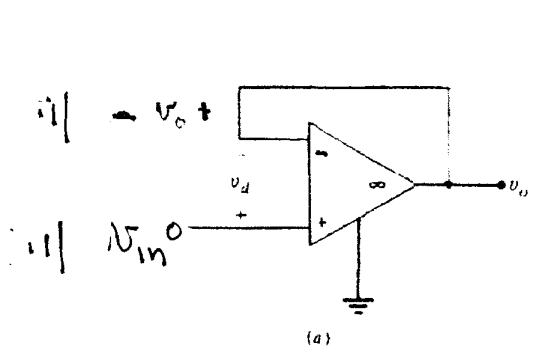
Positive and Negative Feedback and Saturation



$$\begin{aligned}
 v_o &= v_o \\
 v_d &= v_{in} - v_o \\
 v_o &= A v_d \\
 &= A(v_{in} - v_o) \\
 v_o &= \frac{A v_{in}}{1 + A}
 \end{aligned}$$

negative feedback

Figure 3.5 (a) A negative feedback circuit and (b) its transfer characteristic.

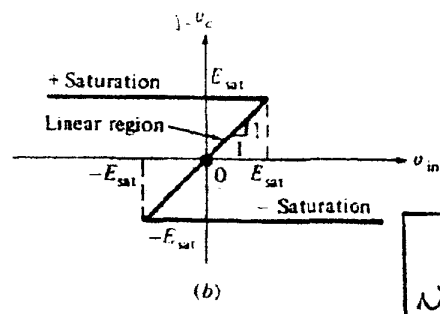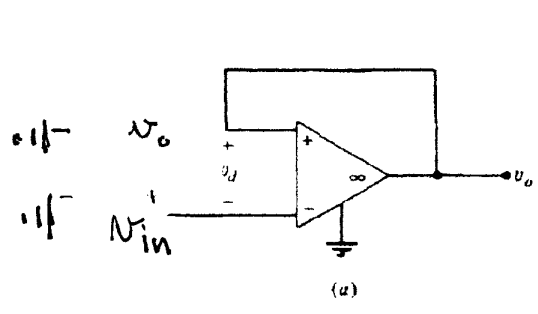

$$\begin{aligned}
 v_o &= v_o \\
 v_d &= v_o - v_{in} \\
 v_o &= A(v_o - v_{in}) \\
 v_o(1 - A) &= -A v_{in} \\
 v_o &= -\frac{A v_{in}}{1 - A}
 \end{aligned}$$


positive feedback

Figure 3.6 (a) A positive feedback circuit and (b) its transfer characteristic.




For Fig 3.6

- ① when saturated with $v_{in} = E_{sat} = v_o$
- ② $v_o = +E_{sat}$ but when $v_{in} > E_{sat}$
- ③ v_d becomes negative so v_o switches to $-E_{sat} = v_o^-$
- ④ But Now Op amp is saturated until $v_{in} < -E_{sat}$ and then it must switch to $+E_{sat}$

This gives bi-stable behavior

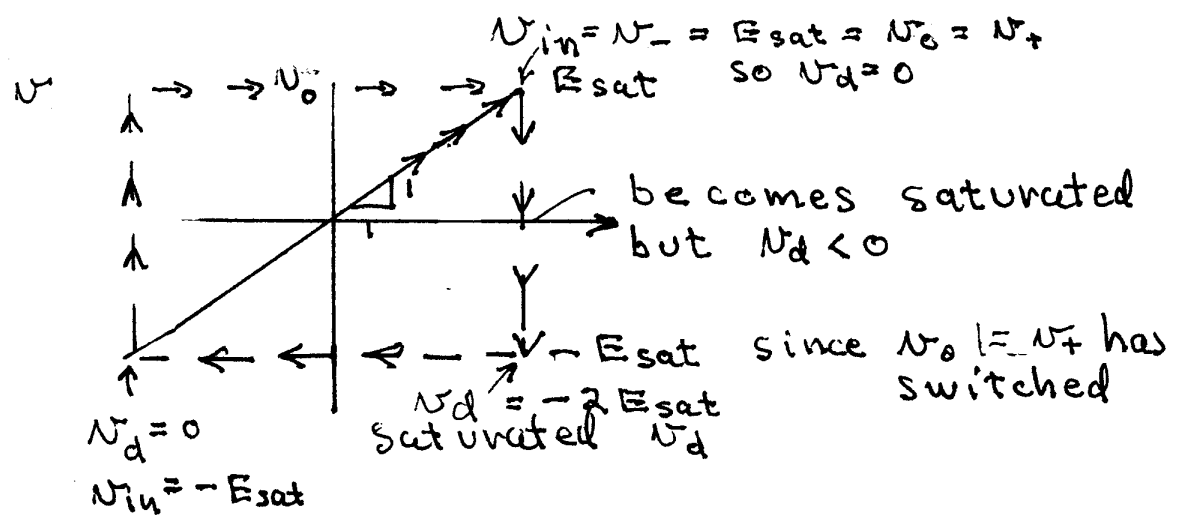

Bistable behavior

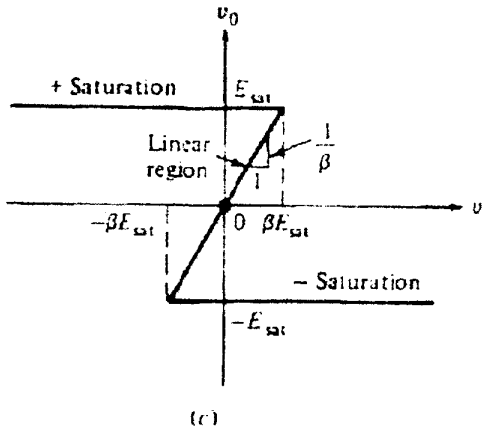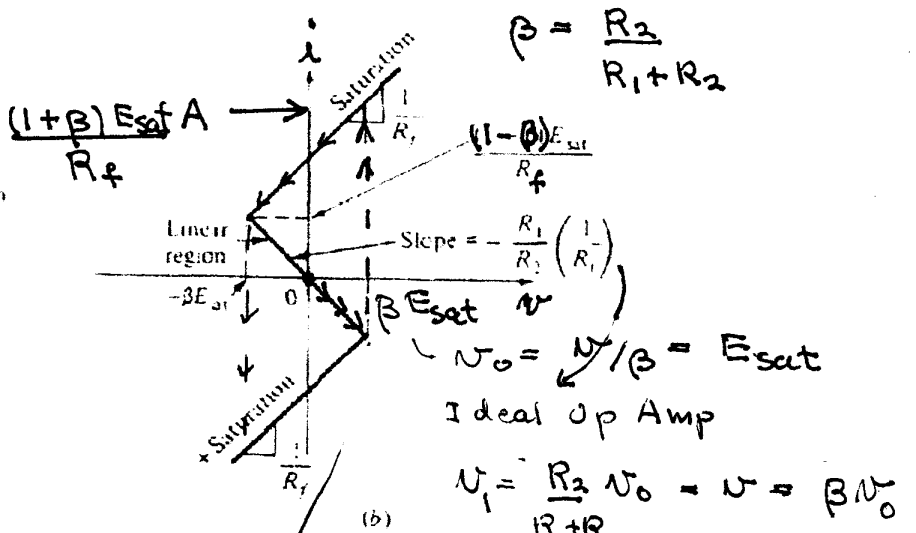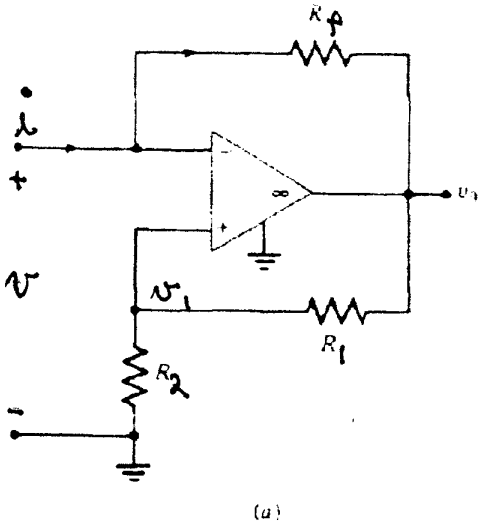


$\frac{v_o - v_i}{R_f} = -i$ sub for v_o
 $\frac{R_1}{R_2} \frac{v}{R_f} = -i$

at this point $v = v_i = \beta v_o$
 just the edge of sat
 for $v > \beta E_{sat}$ $N_+ - N_-$ is < 0

Thus the equivalent

Figure 3.8 A negative-resistance converter and its driving-point and transfer characteristics. Here, $\beta \triangleq R_2 / (R_1 + R_2)$.

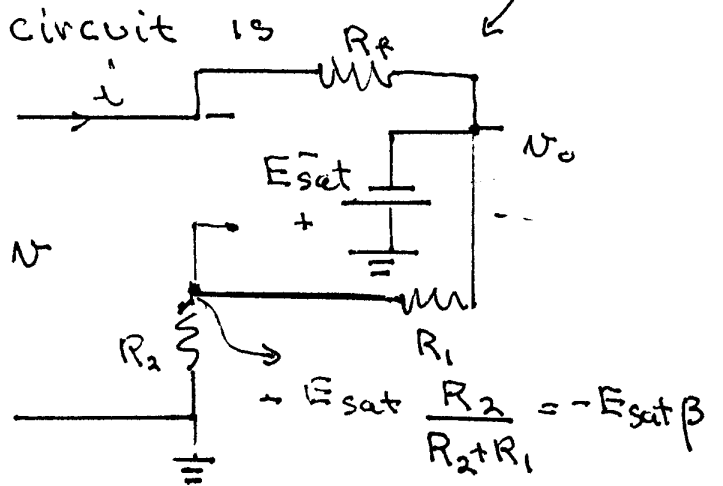

$i = \frac{v + E_{sat}}{R_f} = \frac{\beta E_{sat} + E_{sat}}{R_f}$
 at point A