

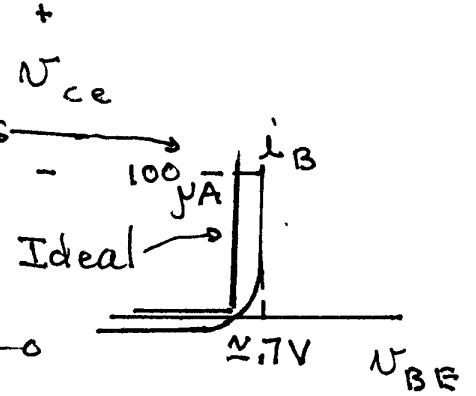
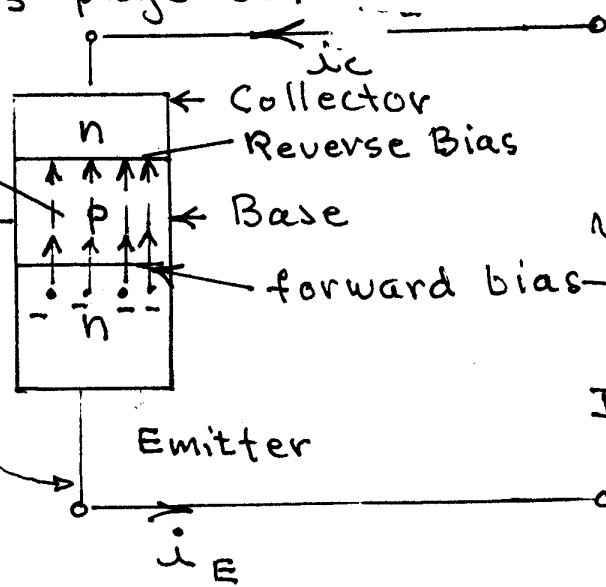


This is a Diffusion process
 Most of the electrons reach the Collector Diode

$V_{be} > 0$
 $\approx 0.7V$

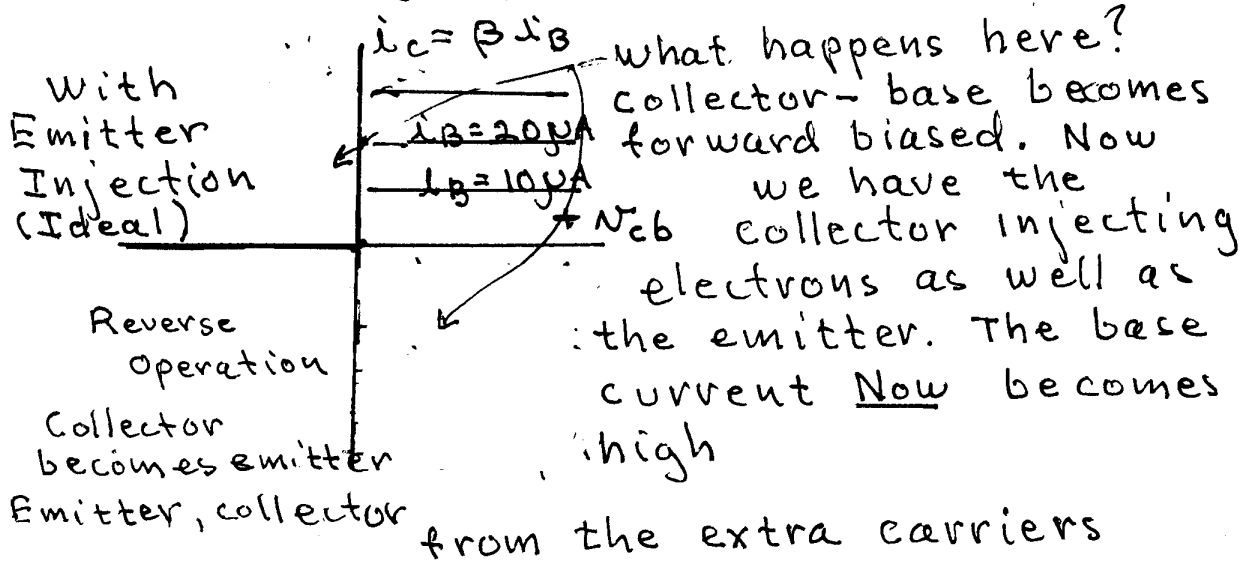


collector Diode

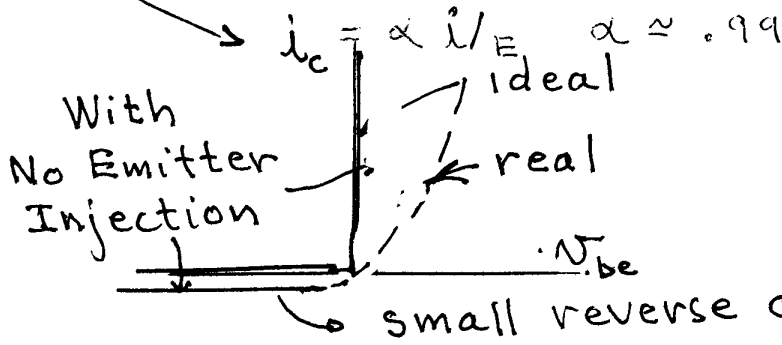

The base current is the recombination current of the electrons on their way to the collector

Bipolar Ebers-Moll Model

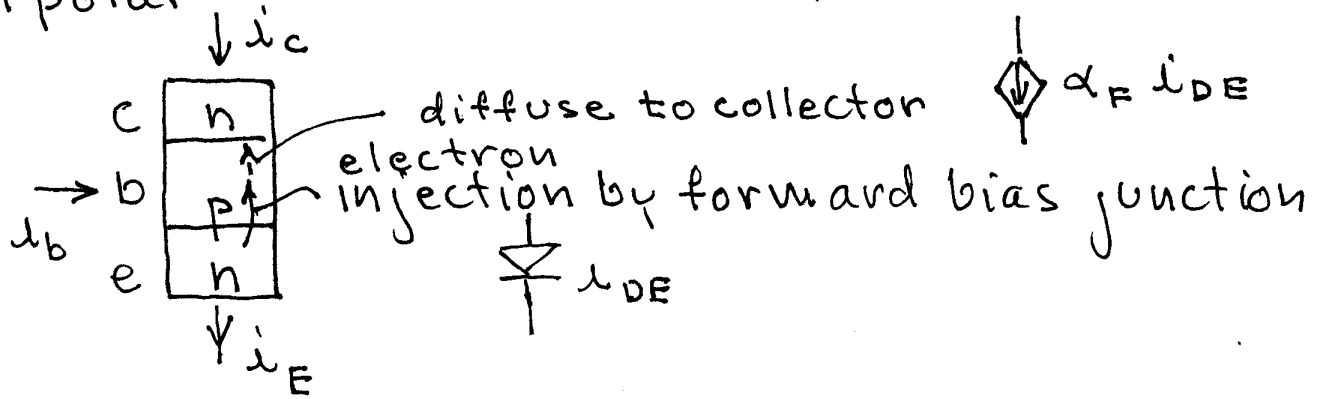

In forward active mode collector is reversed bias (+ potential). Thus collector "attracts" electrons diffusing across the base (when they reach the collector-base depletion region)

The $(1 - \alpha_F) i_{DE}$ electrons combine with base holes supplied by i_b

Thus $i_c = \alpha_F i_E$


$i_b = (1 - \alpha_F) i_E$

and thus also

$$i_c = \frac{\alpha_F}{(1 - \alpha_F)} i_b = \beta i_b$$

Since $\alpha_F \approx .9$ or greater β is large i_b is small.

Example: Current mirror

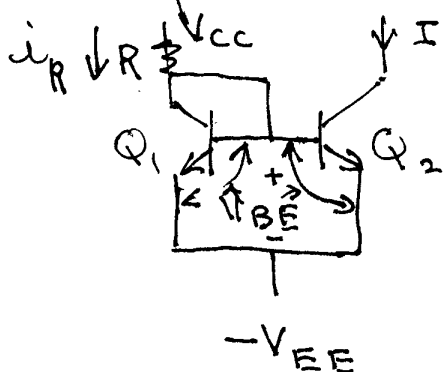

$$I = \frac{V_{CC} - (-V_{EE}) - V_{BE}}{R}$$

Since V_{BE} 's are same

I_c 's are same

Thus $I = I_R$ ($I_B \approx 0$)