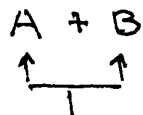



# Binary Adder.



to produce S a sum plus K the carry!

## Truth Table


A	B	C	S	K
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

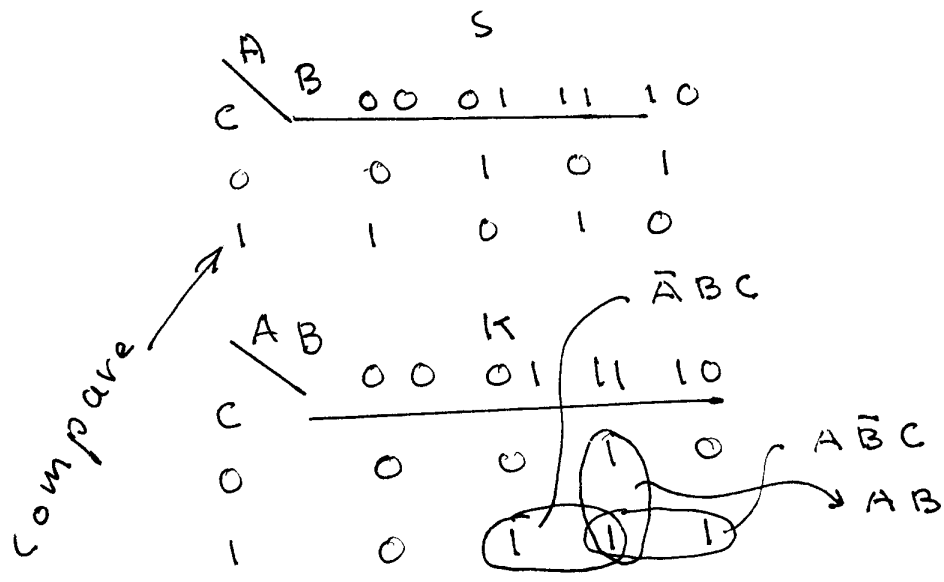

$$K = AB + CA + BC$$

$$S = (\bar{A}B + A\bar{B})\bar{C} + (\bar{A}\bar{B} + AB)C$$

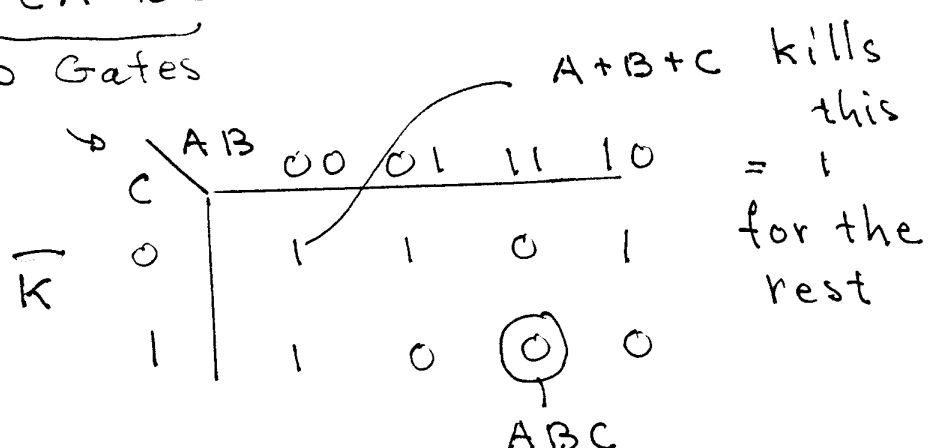
Note  $\bar{K} = \overline{ABCA BC}$   
NAND Gates



$$S = ABC + (A+B+C)\bar{K}$$

$$= \overline{\overline{ABC} \overline{A\bar{K}} \overline{B\bar{K}} \overline{C\bar{K}}}$$

Implement with NAND Gates

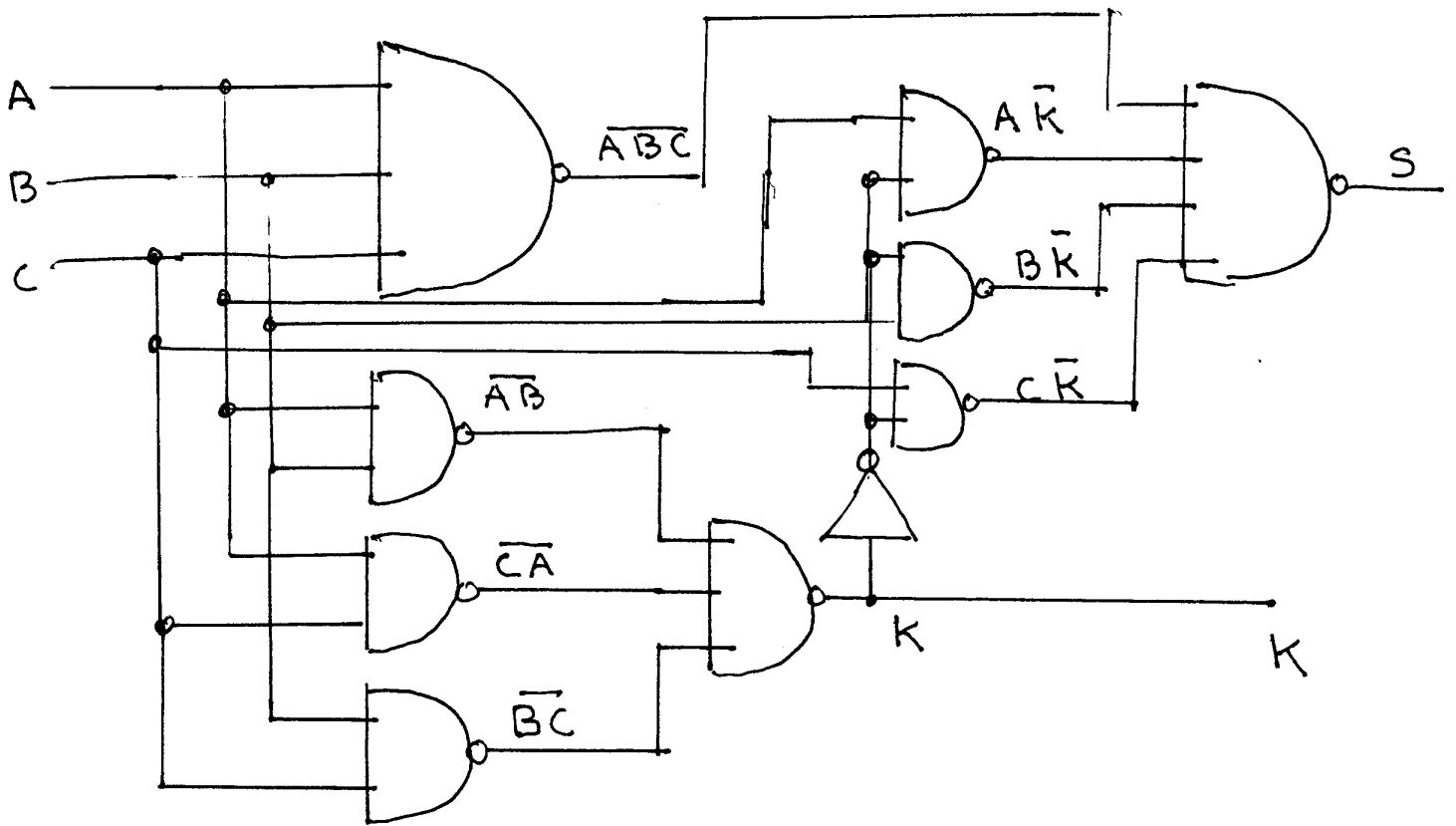

## NAND Gate Implementation

2<sup>nd</sup> implementation

$$S = (A \oplus B) \bar{C} + C(A \oplus \bar{B}) = (A \oplus B) \oplus C$$

$$= (A \oplus B) \bar{C} + \overline{(A \oplus B)} C$$


Note 2<sup>nd</sup> term is equal to  $C(A\bar{B} + B\bar{A})$  ←

$$= C \overline{A\bar{B} B\bar{A}} = C (\bar{A} + B)(\bar{B} + A)$$

$$= C(\bar{A}\bar{B} + BA + \underbrace{\bar{A}A}_0 + \underbrace{B\bar{B}}_0)$$

$$K = AB + AC + BC$$
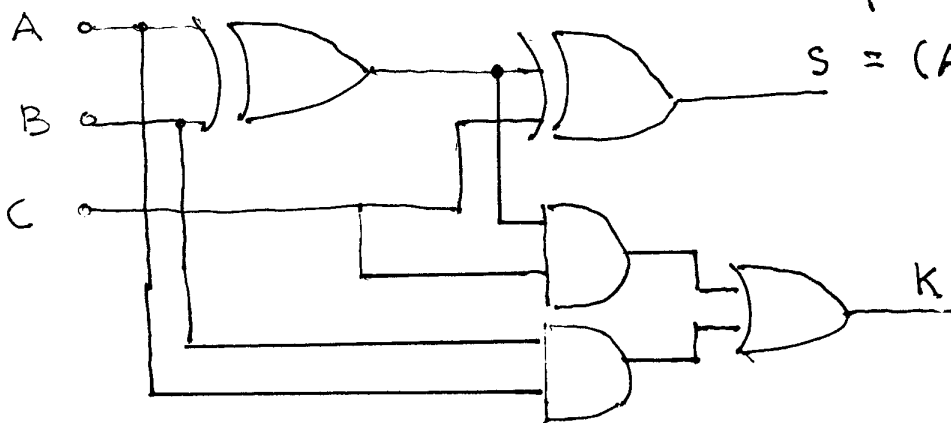
$$= AB + C(A \oplus B) \quad (\text{see Karnaugh map previous page})$$



$$S = (A \oplus B) \oplus C$$

But must

implement the  
exclusive OR

$$K = AB + C(A \oplus B)$$

Wikipedia

Gives This