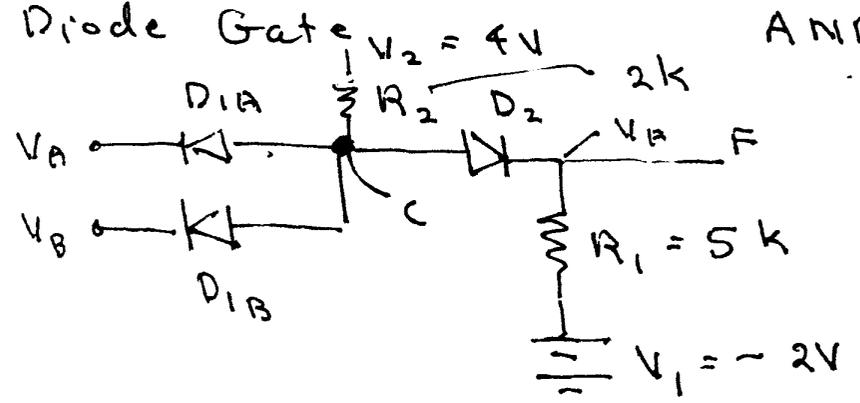


3) Diode Gate AND Gate (Diode Gate)



$V_2 + V_1 > 0$

$F = 2.9 (G+S)$

And Gate


Determine  $V_F$  for

a)  $V_A = -2V$   $V_B = -2V$

$D_{1A}, D_{1B}$  on  $V_C = 0.9V$   $D_2$  on  
 $V_F = 0.2V$  (low)

b)  $V_A = 4 = V_B = 4V$   $D_{1A}, D_{1B}$  off.  
 $V_F = [(6 - 0.7) / 7] \times 5 - 2 = \frac{5.3 \times 5}{7} - 2 = 2.25 - 2 = 0.25$  Volts

OR gate

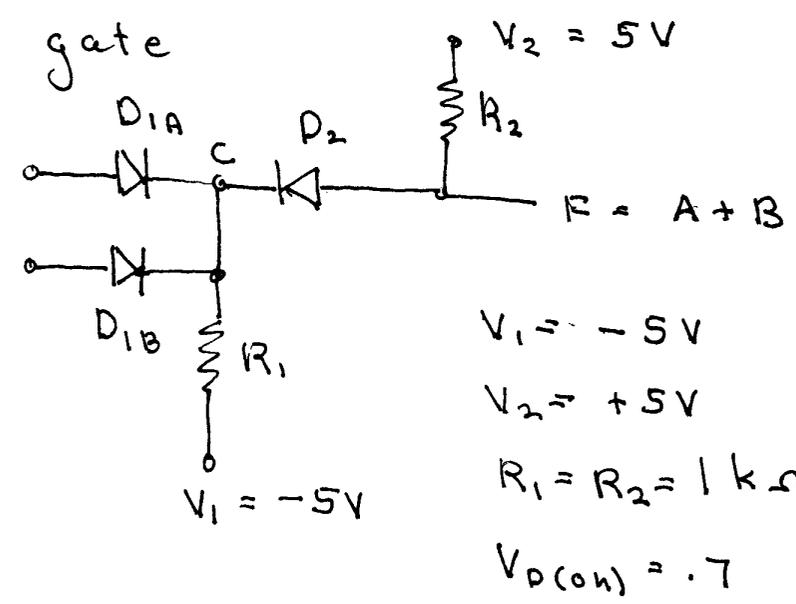

(Diode Gate)

$V_1 = -5V$   
 $V_2 = +5V$   
 $R_1 = R_2 = 1k\Omega$   
 $V_D(on) = 0.7$

$A = 1V$   $B = 1V$  - low  $D_{1A}, D_{1B}$  off



$D_2$  on current =  $\frac{10}{2k\Omega} = 5mA$

$V_F = 5 - 5 = 0$

$A = 4V$  ,  $B = 1V$  -  $D_{1A}$  on  $D_{1B}$  off


$V_C = 3.3V$   $V_F = 4V$
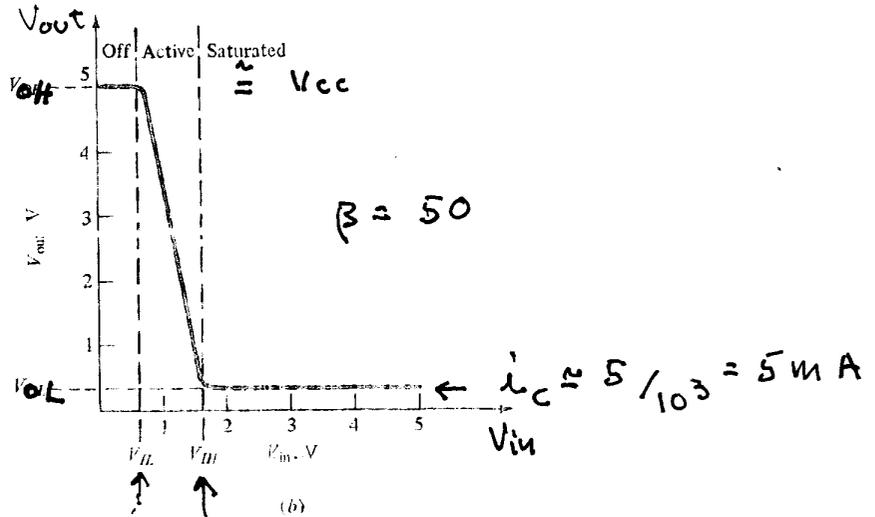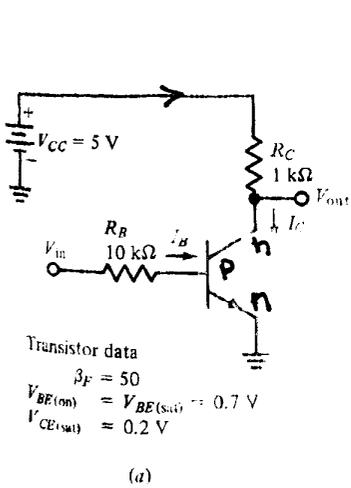
# Transistor Inverter - Digital Application



$I_C \approx I_B = 0$   
 base just barely on  
 $\therefore V_{in} \approx 0.7 \text{ V}$

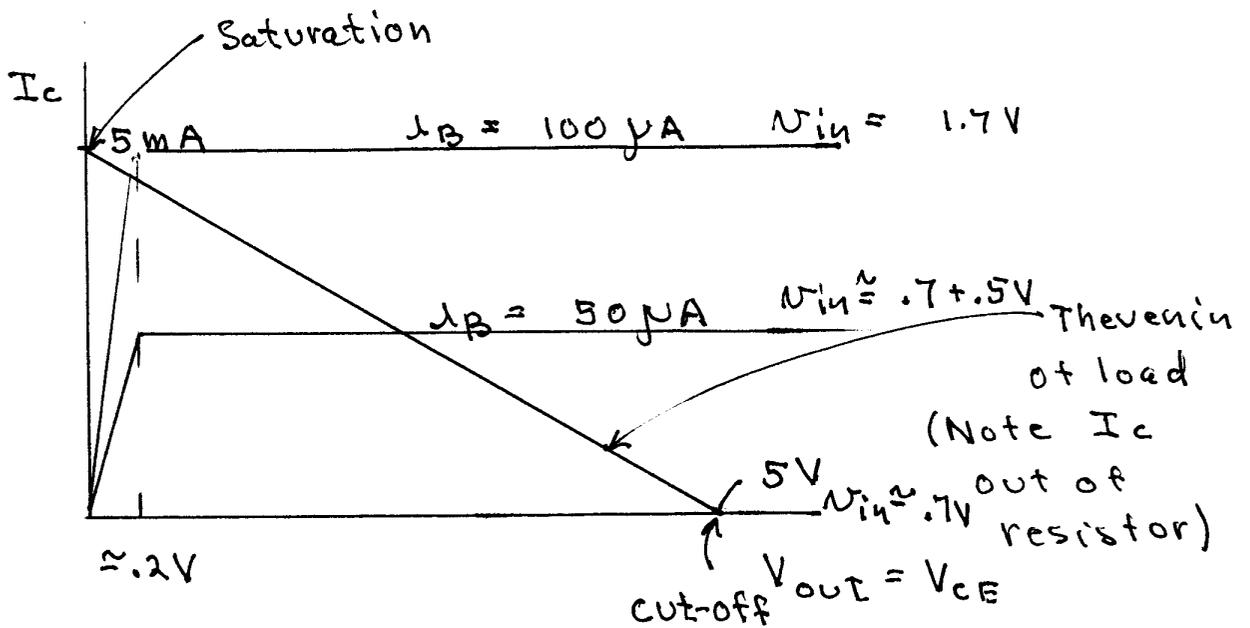$I_C \approx 5 \text{ mA} = I_B \beta$   
 $\therefore I_B \approx \frac{5 \text{ mA}}{50} = 100 \mu\text{A}$   
 $V_{in} \approx 0.7 + 10 \text{ k}\Omega \times 100 \times 10^{-6}$   
 $\approx 0.7 + 1 \approx 1.7 \text{ V}$



# The NOR (or NAND) Gate

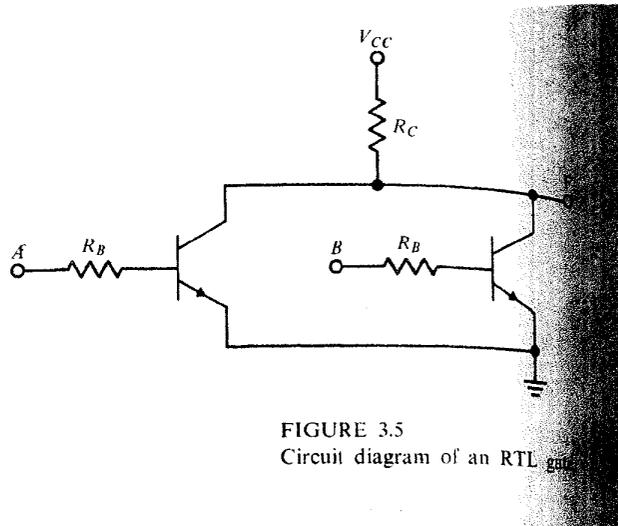


FIGURE 3.5  
Circuit diagram of an RTL gate

Voltage level HIGH = H LOW = L		
A	B	F
L	L	H
L	H	L
H	L	L
H	H	L

(a)

Positive logic H = 1 L = 0		
A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

(b)

Negative logic L = 1 H = 0		
A	B	F
1	1	0
1	0	1
0	1	1
0	0	1

(c)

NOR

NAND

$$F = \overline{A + B}$$

$$F = \overline{A B}$$

By De Morgans Th =  $\overline{A} \overline{B}$

$$= \overline{A} + \overline{B}$$

Example  $V_{BE(sat)} = 0.7V$


$$V_{CE(sat)} = 0.2V$$

$$\beta_F = 50$$

$$R_B = 1k\Omega$$



$$V_{CC} = 3V$$

$$R_C = 2k\Omega$$

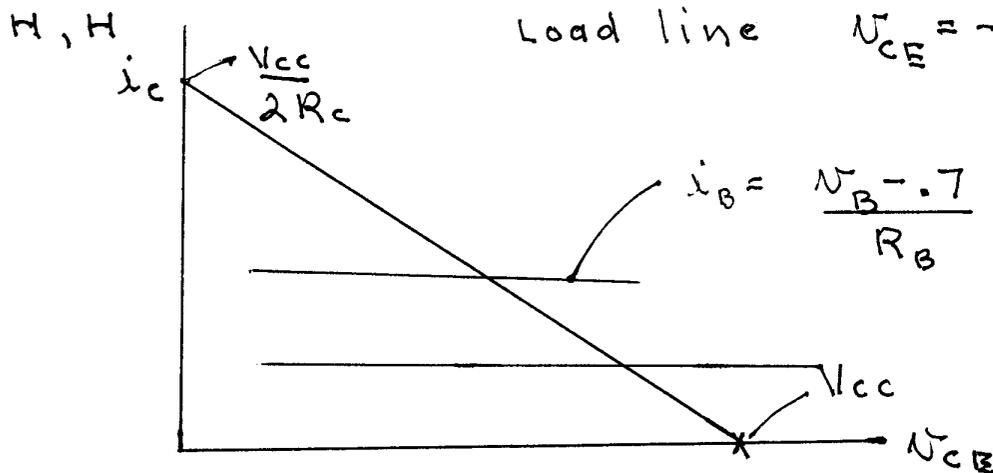

MOS Inverter  
Passive Load

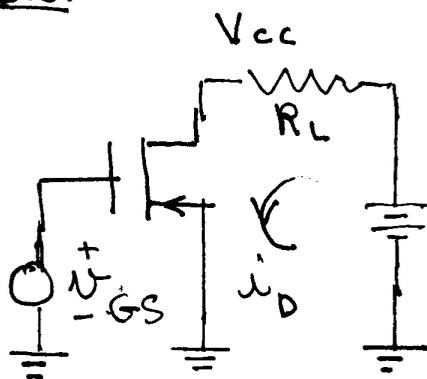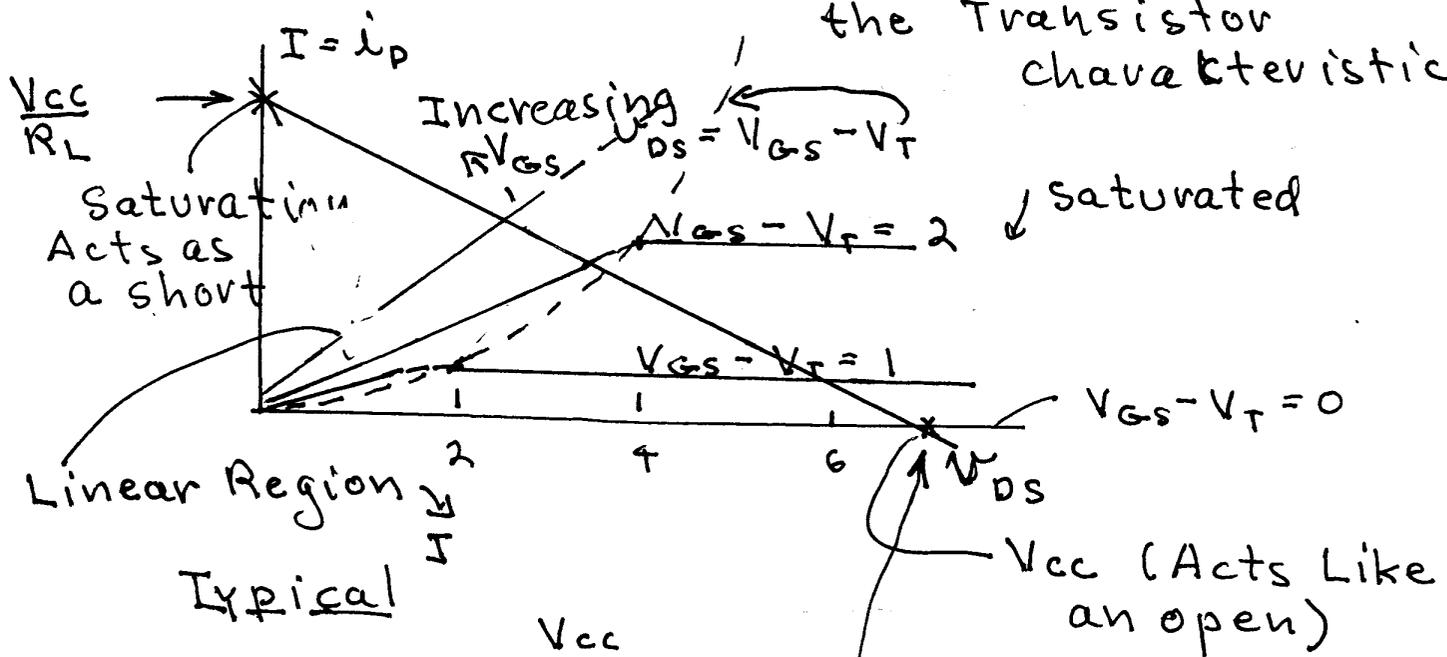
Thevenin of Load on  
the Transistor  
characteristic



KVL  
 $V_{DS} = -R_L i_D + V_{CC}$   
 when  $V_{DS} = 0$

$$i_D = \frac{V_{CC}}{R_L}$$

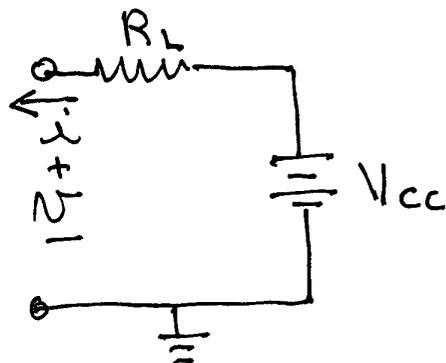The line, which is the Thevenin equivalent of the load circuit is called the "load line". Its simply this



The negative slope is simply the opposite reference for current

The solution approach is the same as for the diode but we can now "move" the solution with  $V_{GS}$