
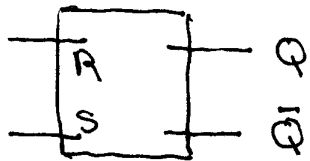


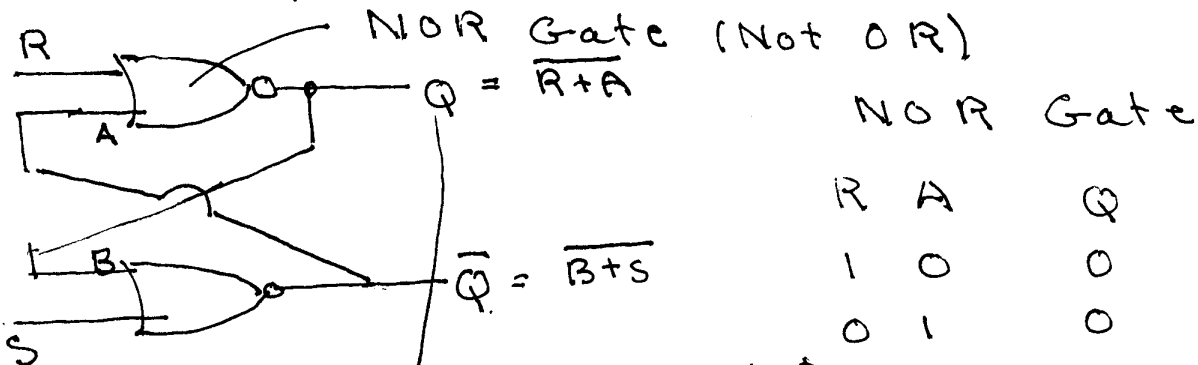RS Flip-Flop - Simple Digital Design using NOR Gates



R	S	Q_{n+1}	\bar{Q}_{n+1}
0	0	Q_n	Q_n ← Doesn't change
1	0	low	high
0	1	high	low
1	1	↔ Avoid	

Simple Implementation




1st NOR $Q = R + A = \bar{R} \bar{A} = \bar{R} \bar{Q} = \bar{R} (\overline{B+S}) = \bar{R} (B+S)$

2nd NOR $\bar{Q} = \overline{S+B} = \bar{S} \bar{B} = \bar{S} \bar{Q} = \bar{S} (\overline{R+A}) = \bar{S} (R+\bar{A})$

Example Application


Simple De-Bouncer

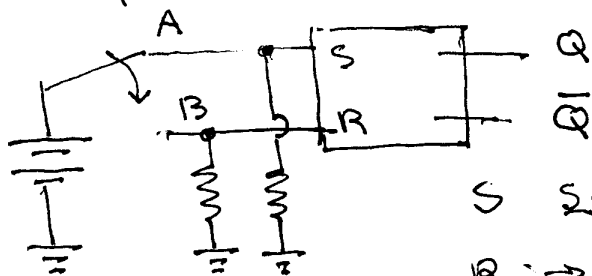

S set goes to 0 permanently
 R → resets \bar{Q} to 1 and Q to 0. Bounce at B does not matter since 0, 0 does nothing

R	S	Q	\bar{Q}
1	0	0	1
0	1	1	0
0	0	No Change	
1	1	Avoid	


The Clocked RS Flip-Flop

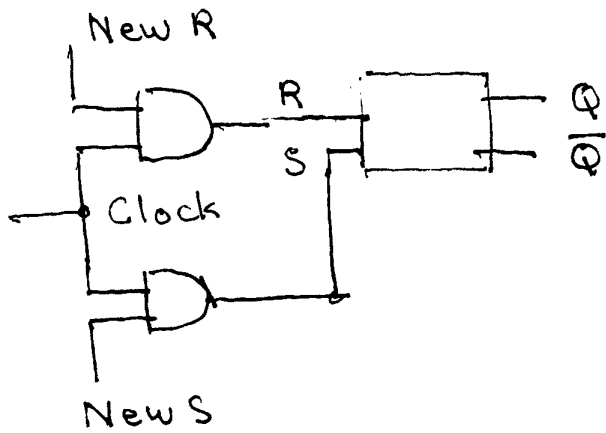

Can also include a Clear and a Preset as inputs on NOR Gates of RS

Other types of Flip-Flops

J K Flip-Flop

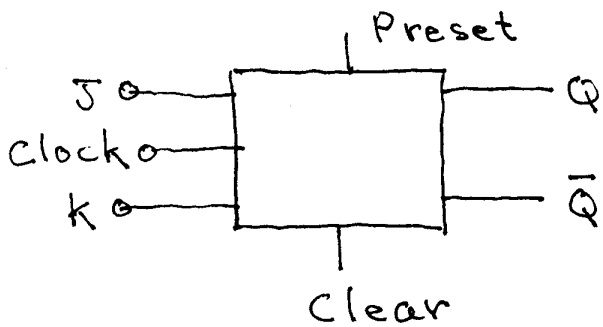


J	K	Q_n	After Pulse Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


Applications: Frequency division
Ripple Counter.
Shift Registers.

State Diagrams - Example - 2 bit binary counter

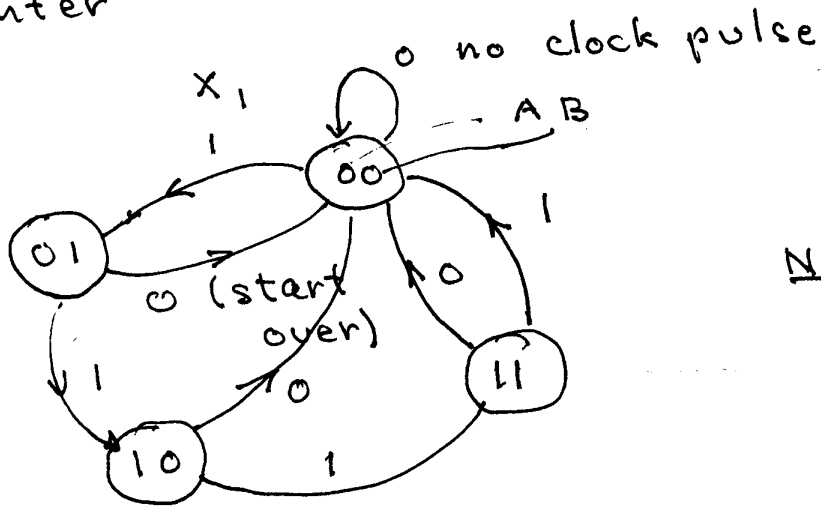State Diagram For the 2 bit binary counter



Need 2 flip-flops

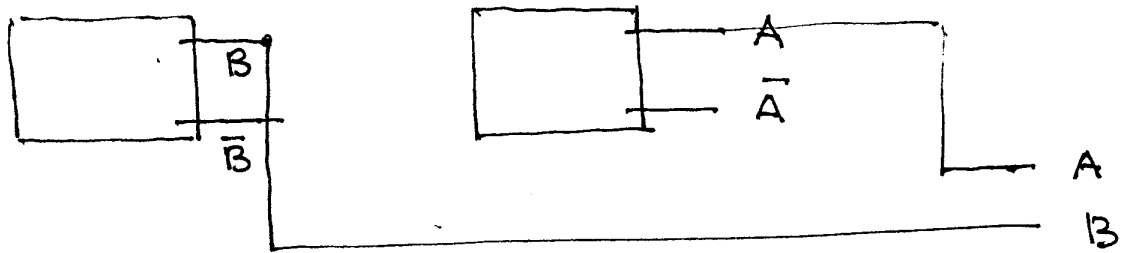

Excitation Table

Present State		X_1	Next State		FF Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	x	0	x	
0	0	1	0	1	x	1	x	
0	1	0	0	0	x	x	1	
0	1	1	1	0	x	x	1	
1	0	0	0	0	x	1	0	
1	0	1	1	1	x	0	1	
1	1	0	0	0	x	1	x	
1	1	1	0	0	x	1	x	

Now use Kar naugh Maps for J_A and J_B , K_A & K_B

X_1 / $\begin{matrix} \text{A} \\ \text{B} \end{matrix}$ present state

	00	01	11	10
0			X	X
1		1	X	X

$$J_A = B X_1$$

Similarly

$$K_A = \bar{X}_1 + B = \overline{X_1 \bar{B}}$$

$$J_B = X_1$$

$$K_B = B$$

