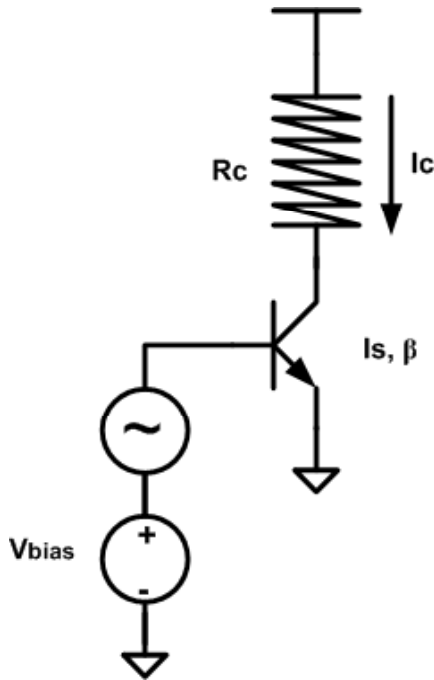


# Part 1. Temperature Variation of CE Amplifier



Assume  $R_c \gg r_o$ ,

$$A_v = g_m \cdot R_c$$

$$A_v = \frac{I_c}{V_{th}} \cdot R_c$$

$$A_v = \frac{I_s \cdot e^{V_{bias}/V_{th}}}{V_{th}} \cdot R_c$$

$$S_{\Delta T} = \frac{\partial A_v}{\partial T} \cdot \frac{T}{A_v} = \frac{T \cdot I_s}{A_v} \cdot \frac{\partial}{\partial T} \left( \frac{e^{V_{bias}/V_{th}}}{V_{th}} \cdot R_c \right)$$

$$S_{\Delta T} = \frac{T \cdot R_c \cdot I_s}{A_v} \cdot \left[ \frac{V_{bias} \cdot e^{V_{bias}/V_{th}}}{V_{th}^3} - \frac{e^{V_{bias}/V_{th}}}{V_{th}^2} \right] \cdot \left( -\frac{k}{q} \right)$$

Assume  $V_{bias} \gg V_{th}$ ,

$$S_{\Delta T} \approx -\frac{T \cdot R_c \cdot I_s}{A_v} \cdot \frac{V_{bias} \cdot e^{V_{bias}/V_{th}}}{V_{th}^3} \cdot \frac{k}{q}$$

$$S_{\Delta T} \approx -\frac{T}{A_v} \cdot \frac{V_{bias}}{V_{th}} \frac{g_m R_c}{T}$$

$$S_{\Delta T} \approx -\frac{V_{bias}}{V_{th}}$$


Example: Suppose that at room temperature, 27C, the common emitter amplifier is biased at  $V_{BE}=0.75V$ , the measured gain is -100. Estimate the gain at 28C.

$$S_{\Delta T} = \frac{\Delta A_v}{A_v} \cdot \frac{T}{\Delta T} = -\frac{V_{BE}}{V_{th}}$$
$$\frac{\Delta A_v}{-100} \cdot \frac{300K}{1K} \approx -\frac{750mV}{25mV} = -30$$

$$\Delta A_v = 10$$

- The gain under  $T=28C$  is:  $A_v' = -90$
- The gain drops 10% when temperature increases by 1C

# Temperature Variation of CE Amplifier

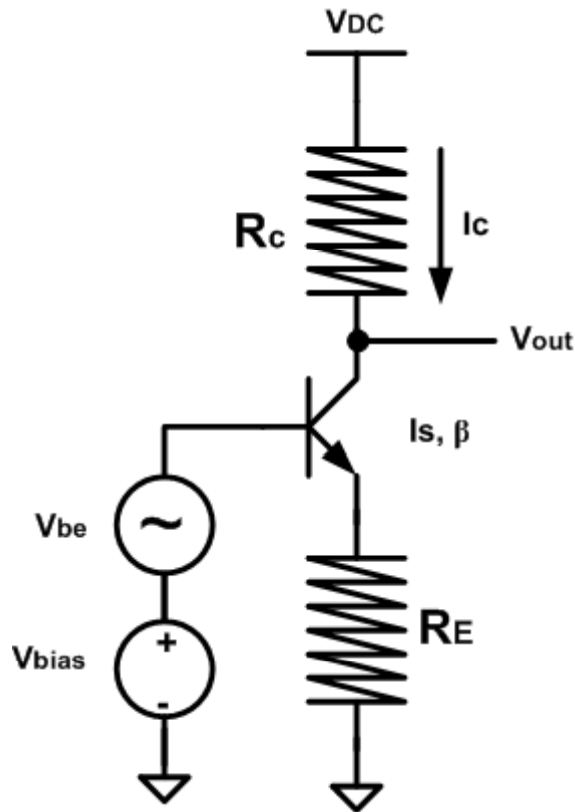

Ignore \$r\_o\$, use small signal analysis,

$$A_v = - \frac{g_m R_c}{1 + g_m R_E + \frac{R_E}{r_\pi}} \quad (\text{Exercise to verify})$$

$$A_v = - \frac{g_m R_c}{1 + g_m R_E (1 + 1/\beta)} \approx - \frac{g_m R_c}{1 + g_m R_E}$$

$$S_{\Delta T} = \frac{1}{(1 + g_m R_E)^2} \cdot \frac{T \cdot R_c}{g_m R_c} \cdot \frac{\partial g_m}{\partial T}$$

$$S_{\Delta T} = \frac{\partial A_v}{\partial T} \cdot \frac{T}{A_v} = \frac{T}{A_v} \cdot \frac{\partial}{\partial T} \left( \frac{g_m R_c}{1 + g_m R_E} \right)$$

$$S_{\Delta T} = \frac{\partial A_v}{\partial T} \cdot \frac{T}{A_v} = \frac{T \cdot R_c}{A_v} \cdot \left[ \frac{1}{(1 + g_m R_E)} - \frac{g_m R_E}{(1 + g_m R_E)^2} \right] \frac{\partial g_m}{\partial T}$$

$$S_{\Delta T} = \frac{\partial A_v}{\partial T} \cdot \frac{T}{A_v} = \frac{T \cdot R_c}{A_v} \cdot \frac{1}{(1 + g_m R_E)^2} \frac{\partial g_m}{\partial T}$$

(Next page)

Plug Av into the formula,

$$S_{\Delta T} = \frac{1}{(1 + g_m R_E)^2} \frac{T \cdot R_c}{g_m R_c} \frac{\partial g_m}{\partial T}$$

$$S_{\Delta T} = \frac{1}{(1 + g_m R_E)} \underbrace{\left[ \frac{\partial g_m R_c}{\partial T} \cdot \frac{T}{g_m R_c} \right]}$$

This term is exactly the  $S_{\Delta T}$  of  
Common emitter amplifier in  
part 1

$$S_{\Delta T} = \frac{1}{(1 + g_m R_E)} S_{\Delta T, CE}$$

Comparing to Common Emitter Amplifier

- The emitter degeneration reduce the gain by a factor of  $(1+g_m R_E)$
- The emitter degeneration reduce the thermal sensitivity also by the same factor of  $(1+g_m R_E)$