

Read Sections Sections 4.1–6 and 4.8 in Alexander & Sadiku.

1. Redo Example 4.4 in Alexander & Sadiku for the following component values: $20\text{ V} \rightarrow V_1 = \quad \text{V}$, $4\text{ A} \rightarrow I_1 = \quad \text{mA}$, $1\ \Omega \rightarrow R_1 = \quad \text{k}\Omega$, $2\ \Omega \rightarrow R_2 = \quad \text{k}\Omega$, $3\ \Omega \rightarrow R_3 = \quad \text{k}\Omega$, $4\ \Omega \rightarrow R_4 = \quad \text{k}\Omega$ and $5\ \Omega \rightarrow R_5 = \quad \text{k}\Omega$.

$i_o = \quad \quad \quad \begin{matrix} 4\text{ pts.} \\ 0 \end{matrix}$




2. Redo Example 4.8 in Alexander & Sadiku for the following component values: $32\text{ V} \rightarrow V_1 = \quad \text{V}$, $2\text{ A} \rightarrow I_1 = \quad \text{mA}$, $1\ \Omega \rightarrow R_1 = \quad \text{k}\Omega$, $4\ \Omega \rightarrow R_2 = \quad \text{k}\Omega$, $12\ \Omega \rightarrow R_3 = \quad \text{k}\Omega$.

$i_{R_L}(R_L = 1\ \text{k}\Omega) = \quad \quad \quad \begin{matrix} 2\text{ pts.} \\ 1 \end{matrix}$
 $i_{R_L}(R_L = 4\ \text{k}\Omega) = \quad \quad \quad \begin{matrix} 2\text{ pts.} \\ 2 \end{matrix}$
 $i_{R_L}(R_L = 9\ \text{k}\Omega) = \quad \quad \quad \begin{matrix} 2\text{ pts.} \\ 3 \end{matrix}$

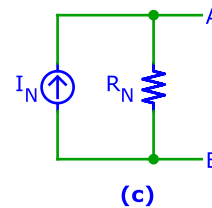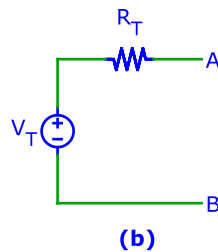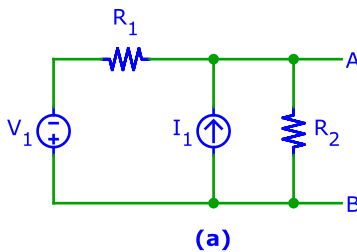3. Find component values such that all three circuits shown behave identically.

Parameter: $I_1 = \quad \text{mA}$, $V_1 = \quad \text{V}$, $R_1 = \quad \text{k}\Omega$ and $R_2 = \quad \text{k}\Omega$.

$V_T = \quad \quad \quad \begin{matrix} 1\text{ pt.} \\ 4 \end{matrix}$
 $R_T = \quad \quad \quad \begin{matrix} 1\text{ pt.} \\ 5 \end{matrix}$
 $I_N = \quad \quad \quad \begin{matrix} 1\text{ pt.} \\ 6 \end{matrix}$
 $R_N = \quad \quad \quad \begin{matrix} 1\text{ pt.} \\ 7 \end{matrix}$




4. Find an equivalent representation for the I/V characteristics at terminals A and B of the circuit below consisting of only a current source I_x and resistor R_x .

Draw the schematic of the equivalent circuit consisting of a current source I_x and resistor R_x . Label the components and terminals A and B.


Calculate the values of I_x and R_x for $I_1 = \quad \text{mA}$, $V_2 = \quad \text{V}$, $I_3 = \quad \text{mA}$, $R_1 = \quad \text{k}\Omega$, $R_2 = \quad \text{k}\Omega$, and $R_3 = \quad \text{k}\Omega$.

$I_x =$ 1 pt.
 $R_x =$ 8
1 pt.
9

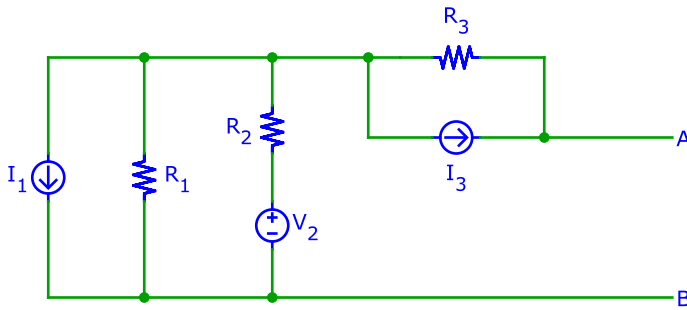

5. Calculate the value of current i_x . Parameter $I_1 = \quad \text{mA}$, $V_2 = \quad \text{V}$, $V_3 = \quad \text{V}$, $R_1 = \quad \text{k}\Omega$, $R_2 = \quad \text{k}\Omega$, $R_3 = \quad \text{k}\Omega$ and $R_4 = \quad \text{k}\Omega$.

$i_x =$ 12 pts.
10

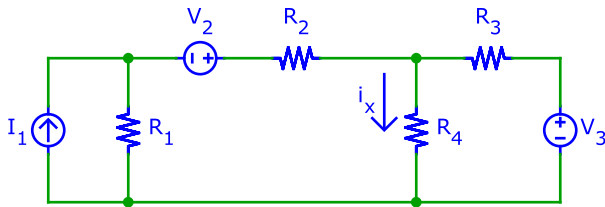

6. For evaluation, circuit (a') is temporarily connected to circuit (a) and the following measurements are taken with the ampère- and volt-meters shown in circuit (a') (for different values of R_L):


- i) $V = \quad \text{V}$ $A = \quad \text{mA}$
- ii) $V = \quad \text{V}$ $A = \quad \text{mA}$

a) Determine the values of V_T and R_T such that circuits (a) and (b) behave identically.

$V_T =$ opt.
 $R_T =$ 11
opt.
12


b) The apprentice is asked to verify the measurement, but inadvertently mixes up the volt- and ampère-meters. What readings does he get when redoing measurement (i) above? Use the values from part (a) for V_T and R_T .

$V =$ opt.
 $A =$ 13
opt.
14

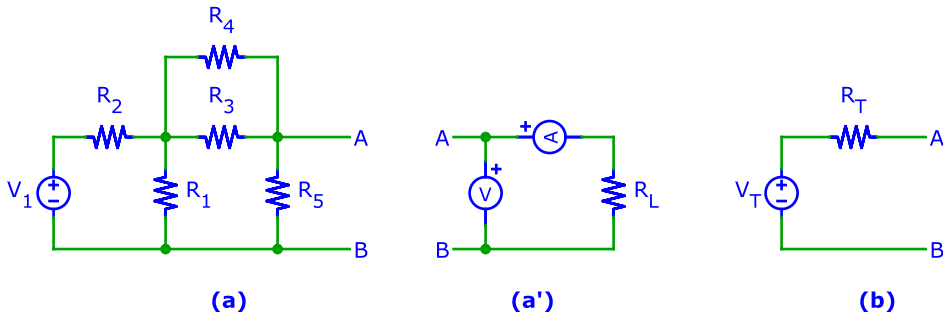

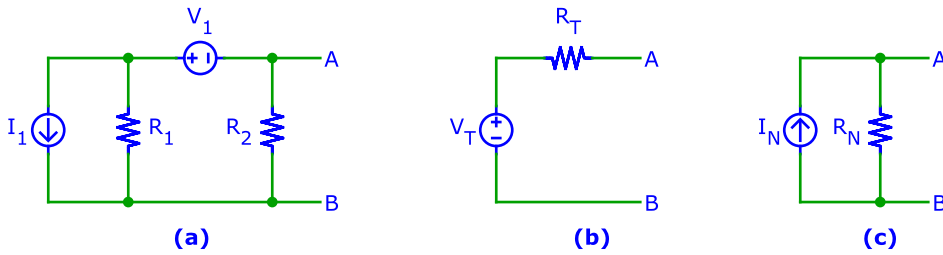
7. Find component values such that all three circuits shown behave identically. Given: $I_1 = \quad \text{mA}$, $V_1 = \quad \text{V}$, $R_1 = \quad \text{k}\Omega$ and $R_2 = \quad \text{k}\Omega$.

$V_T =$ opt.
15
 $R_T =$ opt.
16
 $I_N =$ opt.
17
 $R_N =$ opt.
18




8. Find the value of current i_2 . Parameters: $V_1 = \quad \text{V}$, $I_1 = \quad \text{mA}$, $R_1 = \quad \text{k}\Omega$, $R_2 = \quad \text{k}\Omega$, $R_3 = \quad \text{k}\Omega$, $R_4 = \quad \text{k}\Omega$. Hint: Use source transformation.

$i_2 =$ opt.
19

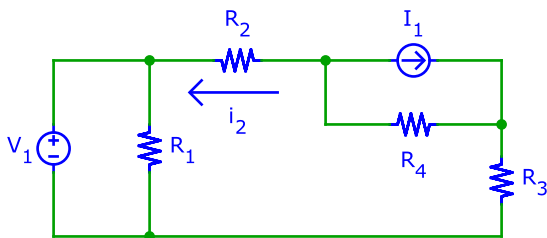

9. Find the Thevenin equivalent for port A-B in the circuit shown below. Use the following component values: resistors $\quad \text{k}\Omega$, voltage sources $\quad \text{V}$, current sources $\quad \text{mA}$.

$V_T =$ opt.
20
 $R_T =$ opt.
21

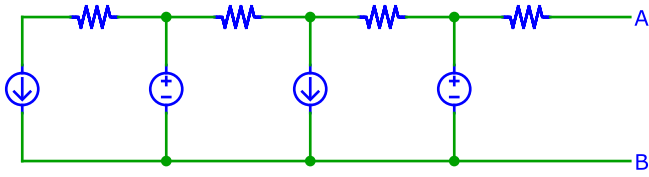

Password:
