

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**

**B. E. BOSER**


**Problem Set 4**  
**Due Tuesday, February 19, 2008**

**EE 42 / 100**  
**Spring 2008**


In problems you are asked to verify your result with a circuit simulator. Please follow the guidelines presented in Problem Set 3 which apply to this and all future homework sets.

1. Solve problem 2 of quiz 2 for  $I_1 = 3$  A. Use the values stated in the quiz for elements not specified here.
2. Quiz 2, problem 4: Find the value of  $I_3$  for  $V_1 = 5$  V.
3. Quiz 2, problem 7: Find the value of  $R_{eq}$  for  $R_2 = 10$  k $\Omega$ .
4. Quiz 2, problem 7: Find the value of  $R_3$  for  $R_{eq} = 5$  k $\Omega$ ,  $R_1 = 1$  k $\Omega$ , and  $R_2 = 10$  k $\Omega$ .
5. Quiz 2, problem 9: Find the power dissipated in  $R_2$ .
6. Problem 4.6 in Nilsson and Riedel, 8<sup>th</sup> edition
7. Problem 4.15 and verify your solution with circuit simulation. The simulator output (operating point analysis) should include a list of all node voltages and branch currents.  
Suggestion: Use a program (e.g. Matlab) to solve the equations numerically.
8. Problem 4.21 and verify your result with circuit simulation
9. Suggestion only: do the assessment problems on page 123 in Nilsson and Riedel, 8<sup>th</sup> edition
10. Draw the Thévenin and Norton equivalent circuits for the circuit shown in Figure P4.65 (in Nilsson and Riedel, 8<sup>th</sup> edition) and calculate the values of the circuit elements.
11. Problem 4.68
12. Problem 4.69

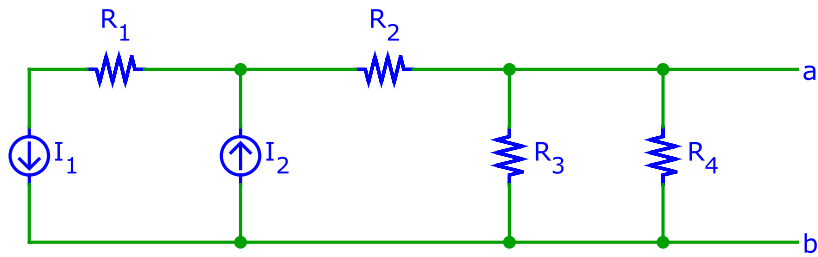
13. Find algebraic expressions for the circuit elements of a Norton equivalent circuit representing the behavior at terminals a-b of the circuit shown below.



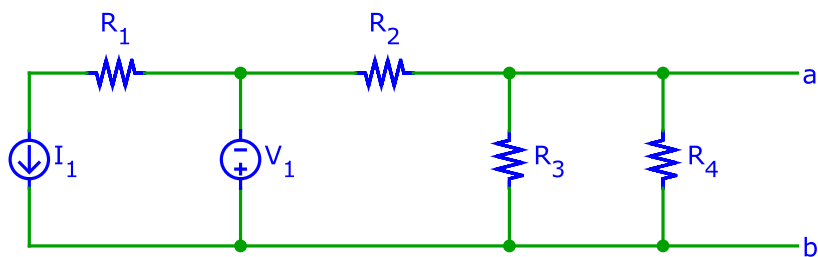14. Find algebraic expressions for the circuit elements of a Thévenin equivalent circuit representing the behavior at terminals a-b of the circuit shown below.



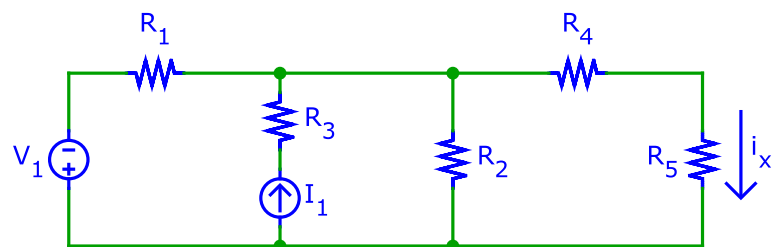15. Find an algebraic expression for  $i_x$ . Simplify your result as much as possible (e.g. no fractions of fractions).



16. Assume that the operational amplifier in the circuit below is ideal.

- (a) Find an expression for voltage  $v_x$ .  
 (b) Find an algebraic expression for the value of the voltage gain,  $\frac{v_o}{v_i}$ . Simplify your result as much as possible (e.g. no fractions of fractions).

