

# Electronics for IoT

## Electricity

Bernhard E. Boser

University of California, Berkeley

[boser@eecs.berkeley.edu](mailto:boser@eecs.berkeley.edu)

# Electricity

---

Topics:

- Characteristics
- Metrics (voltage, current)
- Measure
- Devices
- Circuits

# Electricity

---



# Electricity

---

- Charged particles
  - Usually electrons
- Can't see electrons
  - Only consequences of their actions



# Feel?



# Feel!



# In the EE 49 lab ...






# Water Analogy

---




# Water Analogy

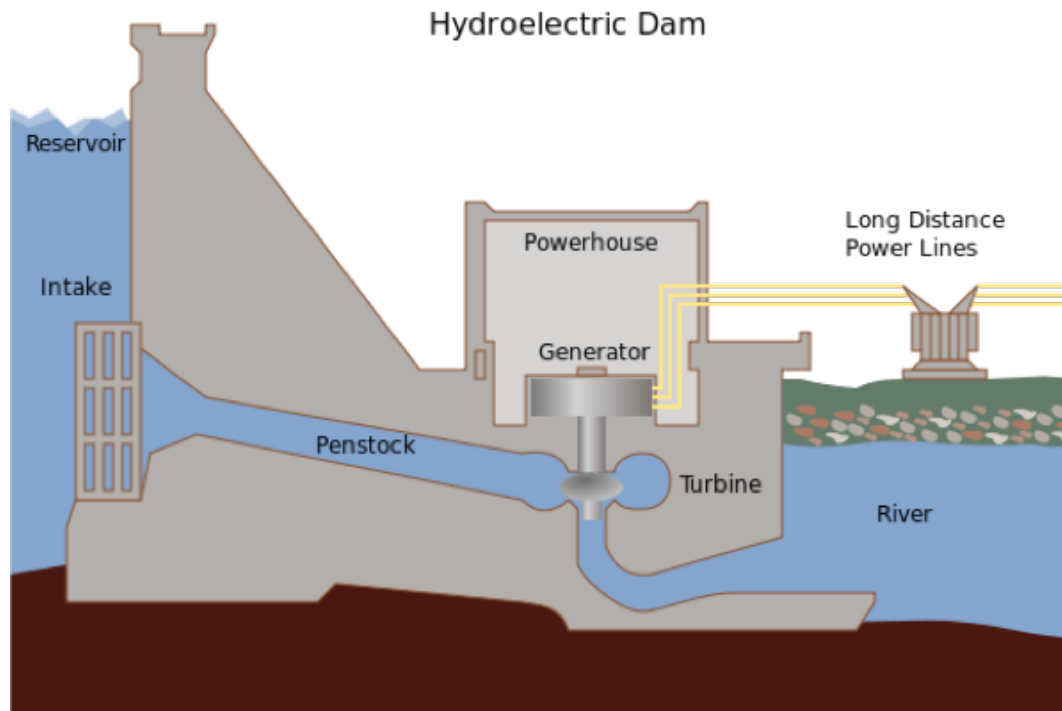

Water molecules ~ Electrons

# Voltage

Pressure [  $\text{N/m}^2$  ]

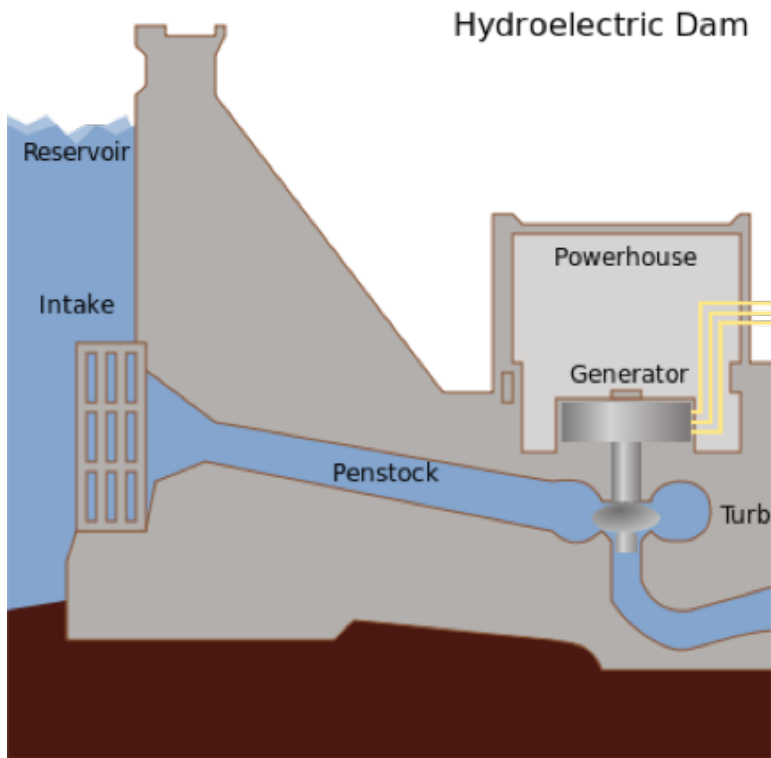

Voltage [ V ]



# Measuring Voltage

- Digital Multi-Meter
- AC versus DC
- Wires (pipes for electrons)
- Loop:
  - Electrons need to get back to where they came from
  - Water is more flexible
    - But it's also nice when it eventually comes back ...





# Experiments ... Parts!



# Parts

- Distributed to each team of two in the first lab
- You'll use them throughout the semester
- **A storage box is more convenient than the bag they come in**
- Many parts are “multi-use”: used in several labs and the project







# Electrical Circuit



# Circuit Symbols



# Circuit Symbols

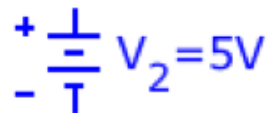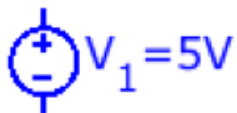


# Circuit Diagram

---

# Circuit Diagram

---

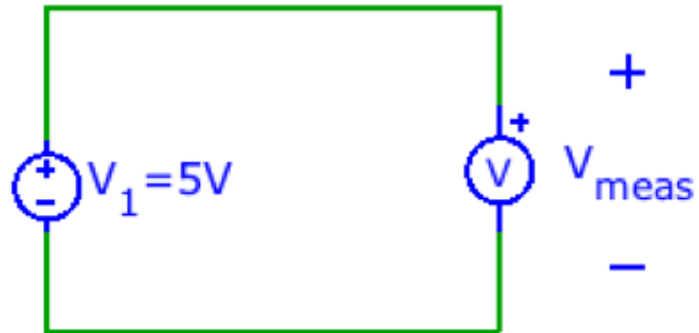




# Mixing up wires – red to black???

---



# What can we do with it?

## Spin a turbine ...

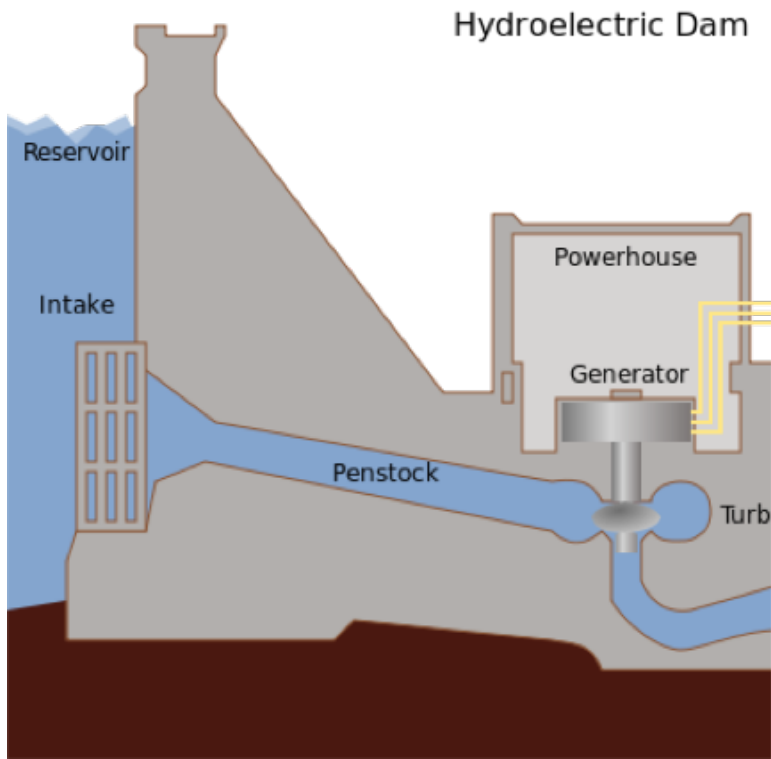


## Make “sound”





# Circuit Diagram

---

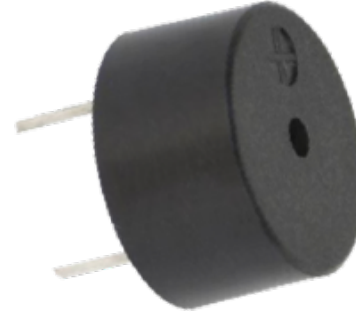

# Circuit Diagram

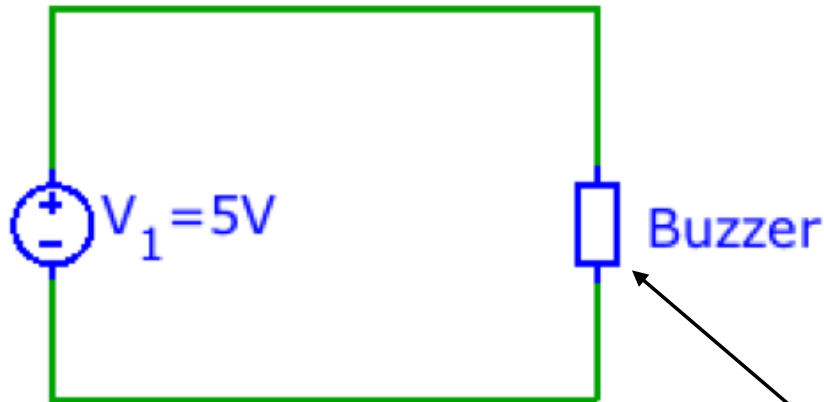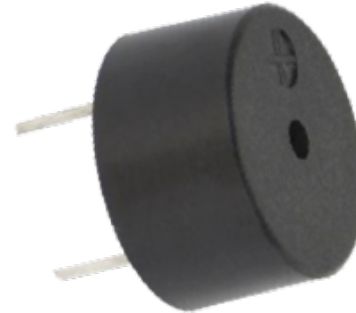

Rectangle:  
Generic circuit  
symbol

# Current

---

## Water flow


- Water molecules
- Water volume [  $\text{m}^3$  ]
- Flow [  $\text{m}^3 / \text{s}$  ]

## Current

- Electrons
- Charge [ Coulomb = C ]
- Current [  $\text{C} / \text{s} = \text{A}$  ]

# Measuring Current

Where does the meter go?

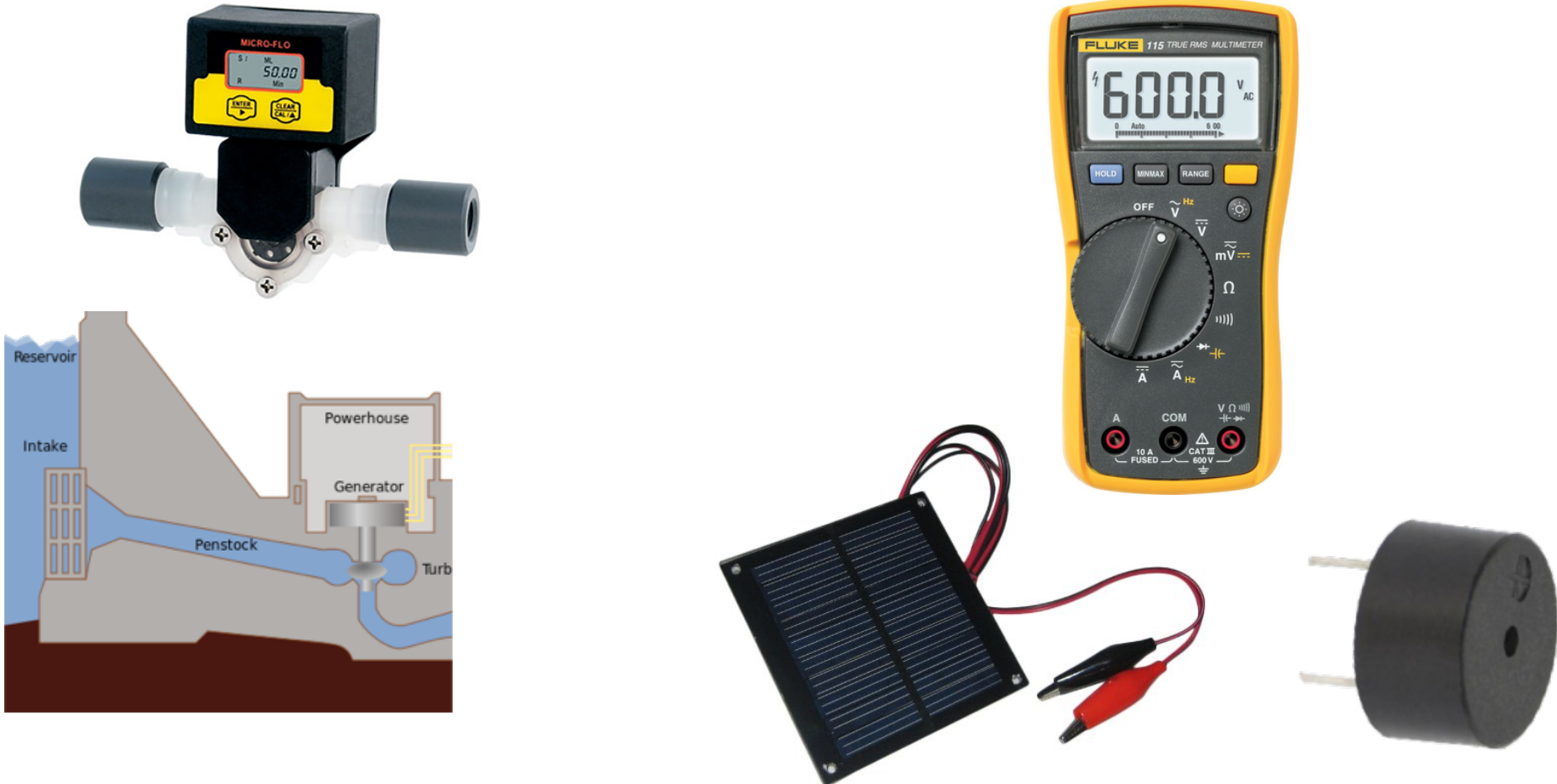


# Circuit Diagram

---





# Measuring Voltage and Current

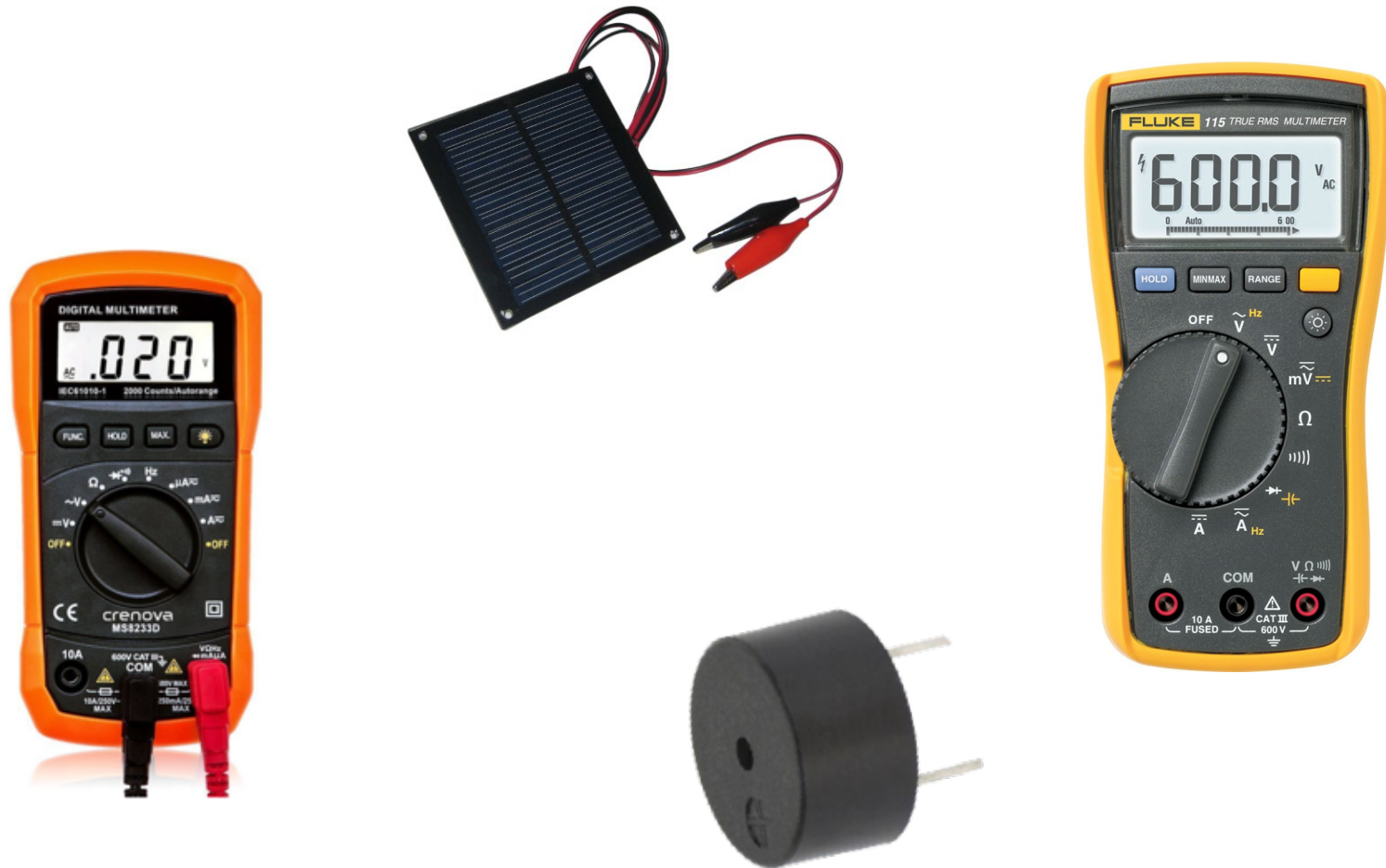

# Circuit Diagram

---


# Beyond “sound” ...

---


- What can we do with it?
  - Light the room?
  - Charge the smartphone?
  - Run the microcontroller?
  
- How can we figure that out?
  - Voltage
  - Current
  - ???

# Power

Pressure x Flow [ W ]

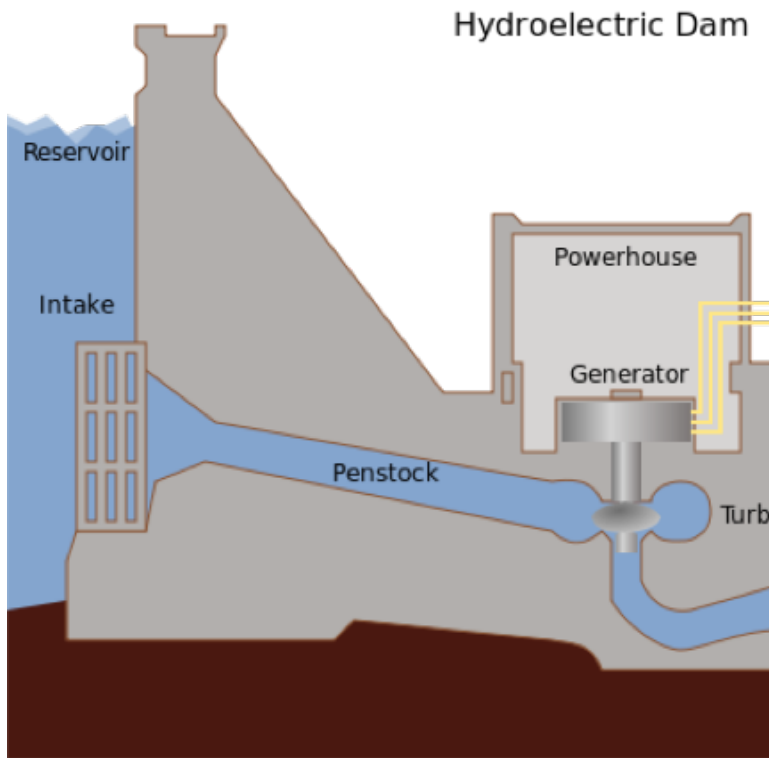



Voltage x Current [ W ]

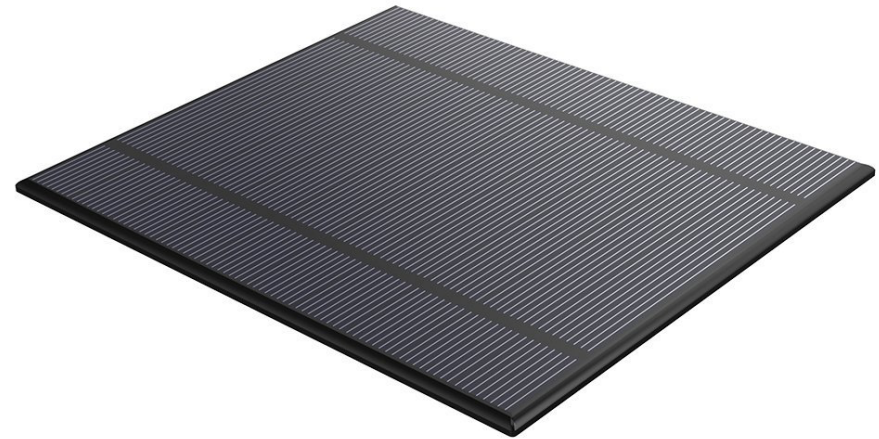

# Power



# Signal Ground

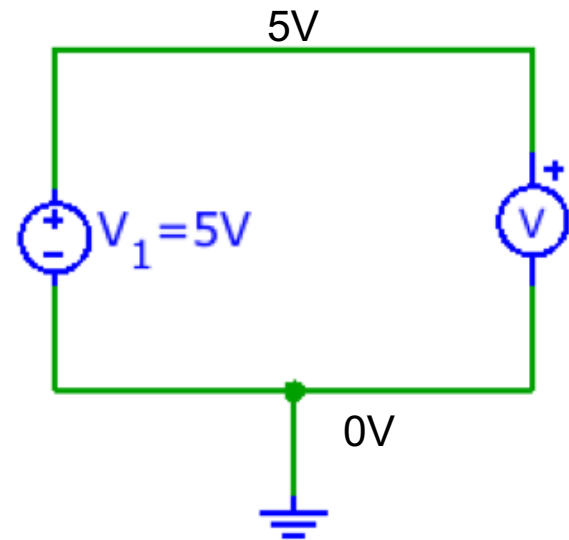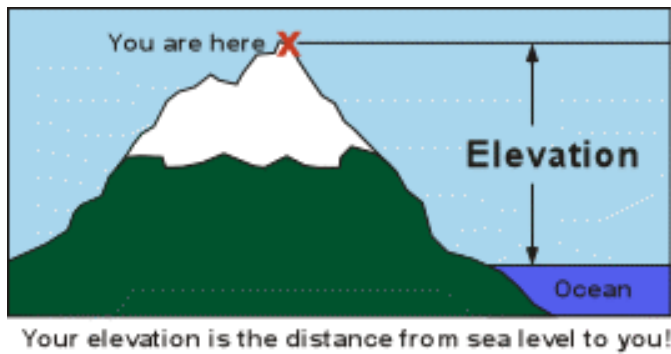



# Short Circuit




BIGSTOCK

Image ID: 180767107  
bigstock.com




# Interpretation

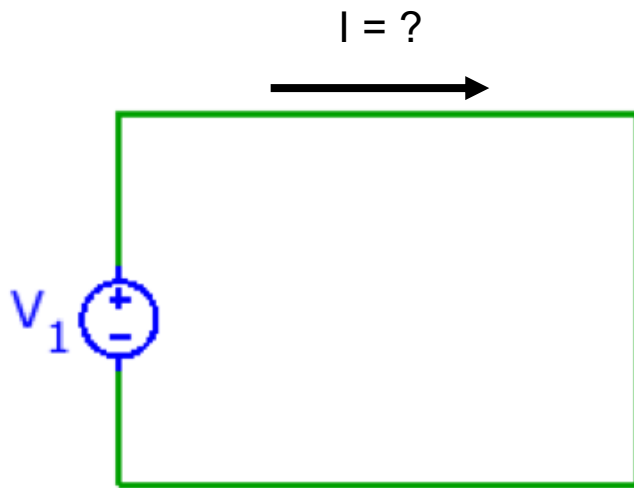

- What is the current flowing?
- Depends on source, e.g.
  - Nuclear power plant
  - Solar cell
  - ...

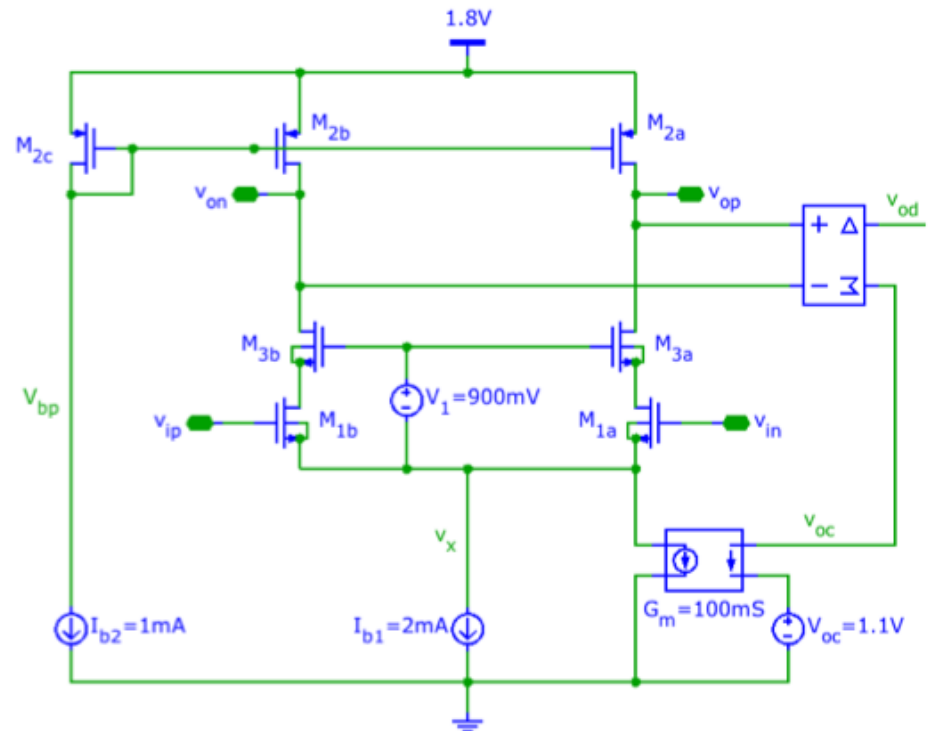
# Short Circuit Current

- “Current through wire between any two points in a circuit”
- Whether this is a good idea or not (e.g. causes fire) depends on circuit and connection points
- Common terminology used by electrical engineers
- Use ammeter to measure, behaves like short circuit (“wire”)


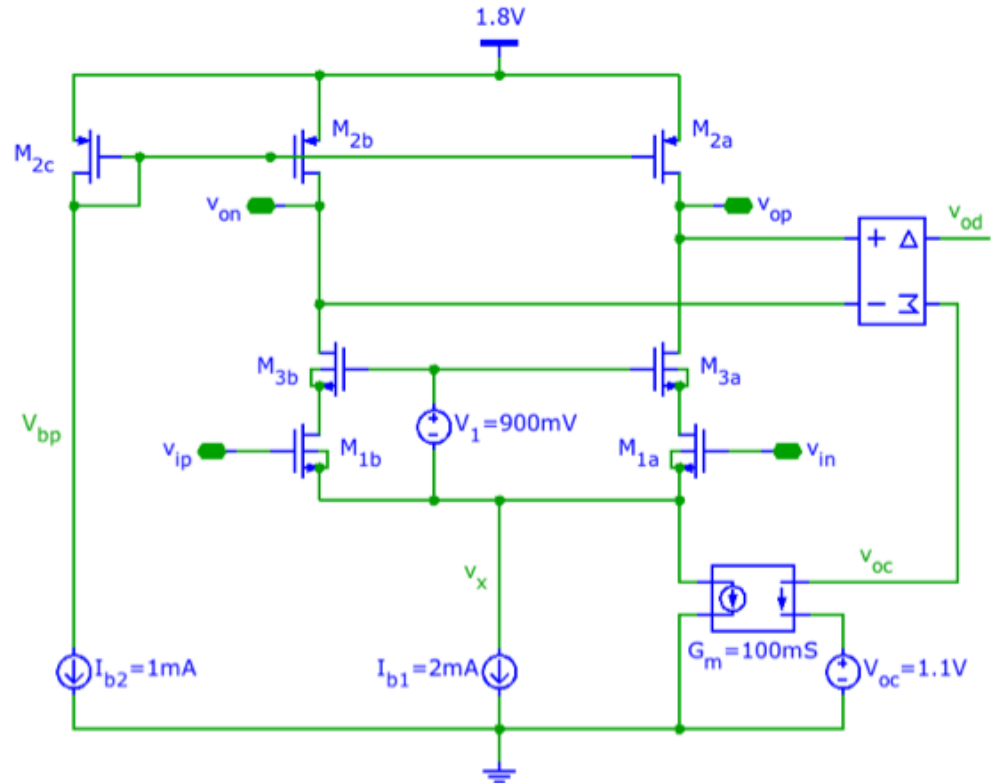
# Open Circuit Voltage

- “Voltage between any two points in a circuit without adding a wire between them”
- Note: no current flow → no sparks
- Use voltmeter to measure, behaves like open circuit (“no wire”)



# Typical Voltages

---

- Household current (ac)
- Car battery
- “Typical” Electronic circuits

# Electric Shock

- Is 5V dangerous?
- 100V?
- What about this:



# “Dangerous” Voltages

- Humans:
  - >30V if current not limited
- Integrated circuits:
  - Typical: < 5V!
  - E.g.

GPIO	ALT	μPy		μPy	ALT	GPIO
			1			
		RESET	2			
		3.3V	3			
			4			
		GND	5			
26	DAC2	A0	6			
25	DAC1	A1	7			
34	ADC6	A2	8			
39	ADC3	A3	9			
36	ADC0	A4	10			
4		A5	11			
5	SCK	A16	12			
18	MOSI	A17	13			
19	MISO	A18	14			
16		A19	15			
17		A20	16			
21		A21	17			
			18			
			19			
			20			
			255			



# Typical Currents

---

- Household
- Train
- CPU
- EE 49 circuits

# Summary

---

- Electrical quantities:
  - Voltage
  - Current
  - Power
- Components (devices):
  - Solar cell (source)
  - Buzzer
  - DMM
    - Voltage and current meter
- Circuits:
  - Symbols, diagrams
  - Short and open circuits